

Code: AE08  
Time: 3 Hours

Subject: CIRCUIT THEORY &  
Max. Marks: 100

**JUNE 2011**

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Current of 3A flows through a resistance of 20 ohms. The energy dissipated in the resistor per minute is
- (A) 1.80 W (B) 0.18 W  
(C) 3.6 W (D) 180 W
- b. A Hurwitz polynomial has
- (A) only zeros in the left half of s-plane  
(B) only poles in the left half of s-plane  
(C) zeros anywhere in s-plane  
(D) poles anywhere in s-plane
- c. The function  $Z(s)$  is  $Z(s) = s(s+3)/(s+2)(s+4)$
- (A) L-C (B) R-C  
(C) R-L (D) R-L-C network
- d. In a two port network, the condition for reciprocity in terms of h-parameters is
- (A)  $h_{12} = h_{21}$  (B)  $h_{11} = h_{22}$   
(C)  $h_{11} = -h_{22}$  (D)  $h_{12} = -h_{21}$
- e. A series RLC circuit consist of resistance 10 ohms, and inductance of 0.1H, capacitance of  $0.001 \mu\text{F}$ . The frequency at resonance
- (A)  $10^5 \text{ Hz}$  (B)  $10^7 \text{ Hz}$   
(C) 15920Hz (D) 920Hz
- f. In a linear network, the ratio of voltage excitation to current response is unilateral when the position of excitation and response are interchanged. This is
- (A) Principle of duality (B) Reciprocity theorem  
(C) Tellegan's theorem (D) Principle of superposition

- g. If the source impedance is  $3 + 4j$ , then for maximum power transfer, impedance should be
- (A) 3 (B) 4  
(C)  $3-4j$  (D)  $-4j$
- h. An RC circuit has a capacitor  $C = 2 \mu\text{F}$  in series with a resistance  $R=1\text{M}\Omega$ . The time of 6 secs will be equal to
- (A) one time constant (B) two time constant  
(C) three time constant (D) none of these
- i. Quality of a coil is defined as
- (A)  $Q = \omega L/R$  (B)  $Q = \omega C/R$   
(C)  $Q = \omega R/L$  (D)  $Q = \omega CL/R$
- j. If all the elements in a particular network are linear, then the superposition theorem would hold, when the excitation is
- (A) dc only (B) ac only  
(C) ac or dc (D) an impulse

**Answer any FIVE Questions out of EIGHT Questions.**

**Each question carries 16 marks.**

- Q.2** a. Determine  $i(0+)$ ,  $di/dt(0+)$ , and  $d^2i/dt^2(0+)$  in the given Fig.1 if  $V=10\text{ V}$ ,  $R=10\ \Omega$ ,  $L=1\text{ H}$ ,  $C=10\mu\text{F}$  and  $V_c(0)=0$ . (8)

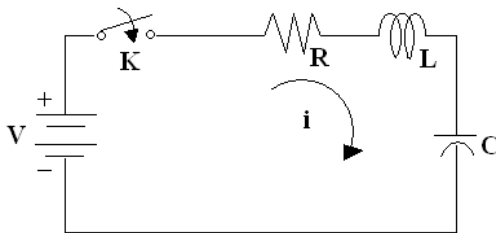


Fig.1

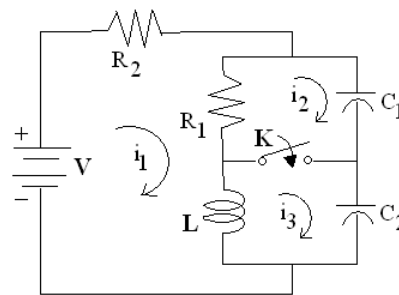


Fig.2

- b. In the given Fig.2, find the initial values of all three loop currents when a steady state is reached with the switch K open, and at  $t=0$  the switch is closed. (8)

- Q.3** a. Using Nodal analysis, find the node voltages  $V_1$  and  $V_2$  in Fig.3. (6)

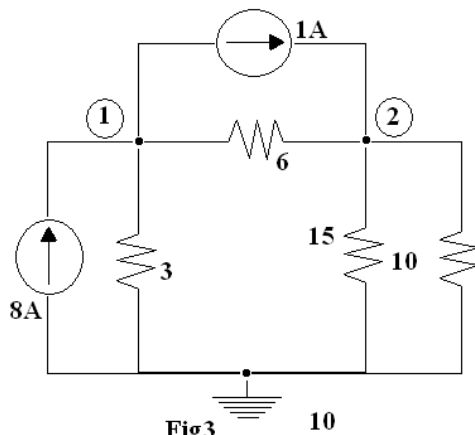


Fig3

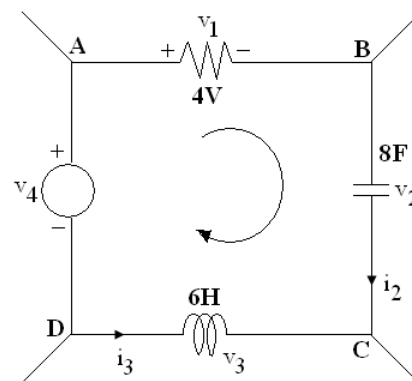


Fig.4

- b. In the network shown in Fig.4  $v_1 = 4 \text{ V}$ ,  $v_4 = 4 \cos 2t$  and  $i_3 = 2 \text{ A}$ . Determine  $i_2$ .
- c. Applying Kirchhoff's laws to different loops in Fig.5, find the values of  $V_1$  and  $V_2$ . (4)

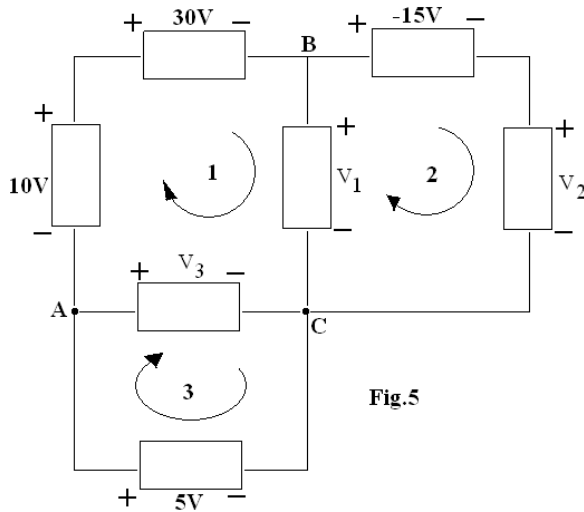


Fig.5

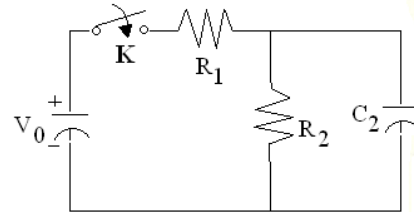


Fig.6

- Q.4** a. In the given Circuit (Fig.6) Find the current in the resistor  $R_2$ . Assuming capacitor  $C_2$  is initially uncharged. The switch  $K$  is closed at  $t=0$ . (8)
- b. In the network given in Fig.7 the switch closes at  $t=0$ . It is given that  $v(t) = 0.1 e^{-5t}$ ,  $R_2 = 2 \text{ ohms}$  and all initial currents and voltages are zero. Find the current  $i_2$  by Norton's theorem. (8)

- Q.5** a. Consider the network in Fig.8 find the values of node voltages  $V_1(t)$  and  $V_2(t)$ . Assume at  $t=0$ , switch is open. It is given that  $L=1/2 \text{ H}$ ,  $C = 1 \text{ F}$ ,  $G=1 \text{ mho}$ ,  $V=1 \text{ V}$ . (8)

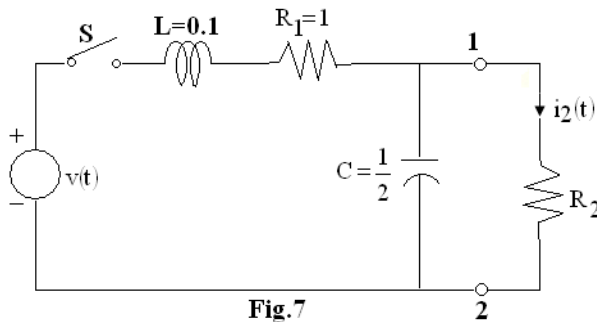


Fig.7

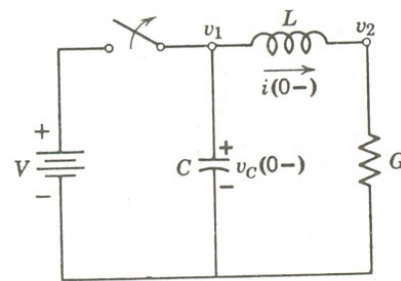


Fig.8

- b. What do you understand by sinusoidal steady state system?  
For the network of Fig.9, find  $i_2$  in the steady state if  $v_1 = \cos 2t$ , the values of  $L=1 \text{ H}$ ,  $C=1/2 \text{ F}$  and  $R=2\Omega$ . (4+4)

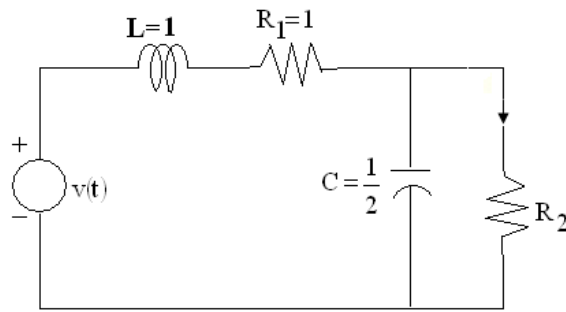


Fig.9

- Q.6**
- Calculate the following for half wave alternating current
    - Average value
    - Rms Value
    - Form factor
  - State and prove Maximum Power transfer theorem. Give its applications also. With the help of superposition theorem, obtain the value of current  $I$  and voltage  $V_o$  in the Fig.10. (4+4)

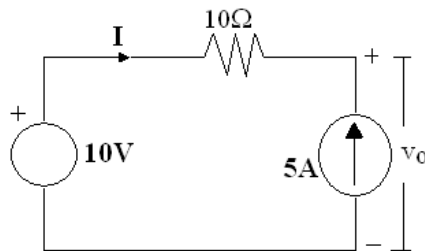


Fig.10

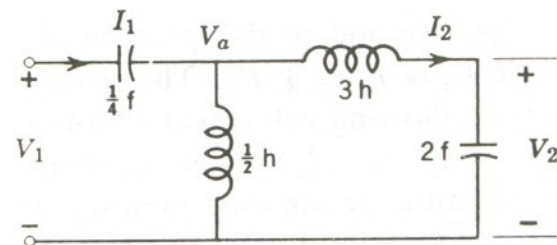


Fig.11

- Q.7**
- Find the voltage ratio  $V_2/V_1$ , the current ratio  $I_2/I_1$ , input impedance  $Z_1$  and the transfer impedance  $Z_{21}$  for the network given in Fig.11. (8)
  - Find the short circuit admittance functions  $y_{11}$  and  $y_{21}$  for the network in Fig.12. (8)

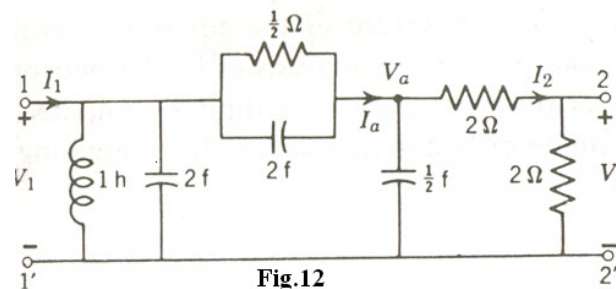


Fig.12

- Q.8**
- Synthesise the Cauer-I form of given admittance function
 
$$z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$
  - Check whether the polynomial  $s^5 + 2s^3 + 4s$  is Hurwitz or not.
- Q.9**
- Design constant  $k$  of low pass filter having cut off frequency = 3000Hz and nominal characteristic impedance  $R_0 = 600\Omega$ .
  - Design and derive T and  $\pi$ -sections low pass filter for nominal characteristic impedance  $R_0 = 600\Omega$ , cut off frequency = 1800Hz and infinite attenuation frequency  $f_\infty = 2\text{KHz}$ .