

**JUNE 2011****NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. The minimum gain required for an op amp so that the error in the gain from the ideal is less than 0.1% when the op amp is used as a voltage follower is \_\_\_\_\_

(A) 999 (B) 1000  
(C) 1001 (D) 10000

- b. An op amp has a common mode gain of 5, and CMRR of 94dB. If its differential input is  $2\mu\text{V}$  and the common mode input of 1mV, the output in mV is equal to\_\_\_\_\_.


(A) 495 (B) 500  
(C) 505 (D) 510

- c. The slew rate of an op amp is  $3.14 \text{ V}/\mu\text{sec}$ . If the frequency of the sinusoidal input to the voltage follower using this op amp is 5 kHz, the maximum amplitude of the input that could be applied so that the output is not distorted is equal to\_\_\_\_\_.

(A) 31.4 V (B) 50 V  
(C) 62.8 V (D) 100 V


- d. The output voltage in the circuit of Fig.1 is equal to\_\_\_\_\_.

(A) 0 V  
(B) -1 V  
(C) +1 V  
(D) -4 V

 **Fig. 1**

- e. In the Schmitt trigger circuit of Fig.2, the UTP (Upper Trigger Point) is equal to \_\_\_\_\_.

 (A) -6 V  
(B) -4 V  
(C) +4 V  
(D) +6 V



- f. The hexadecimal equivalent of the decimal number 4444 is equal to \_\_\_\_\_.

(A) 115C  
(B) 114D  
(C) C511  
(D) D411

- g. The 2-input EXCLUSIVE-OR gate gives HIGH output when both the inputs are \_\_\_\_\_.

(A) LOW  
(B) HIGH  
(C) Equal  
(D) Different

- h. The minimum number of NOR gates required to realize an EXCLUSIVE-OR function (using only NOR gates) is \_\_\_\_\_.

(A) 3  
(B) 4  
(C) 5  
(D) 6

- i. If the input frequency to a ripple counter using 5 flip flops is 1 MHz, the output frequency is equal to \_\_\_\_\_.

(A) 100 kHz  
(B) 20 kHz  
(C) 3.5 kHz  
(D) 31.25 kHz


- j. The main advantage of parallel comparator A/D converter is

(A) Accuracy  
(B) Low noise  
(C) Low cost  
(D) Low conversion time


### PART (A)

Answer At least TWO questions. Each question carries 16 marks.

 
- Q.2** a. In the circuit of Fig.3, determine the voltage gain  $v_o/v_i$  and the input impedance of the non-inverting amplifier. The op amp has an input impedance of 500 K $\Omega$ , output impedance of 500 $\Omega$  and an open loop gain of  $10^4$ . (8)



 - b. In the circuit of Fig.4, determine the output voltage if the input voltage is 10mV. Assume that the op-amp is ideal. (8)



 - Q.3** a. Design a circuit using two ideal op amps to obtain an output  $V_0 = V_1 - 2V_2 + 3V_3 - 4V_4$ . Inputs available are only  $+V_1, +V_2, +V_3$  and  $+V_4$ . (8)
- b. In the circuit of Fig.5, obtain the expression for  $I_L$ . (8)



- Q.4** a. Draw the circuit of a integrator using an ideal op amp, and prove that it works as an integrator. (5)
- b. What modifications are required to make the circuit in Q.4 (a) a practical integrator circuit. (3)

- c. Design a Schmitt trigger circuit using an ideal op amp operating with  $+15V$  and  $-15V$ , to have the upper and lower trigger points as  $+8V$  and  $-6V$  respectively. Also draw the output waveform if the input is a  $10V$  peak sinusoidal signal. (8)


- Q.5** a. With a neat diagram explain the working of an R-2R ladder type D/A converter. What are its main advantages with respect to a weighted resistor D/A converter? (8)
- b. Draw the circuit of a monostable multivibrator using 555 timer IC, and design the values for the different components in the circuit so that the output pulse width is  $0.2$  msec. (8)

### PART (B)

Answer At least TWO questions. Each question carries 16 marks.

- Q.6** Perform the following conversions: (2×8)
- (i)  $(756.75)_{10} = ( )_2$  (ii)  $(101111.101)_2 = ( )_{10}$  (iii)  $(463.25)_{10} = ( )_8$
- (iv)  $(672.46)_8 = ( )_{10}$  (v)  $(4680.125)_{10} = ( )_{16}$  (vi)  $(9A8E.D)_{16} = ( )_{10}$
- (vii)  $(76EF.AB)_{16} = ( )_8$  (viii)  $(125.75)_8 = ( )_{16}$

 - Q.7** a. Implement the given function  $f(A, B, C) = A + BC$  by using (5)
- (i) NAND gate (ii) NOR gate
- b. Draw the logic circuit to implement the OR function using only NAND gates. (5)
- c. Obtain the logic expression for the output X of the circuit in Fig.6, and simplify it using De Morgan's theorems. (6)



- Q.8** a. Show how a 16 input multiplexer is used to generate the function (6)
- $$f(A, B, C, D) = \overline{A} \overline{B} \overline{C} D + BCD + A \overline{B} \overline{D} + ABCD$$
- b. Draw the truth table for 'DIFFERENCE' and 'BORROW' of a FULL SUBTRACTOR. From the truth table, obtain logic expressions for them. From these expressions realize the FULL SUBTRACTOR using logic gates. (10)
- Q.9** a. Draw the circuit of a latch using two NOR gates and explain its operation. (4)
- b. Draw the internal circuit of an edge triggered D flip-flop and explain its functioning using necessary waveforms. (6)
- c. Draw the circuit of a MOD-60 ripple counter to reduce  $60Hz$  to  $1Hz$ , using JK flip-flops and explain its operation with its state transition diagram. (6)