

DipIETE – ET (OLD SCHEME)

Code: DE08
Time: 3 Hours

JUNE 2011

Subject: ANALOG ELECTRONICS
Max. Marks: 100

NOTE: There are 9 Questions in all.


- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- A transistor is said to be in quiescent stage when
 - emitter junction bias is just equal to collector junction bias.
 - no currents are flowing.
 - no signal is applied to the input.
 - it is unbiased.
- The main component responsible for lowering of gain in an R-C coupled amplifier in low frequency range is
 - Biasing system.
 - resistor R_E .
 - Coupling capacitor C_C
 - transistor itself.
- Which of the following classes of amplifiers has maximum distortion?
 - Class A
 - Class B
 - Class AB
 - Class C
- Feedback in amplifier always helps in
 - controlling its output.
 - increasing its gain.
 - reducing its input impedance.
 - stabilizes its gain.
- A crystal oscillator provides very stable frequency because of
 - high stability of the crystal
 - the rigid crystal structure
 - low $\frac{X_L}{R}$ ratio of the crystal
 - high Q of the crystal
- Stagger tuning is achieved by
 - double tuned circuit.
 - tuned circuits which are tuned to same frequency.
 - tuned circuits which are tuned to slightly different frequencies.
 - circuits tuned at harmonic frequencies.

- g. In a JFET, increase in applied external bias to the gate causes
- (A) decrease in size of depletion regions.
 - (B) increase in drain current.
 - (C) decrease in channel resistance.
 - (D) decrease in drain current to achieve pinch-off voltage.
- h. Schmitt trigger is basically
- (A) an astable multivibrator
 - (B) a monostable multivibrator
 - (C) a bistable multivibrator
 - (D) an oscillator
- i. For faster switching action of a transistor
- (A) a capacitor may be connected across the base resistance.
 - (B) a capacitor may be connected in series with the base resistance.
 - (C) a capacitor may be connected across R_E .
 - (D) the value of the coupling capacitor may be increased


j. The circuit shown in Fig.1 is

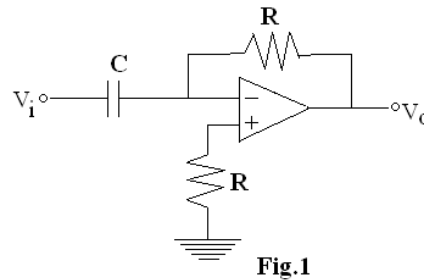


- (A) an adder
- (B) a differentiator.
- (C) an integrator
- (D) comparator

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

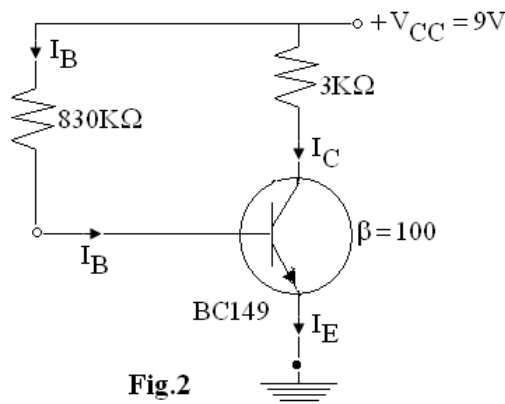- Q.2** a. Draw the circuit diagram of self Biasing and explain how does this circuit provides bias stabilization automatically. (10)
- b. Calculate the operating point for the Fixed Biasing transistor circuit shown in Fig.2 and draw its dc load line. (6)



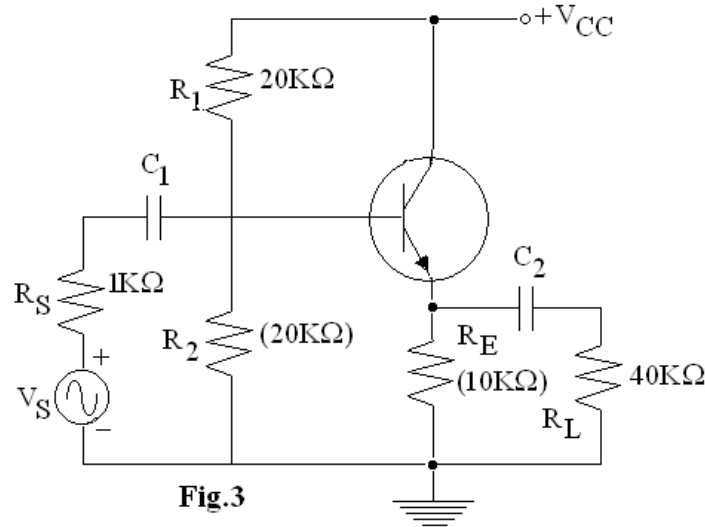
- Q.3** a. Draw the hybrid Pi model for transistor in CE configuration at lower frequency and briefly explain the components of the model. (9)
- b. Calculate the current gain (A_I), voltage gain (A_V) and power gain (A_P) for the common collector amplifier shown in Fig.3. The given transistor h-parameters are $h_{ic} = 1.4K\Omega$, $h_{fc} = 100$ and $h_{rc} = 20\mu A/V$. (7)



- Q.4** a. Compare the characteristic performances of CE, CB, CC configurations with their applications. (7)
- b. Draw the circuit diagram of single tuned voltage amplifier and explain its working. What are its limitations? (9)
- Q.5** a. Draw the circuit of class-B Push-Pull amplifier and explain its operation with neat waveforms. (10)
- b. A transformer-coupled class-A Power amplifier draws a current of 200 mA from a collector supply of 10V, when no signal is applied to it. Determine
- Maximum output power, P_{out}
 - DC power input, P_{in}
 - Maximum collector efficiency, η_{max}
- (6)
- Q.6** a. What is an oscillator? Draw the circuit diagram of RC-phase shift oscillator using BJT and explain its operation. Mention its applications. (10)
- b. The R-C circuit of a Wein-bridge oscillator consists of $R_1 = R_2 = 220K\Omega$ and $C_1 = C_2 = 250PF$. Determine the frequency of oscillation. (6)
- Q.7** a. Draw the circuit of zero-crossing detector using Op-Amp and explain its operation with the help of input and output waveforms. (8)

- b. An Op-Amp inverting amplifier has $R_f = 500K\Omega$ and $R_1 = 5K\Omega$. Determine its
- Voltage gain (A_v)
 - Input resistance (R_{in})
 - Output resistance (R_o)
 - Output voltage (V_{out})
- (8)

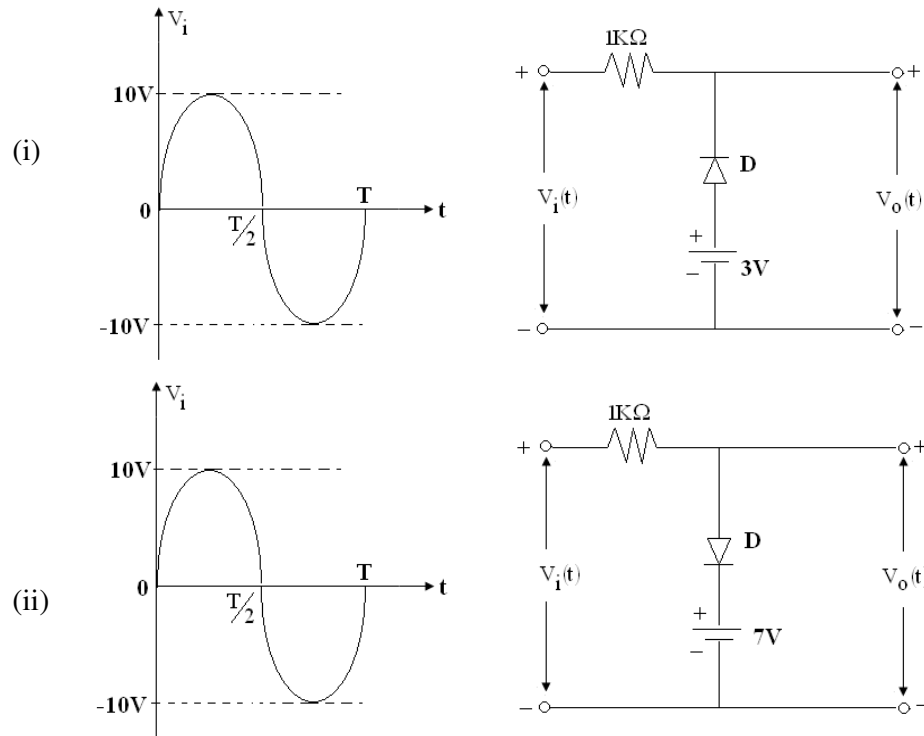- Q.8** a. Determine the output voltages for the following biased clipping circuits. Assume ideal diodes. (6)



- b. Draw the circuit of monostable multivibrator using Bipolar Junction Transistors and explain its working. What are its applications? (10)

- Q.9** a. What is Thermal Run-away in Transistors? How to avoid it? (4)

- b. Why harmonic distortion is prominent in Power amplifiers? Support your answer with mathematical expressions. (6)

- c. What is Input offset voltage and explain its significance in Op-Amp? (6)