

DipIETE – ET (OLD SCHEME)

Code: DE11
Time: 3 Hours

Subject: ELECTRONIC INSTRUMENTATION & MEASUREMENT
Max. Marks: 100

JUNE 2011

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Systematic errors are

- | | |
|--------------------------|---------------------------|
| (A) Instrumental errors. | (B) Environmental errors. |
| (C) Random errors | (D) Both (A) & (B) |

b. The wheat stone bridge method of resistance measurement is ideally suitable for the measurement of resistance values in the range of

- | | |
|-----------------------------------|-------------------------------------|
| (A) 0.001 Ω to 1 Ω | (B) 0.1 Ω to 100 Ω |
| (C) 100 Ω to 10 k Ω | (D) 100 k Ω to 10 M Ω |

c. In a CRO the quantity to be measured is applied across

- | | |
|--------------------------|--------------|
| (A) Focussing electrodes | (B) Cathode |
| (C) Y –plates | (D) X-plates |

d. The Lissajous pattern with equal voltages of equal frequency and phase shift by 90° is

- | | |
|-------------------|------------|
| (A) Straight line | (B) Circle |
| (C) Ellipse. | (D) Dot |

e. DAC

- (A) Stands for digital to analog converter.
- (B) Referred to an encoding device
- (C) Is considered as a decoding device
- (D) Both (A) & (C)

f. The bridges suitable for the measurement of an unknown inductance in terms of a capacitance would include

- | | |
|----------------------|--------------------------------|
| (A) Maxwell and Hay | (B) Maxwell and Schering |
| (C) Hay and Schering | (D) Maxwell, Hay and Schering. |

- g. Hysteresis in an measuring instrument means
- (A) The change in the same reading when input is first increased and then reduced.
 - (B) The reliability of the instrument.
 - (C) The repeatability of the instrument.
 - (D) The inaccuracy due to change in temperature.
- h. The frequency meter that can be used for measurement of radio frequency is
- (A) Weston.
 - (B) Electrical resonance
 - (C) Heterodyne
 - (D) Vibrating reed.
- i. Which of the following can be measured with the help of piezoelectric crystal?
- (A) Force
 - (B) Temperature
 - (C) Acceleration
 - (D) All the these
- j. The strain gauge factor G is given by
- (A) $G = \frac{\Delta R / R}{\Delta l / l}$
 - (B) $G = \frac{\Delta l / l}{\Delta R / R}$
 - (C) $G = \frac{\Delta R / R}{\Delta D / D}$
 - (D) None of the above

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Explain Gross Errors and Systematic Errors. (8)
- b. Distinguish between Primary sensors and transducers. (8)
- Q.3** a. Explain the basic block diagram of a microprocessor based ramp type digital voltmeter. (8)
- b. How does Hay's bridge differ from Maxwell Bridge? Also derive the condition for calculating the unknown resistance and inductance. (8)
- Q.4** a. Explain the function of delay line used in a CRO. (8)
- b. Distinguish between passive and active probes of CRO. (8)
- Q.5** a. Explain the working of a sweep generator with a suitable block diagram. (8)
- b. Draw the block diagram of a signal generator and explain its working. (8)

- Q.6** a. Explain any one method for the measurement of sensitivity and selectivity of a receiver.
- b. Explain working of Harmonic Distortion Analyser using bridged T- network. (8)
- Q.7** a. Draw the circuit of an R-2R type of D/A converter and explain its operation. (8)
- b. For a 5 bit resistive divider, determine the following:
- (i) The weights assigned to the LSB
 - (ii) The weights assigned to the 2nd and 3rd LSB.
 - (iii) The change in output voltage due to change in the LSB, 2nd LSB and 3rd LSB.
 - (iv) The output voltage for a digital input of 11011 and 10110. (Assuming 0=0V and 1 =+10V) (8)
- Q.8** a. Describe the working of Hall effect displacement transducers. (8)
- b. Explain working principle of Piezoelectric transducers and photoelectric transducer (8)
- Q.9** Write short notes on any **TWO** of the following:
- (i) Measurement of flux by induced emf method.
 - (ii) Bolometer method of power measurement.
 - (iii) Digital frequency counter. (2×8)