

## DipIETE – ET (OLD SCHEME)

Code: DE22  
Time: 3 Hours

Subject: INDUSTRIAL ELECTRONICS  
Max. Marks: 100

**JUNE 2011**

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. An SCR can be operated
- (A) Only under reverse biased condition  
(B) Only under forward biased condition  
(C) Both forward & reverse bias conditions  
(D) Without biasing
- b. A 3-phase full wave fully controlled bridge rectifier uses
- (A) 4 SCR's (B) 6 SCR's  
(C) 8 SCR's (D) 3 SCR's
- c. According to their connections inverters are classified as
- (A) Series inverters (B) Parallel inverters  
(C) Bridge inverters (D) All of the above
- d. Average output of a dc chopper is given by
- (A)  $V_O = V_{dc} / \text{duty cycle}$  (B)  $V_O = V_{dc} \times \text{duty cycle}$   
(C)  $V_O = \text{duty cycle} / V_{dc}$  (D) none of these
- e. A cycloconverter is a device which
- (A) Measures frequency of A.C. mains.  
(B) Converts A.C. of one frequency to A.C. of other frequency.  
(C) Converts A.C. into D.C.  
(D) Converts D.C. into A.C.
- f. UJT is used for
- (A) Controlling the power. (B) Triggering a triac.  
(C) Triggering an SCR. (D) Triggering a Diac.

- g. In dielectric heating process the supply requires
- (A) Low frequency. (B) Very low frequency.  
(C) High frequency. (D) Very high frequency.
- h. ON and OFF frequency of a chopper depends on
- (A) Applied voltage. (B) The load current.  
(C) Type of the chopper. (D) Output voltage.
- i. Induction heating is used for
- (A) Melting (B) Annealing  
(C) Forging (D) All the above.
- j. Induction heating requires
- (A) A.C. input. (B) High frequency A.C. input  
(C) D.C. input. (D) Both A.C. and D.C. input

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

- Q.2** a. Explain the Principle of operation & V-I Characteristics of an SCR. (8)
- b. Explain light triggering and dv/dt triggering circuit of an SCR. (4+4)
- Q.3** a. Explain the circuit of a three - phase bridge inverter for  $180^\circ$  conduction. Also draw the waveforms. (8)
- b. A three - phase bridge inverter is fed by a 400 volts battery. The load is star connected and has a resistance of 10 ohms per phase. Find rms load current, power output, and average and rms thyristor current. Assume  $120^\circ$  mode of operation. (8)
- Q.4** a. Explain the circuit of a single-phase fully controlled bridge rectifier with resistive R- load. Also draw the waveforms. (8)
- b. Explain the principle of operation and application of a single-phase cyclo - converter. (8)
- Q.5** a. Explain the different commutation methods for choppers. (8)
- b. A dc chopper has an input voltage of 230 V and an output voltage of 150 V. It is operating at a frequency of 1 kHz. Find the periods of conduction and blocking in each cycle. (8)

- Q. 6** a. In a dielectric heating process a voltage of 230 V is applied at 30kHz .if the electrodes used have area of  $4 \text{ cm}^2$  separated by 8 cm what is the dielectric loss filled between the electrodes? Assume phase angle of dielectric =  $30^\circ$  and dielectric constant is 10. (8)
- b. Explain the process of resistance welding with a suitable diagram. Also give the applications of resistance welding. (8)
- Q. 7** a. What is meant by thermal loss in dielectric heating? Explain the process of dielectric heating. (8)
- b. Give the classification of inverters and applications of series and parallel inverters. (4+4)
- Q. 8** a. Explain the circuit of the single-phase fully controlled rectifier with RL load and with freewheeling diode. Discuss the function of the diode? Also draw the waveforms. (8)
- b. Why induction heating is preferred over other types of heating? Where all is it used? (8)
- Q.9** Write notes on: -
- (i) D.C. motor speed control. (5)
- (ii) Application of choppers. (5)
- (iii) SCR rating. (6)