

Subject: POWER ELECTRONICS**Time: 3 Hours****JUNE 2011****Max. Marks: 100****NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The _____ is a commonly used device in power electronics.

- (A) PIN Diode (B) UJT
(C) PV Cell (D) SCR.

b. A power MOSFET is a _____ controlled device.

- (A) Current (B) Frequency
(C) Power factor (D) Voltage.

c. An inverter is:

- (A) AC to DC converter (B) AC to AC converter
(C) DC to DC converter (D) DC to AC converter.

d. The DIAC is primarily used as:

- (A) Power thyristor (B) Triggering device
(C) Pulse generator (D) Surge protector

e. The static switches are of the following types:

- (A) Only the AC switches
(B) Only the DC switches
(C) The electro-mechanical AC and DC switches
(D) AC and DC switches for low and high power applications.

f. The gating signals for thyristors of AC-DC converters requires:

- (A) Pulse shaping to generate short duration pulses
(B) Detecting zero crossing of the input voltage.
(C) Phase shifting of signals
(D) All of the above.

g. Optocouplers are:

- (A) Pulse transformers (B) AC voltage converters
(C) Fast switching thyristors (D) Commutation capacitors.

- h. The choppers are commonly used as:
- (A) DC transformers (B) Voltage regulators
(C) Harmonics generators (D) Frequency controllers.
- i. The commonly used device for protection against transient over voltages is:
- (A) Schottky diode (B) Selenium diode
(C) Bipolar junction transistor (D) Heat sink.
- j. For series and parallel operation of thyristors, the preferred approach is to:
- (A) Use a common heat sink
(B) Connect a small resistance in series with each thyristor
(C) Use magnetically coupled inductors
(D) Provide voltage and current sharing networks to protect them under steady-state and transient conditions.

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. With the help of circuit diagrams explain gate turn-off and gate turn-on of a thyristor. (4+4)
- b. Discuss the methods of thyristor protection. (8)
- Q.3** a. What is the role of UJT and MOSFETs in triggering mechanism of power controlled circuits? (8)
- b. Explain the commonly used cooling arrangements for high power devices. What are the merits and demerits of water and air cooled systems? (8)
- Q.4** Write notes on the following:
- (i) Light Activated SCR,
(ii) Thyristor Commutation.
- Give diagrams, schematics and operational characteristics. (8+8)
- Q.5** a. Compare the working of full wave controlled centre tap rectifier with full wave controlled bridge rectifier with the help of circuit explanation. (8)
- b. Why is the power factor of semi-converters better than that of full-converters? (8)
- Q.6** a. With the help of diagram, explain the working principle of Full-wave Half controlled Bridge Rectifiers with FWD. (8)
- b. Using block/schematic diagram explain working of a half-wave three pulse controlled rectifier. (8)

- Q.7** With the help of diagram / circuit explain the working of following:-
- (i) Buck-Boost chopper.
 - (ii) Step down chopper. (8+8)
- Q.8** a. What is the principle of operation of an inverter? Give its performance parameters? (6+4)
- b. What are the advantages and disadvantages of current-source inverters? (6)
- Q.9** 'Static and mechanical switches, Cycloconverters and Controlled rectifiers are used in Power Electronics' --- justify this statement by giving examples, their operating characteristics and their typical utility in industrial applications. (6+10)