

Time: 3 Hours

DECEMBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions, answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Three resistors of value $1K\Omega$, $2K\Omega$ and $4K\Omega$ are connected in parallel. If supply voltage is 2V, the total current in the circuit is _____.

- (A) 3 mA (B) 3.25 mA
(C) 3.5 mA (D) 4 mA

b. The value of voltage equivalent of temperature at room temperature (27°K) is

- (A) 26 mV (B) 37 mV
(C) 100 mV (D) 200 mV

c. Ripple factor for Full wave Rectifier without filter is _____

- (A) 0.462 (B) 0.432
(C) 0.492 (D) 0.482

d. DC current of full wave rectifier is _____

- (A) $\frac{I_m}{\pi}$ (B) $\frac{I_m}{\sqrt{2}}$
(C) $\frac{2I_m}{\pi}$ (D) $\frac{2I_m}{\sqrt{2}}$

e. Current gain β in terms of α is expressed as

- (A) $\frac{\alpha}{1+\alpha}$ (B) $\frac{1+\alpha}{\alpha}$
(C) $\frac{\alpha}{1-\alpha}$ (D) $\frac{1-\alpha}{\alpha}$

f. A Four layer electronic device is _____

- (A) BJT (B) SCR
(C) UJT (D) FET

g. nMOS transistor with potential divider as biasing circuit having $R_1 = R_2 = 100\text{K}\Omega$ will have gate potential for $V_{DD} = 12\text{V}$ as _____

- (A) 8V (B) 6V
(C) 10V (D) 12V

h. The elementary JFET amplifier has $g_m = 1600\mu\text{sec}$, $r_d = 50\text{K}\Omega$, $R_L = 5\text{K}\Omega$. The value of small signal voltage gain is _____

- (A) 8 (B) 0.8
(C) -8 (D) -0.8

i. For class-B amplifier operation, the operating point Q is at _____ of the load line.

- (A) center (B) cut off end
(C) beginning (D) None

j. The length required to fabricate $20\text{K}\Omega$ resistor whose width is $25\mu\text{m}$ and $R_s = 200\Omega/\text{square}$ is

- (A) $250\mu\text{m}$ (B) $1000\mu\text{m}$
(C) $25000\mu\text{m}$ (D) $2500\mu\text{m}$

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

Q.2 a. State superposition and Thevinin's theorem. Give an example for each. (8)

b. Find the value of R in Fig.1 such that the power supplied by 100V source to the network is same as the power supplied by 5A source. (6)

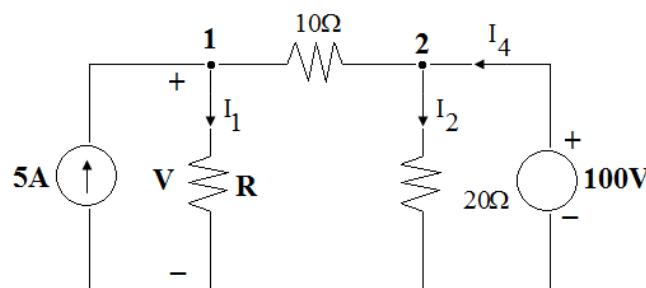


Fig.1

c. Plot Z vs ω response of RLC parallel circuit indicating resonant frequency and half power points. (2)

Q.3 a. With neat diagram explain Zener diode I-V characteristics and how it works as a voltage regulator. (10)

b. For the circuit shown in Fig.2, determine the current I_1 and I_2 for supply voltage $V_s < 0.7V$ and $V_s > 0.7V$. Assume $V_T = 0.7$ for all diodes. (6)

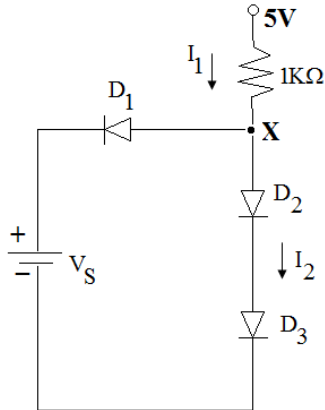


Fig.2

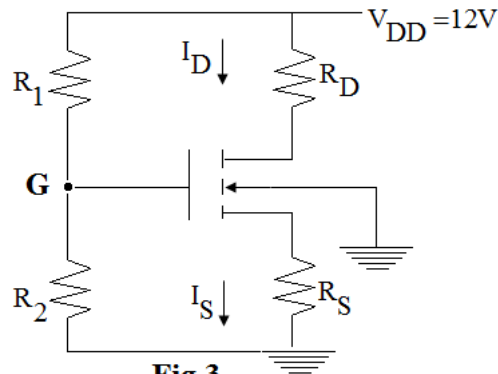


Fig.3

Q.4 a. Explain how MOSFET is different from JFET. (8)

b. An nMOS transistor is used in the circuit of Fig.3. MOSFET has device parameter of $K = 2$. The circuit has $R_D = R_S = 2.5K\Omega$, $R_1 = 100K\Omega$, $R_2 = 200K\Omega$. Determine I_D and V_{DS} . (8)

Q.5 a. Write circuit and small signal model of BJT amplifier (CE configuration). Derive an expression for i_c . (8)

b. The emitter follower circuit of Fig.4 has $\beta = 98$, $r_\pi = 1.275K\Omega$, $R_B = 220K\Omega$, $R_E = 3.3K\Omega$, $V_{CC} = +12V$. Calculate:
(i) voltage gain
(ii) input and output impedances. (8)


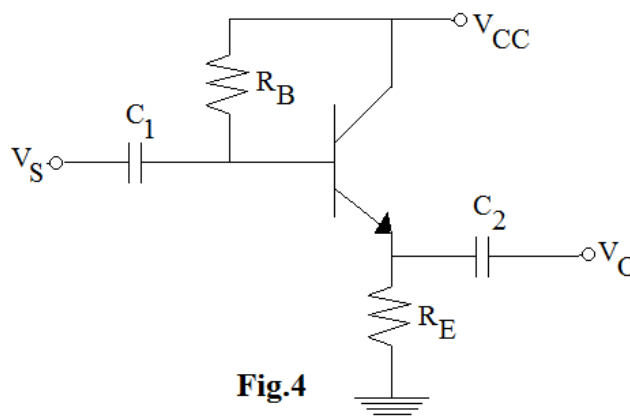


Fig.4

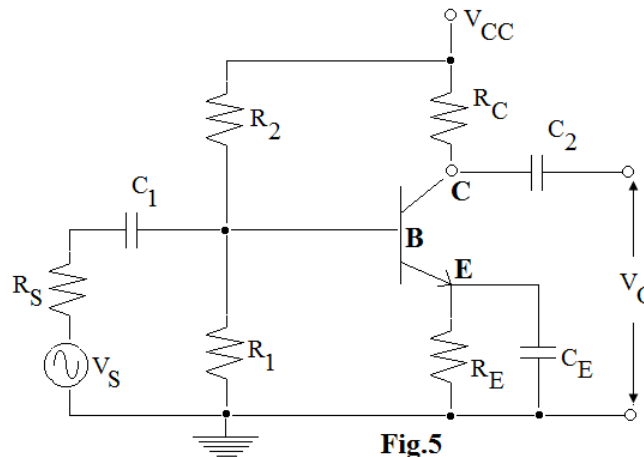- Q.6** a. Briefly explain the importance of the terms 'Quality factor' in Tuned Amplifier. (8)
- b. The amplifier circuit of Fig.5 uses silicon BJT with $\beta = 100$. The values of other circuit elements are $R_1 = 60\text{K}\Omega$, $R_2 = 140\text{K}\Omega$, $R_S = 4\text{K}\Omega$, $R_E = 3\text{K}\Omega$, $R_C = 4\text{K}\Omega$. Capacitances are assumed to be large and $V_{CC} = 10\text{V}$. Find DC bias current I_C and V_{CE} . (8)



- Q.7** a. Explain briefly functioning of series fed class-A large signal amplifier. (8)
- b. With neat sketch explain the working of class-B push-pull amplifier. (8)
- Q.8** a. Explain various types of feedback connections. (8)
- b. A voltage series feedback amplifier has the following data. $A = -500$, $R_I = 1.5\text{K}\Omega$, $R_O = 50\text{K}\Omega$, $\beta = \frac{1}{20}$. Calculate amplifier gain, input and output resistances. (8)
- Q.9** a. Explain briefly oxidation and photolithography process of IC Fabrication technique. (6)
- b. What is the length required to fabricate $20\text{K}\Omega$ resistor whose width is $25\mu\text{m}$, given $R_s = 200\Omega/\text{Square}$? (4)
- c. Write cross-sectional view of CMOS fabrication and explain briefly. (6)