

Time: 3 Hours

**DECEMBER 2012**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Which of them is a non linear device?

- (A) Capacitor (B) Inductor  
(C) Transistor (D) All of these

b. At time  $t=0$ , if the switching of source is done, then an initially relaxed capacitor behaves as a

- (A) Short circuit (B) Open circuit  
(C) Voltage source (D) Current source

c. If a function  $f(t)$  is shifted by 'T', then is correctly represented as

- (A)  $f(t-T)U(t)$  (B)  $f(t)U(t-T)$   
(C)  $f(t-T)U(t-T)$  (D)  $f(t-T)(t-T)$

d. Laplace transform of function  $e^{-2t} \sin 2t$  is

- (A)  $2/(s^2+2s+8)$  (B)  $4/(s^2+2s+8)$   
(C)  $2/(s^2+4)$  (D)  $4/(s^2+4)$

e. Nortons theorem is valid for

- (A) Linear loads only (B) bilateral loads only  
(C) Nonlinear loads only (D) all types of load

f. A lattice with  $Z_a=2s$  and  $Z_b=2/s$  is terminated in a load  $R_L=2$ . Then input impedance is

- (A) An inductor of value 2 H (B) A capacitor of value  $\frac{1}{2}$  F  
(C) A resistor of value 2 ohms (D) A resistor of value  $\frac{1}{2}$  ohms

- g. Use CG:GC transformation to obtain the element values of an LP filter given the values for the HP filter as  $C=2F$  and  $R=2.5\Omega$ .  $R'$  and  $C'$  in LP filter have respectively values

- (A)  $\frac{1}{2.5}\Omega, 1/2 F$  (B)  $2\Omega, \frac{1}{2.5}F$   
 (C)  $2\Omega, 2.5F$  (D)  $\frac{1}{2}\Omega, \frac{1}{2.5}F$

- h. Given  $Z(s)=(s+2)/(s+1)(s+3)$ . The number of elements in a canonical realization is

- (A) 2 (B) 3  
 (C) 4 (D) 5

- i. In a series RLC circuit, the maximum voltage across the capacitor occurs at a frequency

- (A) Equal to resonant frequency (B) Greater than resonant frequency  
 (C) Smaller than resonant frequency (D) Both (A) and (B)

- j. The h parameter of two port network can be obtained by setting

- (A)  $I_1 = 0$  or  $V_2 = 0$  (B)  $I_1 = 1A$  or  $V_2 = 0$   
 (C)  $I_1 = 0$  or  $V_2 = 1V$  (D) All of these

**Answer any FIVE Questions out of EIGHT Questions.**

**Each question carries 16 marks.**

- Q.2** a. For the circuit shown in Fig.1, determine the equivalent voltage source and equivalent current source across the terminal 'a' and 'b' (8)

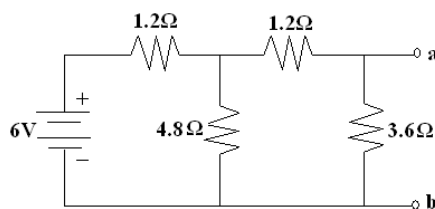


Fig. 1

- b. Express the node voltage  $V$  in Fig. 2 as a function of time if  $R=\frac{1}{2}\Omega$ . Given that the initial voltage across the capacitor ( $C$ ) is  $+10V$  and there is no initial current through the inductor ( $L$ ). (8)

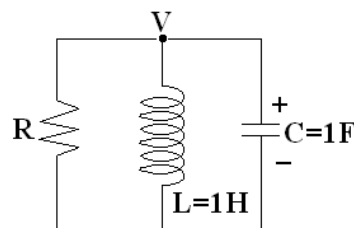


Fig. 2

- Q.3** a. Fig.3 shows a two loop network. Assuming that prior to closing of switch K ( $t=0$ ) there was no voltage across the capacitor nor any current through the inductor. Find  $\frac{di_1}{dt}(t=0^+)$ ,  $\frac{di_2}{dt}(t=0^+)$ ,  $\frac{d^2i_1}{dt^2}(t=0^+)$  and  $\frac{d^2i_2}{dt^2}(t=0^+)$  (8)

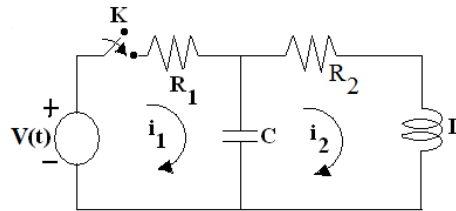


Fig. 3

- b. In the given network, the switch K is opened at  $t=0$ . At  $t=0^+$ , solve the values of  $V$ ,  $\frac{dV}{dt}$  and  $\frac{d^2V}{dt^2}$ , if  $I=10A$ ,  $R=1000\Omega$  and  $C=1\mu F$  (Fig. 4) (8)

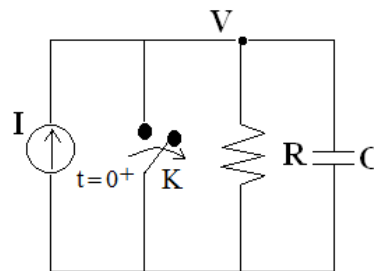


Fig. 4

- Q.4** a. At  $t=0$ , a switch is closed, connecting a voltage source  $V=V_m \sin \omega t$  to a series RL circuit. Find the expression for current by using method of Laplace transform. (8)
- b. For the circuit as shown in Fig. 5 obtain the value of transfer function  $H(s)$  and impulse response  $h(t)$  if the output is taken as voltage across the capacitor. (8)

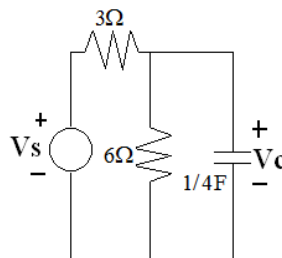


Fig. 5

- Q.5** a. State and explain Norton's theorem. Obtain the Thevenin's equivalent of circuit shown in Fig.6. (8)
- b. State and prove Superposition theorem. (8)

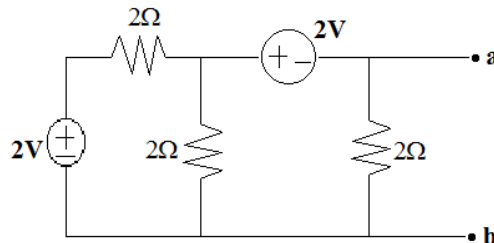


Fig.6

- Q.6**
- Define Y and h parameters of a two-port. Hence obtain the relations between them. (8)
  - For the circuit as shown in Fig.7, find the Z-parameters. (8)

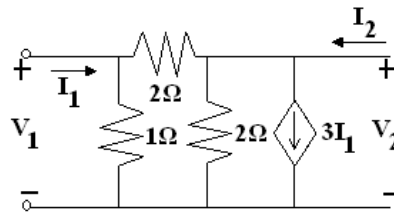


Fig.7

- Q.7**
- Write the properties of positive real functions. (8)
  - For the given polynomial  $P(S) = S^6 + 3S^5 + 4S^4 + 6S^3 + 13S^2 + 27S + 18$ , determine the number of zeros lying in the right half of S-plane, left half of S-plane and on the imaginary axis of S-plane. (8)

- Q.8**
- Given  $F(S) = \frac{6(S+2)(S+4)}{S(S+3)}$ , find the continued function expression and hence synthesise the network for the case when F(S) is an impedance Z(S). (8)

- Given  $\text{Real}[Z_d(j\omega)] = \frac{18\omega^2 + 48}{\omega^4 + 17\omega^2 + 16}$ . Obtain  $Z_d(S)$ . Show that  $Z_d(S)$  is RC impedance and realize it in Cauer form. (8)

- Q.9**
- Design a low pass T and  $\pi$  section filter having a design  $R_o = 600$  ohm and cut-off frequency = 2000 Hz. (8)

- Synthesize the function given below with a 1 ohm termination  

$$Z_{21}(s) = \frac{2}{s^3 + 3s^2 + 4s + 2}$$
(8)