

Code: AE08

Subject: CIRCUIT THEORY &amp; DESIGN

## AMIETE - ET (OLD SCHEME)

Time: 3 Hours

**OCTOBER 2012**

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Which of the following characteristic equation represents a non-linear resistance?

- (A)  $v+10 i=0$  (B)  $i+3v=10$   
 (C)  $v = i^2$  (D) All of these

b. If there are b branches and n nodes, the number of KCL equations required will be

- (A) b (B) n  
 (C) (n-1) (D) b-n+1

c. A 500 watt 220 V bulb is supplied with 110V. The power consumption by the bulb will be \_\_\_\_\_

- (A) 250 W (B) 125 W  
 (C) slightly more than 125 W (D) Slightly less than 125 W

d. The Thevenin's impedance between A and B in the circuit shown below in Fig.1 is

- (A)  $3.0\Omega$   
 (B)  $3.75\Omega$   
 (C)  $3.25\Omega$   
 (D)  $20\Omega$

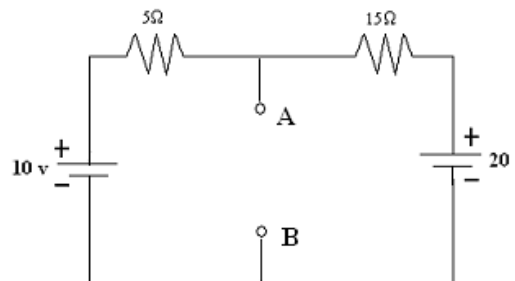


Fig.1

e. What is the efficiency of a network working under maximum power transfer condition?

- (A) 100% (B) 50%  
 (C) 0.0% (D) 70.7%

Code: AE08

Subject: CIRCUIT THEORY & DESIGN

- f. In an RLC series circuit, the impedance at resonance is  
 (A) minimum (B) maximum  
 (C) zero (D) infinity

- g. The open-circuit impedance parameter  $Z_{11}$  for the T-network shown below in Fig.2 is

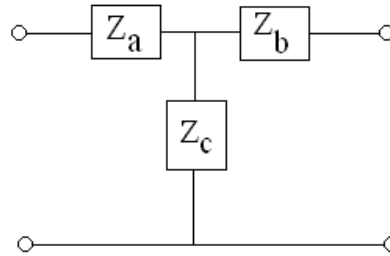


Fig.2

- (A)  $Z_a + Z_b$   
 (B)  $Z_a + Z_b + Z_c$   
 (C)  $Z_b + Z_c$   
 (D)  $Z_a + Z_c$

- h.  $F(S) = \frac{(S+1)(S+3)}{S(S+2)}$  represents an

- (A) R C impedance  
 (B) R C admittance  
 (C) R C impedance and an R L admittance  
 (D) R L admittance.

- i. The transfer function

$$T(S) = \frac{S^2}{S^2 + aS + b}$$

Belongs to an active

- (A) Low pass filter (B) High pass filter  
 (C) Band pass filter (D) Band-reject filter

- j. The coupling between two magnetically coupled coils is said to be ideal if the coefficient of coupling is

- (A) Zero (B) 0.5  
 (C) 1 (D) 2

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

- Q.2 a. Explain what do you understand by the duality in reference electrical networks. (8)

- b. Fig.3 shows a network containing one capacitor and several resistors. The capacitor is charged to voltage  $V_0$ . Find the expression for the current  $i_1(t)$  through the resistance  $R_1$ .

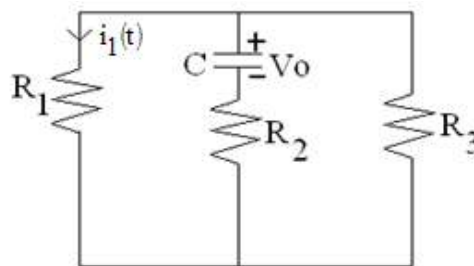


Fig.3

(8)

Code: AE08

Subject: CIRCUIT THEORY & DE

- Q.3**
- State the superposition theorem in reference to electrical network. Can the theorem be applied directly to calculate the power in an element of the network? Explain. (8)
  - In the network shown below in Fig.4 determine the value of impedance  $Z_L$  for maximum power and calculate the maximum power (8)

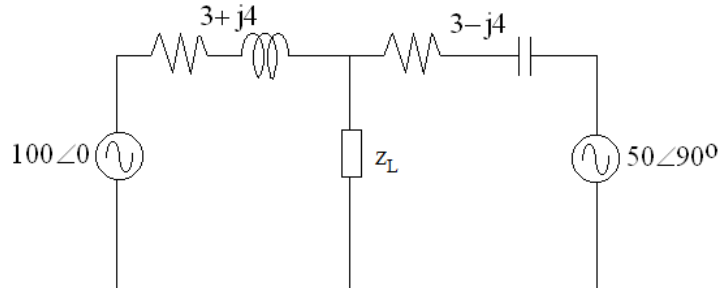


Fig.4

- Q.4**
- Show that the sum of energy stored by the inductor and the capacitor connected in series at resonance at any instant is constant and is given by  $LI^2$  (8)
  - For the circuit shown below in Fig.5 (8)  
 $Z_1 = (5 - j3)\Omega$ ,  $Z_2 = (4 + j2)\Omega$  and  $Z_3 = (2 + j3)\Omega$   
 Find:  
 (i) The input impedance  $Z_{in}$   
 (ii) The input current  $I$   
 (iii) The current through  $Z_2$   
 (iv) Is the series parallel circuits operating at its resonant frequency?

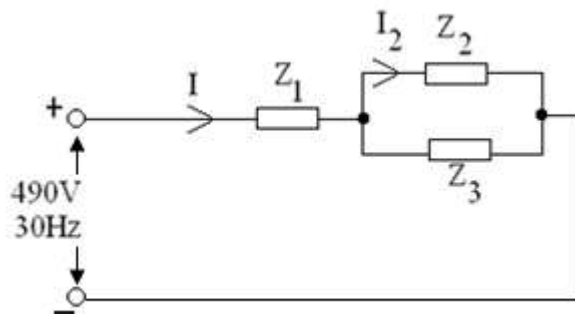


Fig.5

- Q.5**
- Define hybrid-parameters for a two- port network. (8)
  - Obtain Y-parameters of the circuit given below in Fig.6. Draw its equivalent model and find whether the network is reciprocal or symmetrical? (8)

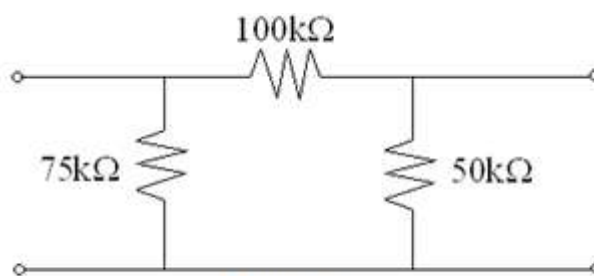


Fig.6

- Q.6** a. State the properties of 'POSITIVE REAL FUNCTIONS'.  
 b. Test whether the polynomial  $P(S) = S^5 + 3S^3 + S$  is Hurwitzian or not. (8)

- Q.7** a. Synthesize the function  $Z(S) = \frac{S(S^2 + 10)}{(S^2 + 4)(S^2 + 16)}$  using first Foster form of realization. (8)

- b. Synthesize the LC impedance function (8)


$$Z(S) = \frac{(S^2 + 1)(S^2 + 3)}{S(S^2 + 2)} \text{ in II Cauar Form}$$

- Q.8** a. List the various properties of transfer functions of electrical networks. (8)

- b. Determine the values of a, b and c for the given function  $|F(j\omega)|$  to be a maximally flat magnitude function. (8)

$$F(S) = \frac{S + a}{S^2 + bS + c}$$

- Q.9** a. An ideal voltage source in series with an impedance is shown in the following Fig.7. Obtain its equivalent current source across AB (4)

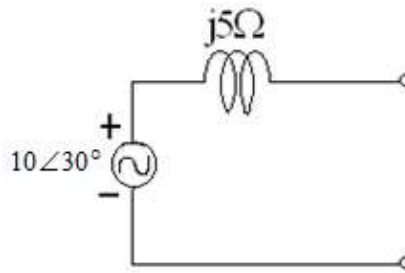

**Fig.7**

- b. Calculate the following for half wave alternating current (8)
- (i) Average value
  - (ii) RMS value
  - (iii) Form factor.
- c. Describe the sine function using two oppositely rotating phasors. (4)