

Time: 3 Hours

**DECEMBER 2013**

Max. Marks: 160

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Karnaugh Map uses \_\_\_\_\_

- (A) Binary Code (B) Grey Code  
(C) BDC Code (D) Both (A) and (B)

b. For impedance matching application, OP-AMP is used as a \_\_\_\_\_


- (A) Voltage Follower (B) Voltage Clamper  
(C) Voltage Clipper (D) Voltage Multiplier

c. An Integrated Circuit which consists of  $10^6 - 10^7$  transistors / chip is called as \_\_\_\_\_

- (A) Medium Scale Integration (B) Large Scale Integration  
(C) Very Large Scale Integration (D) Ultra Large Scale Integration

d. The output voltage ( $V_o$ ) for the OP-AMP circuit of Fig.1 is \_\_\_\_\_

- (A)  $V_o = V_3 - (V_1 + V_2)$   
(B)  $V_o = V_3 + (V_1 + V_2)$   
(C)  $V_o = -V_3 + (V_1 + V_2)$   
(D)  $V_o = -V_3 - (V_1 + V_2)$

 

**Fig. 1**

e. For which of the following flip-flops, the output is clearly defined for all the combinations of two inputs \_\_\_\_\_

- (A) D type flip-flop (B) R-S flip-flop  
(C) J-K flip-flop (D) None of these

f. For the circuit of Fig.2, the input resistance  $R_{id}$  will be \_\_\_\_\_

 


Fig.2

- (A)  $2R_1$  (B)  $2R_1 + R_2$   
(C)  $2(R_1 + R_2)$  (D) Infinity

g. The number of states in its counting sequence that a Ring Counter consisting of 'n' flip-flops is \_\_\_\_\_

- (A)  $+2^{n-1}$  (B)  $2^{n+1}$   
(C) n (D) n-1

h. A one-to-sixteen demultiplexer requires \_\_\_\_\_

- (A) 2 select input lines (B) 3 select input lines  
(C) 8 select input lines (D) 4 select input lines

i. The A/D converter which has maximum speed of conversion is \_\_\_\_\_

- (A) Successive-approximation A/D converter  
(B) Parallel-comparative A/D converter  
(C) Counter ramp A/D converter  
(D) Dual-slope A/D converter

j. Boolean Algebra states that the "OR ing of several variables results in the same regardless of the grouping of the variables" is called \_\_\_\_\_

- (A) Commutative Property (B) Associative Property  
(C) Distributive Property (D) All of these

### PART (A)

Answer At least TWO questions. Each question carries 16 marks.

- Q.2** a. Enlist the various advantages of IC over discrete component circuits. (4)
- b. Draw basic differential amplifier and discuss transfer characteristics of an ideal operational amplifier. (8)
- c. Design an amplifier with a gain of +5 using one OP-AMP (4)
- Q.3** a. State non-ideal DC characteristics of an op-amp. Explain any two of them in detail. (8)
- b. (i) Define Slew Rate of an op-amp  
(ii) What causes the Slew Rate  
(iii) How Slew Rate is measured  
(iv) Can IC 741C be used for high frequency application? (4×2)
- Q.4** a. Draw the characteristics of an ideal comparator and that of a commercially available comparator. Also list different types of comparators. (6)
- b. Explain the following in detail using OP-AMP, assuming 1-V peak to peak square wave as input signal for  
(i) Positive clipper (ii) Negative Clamper (2×4)
- c. State the applications of a precision diode. (2)
- Q.5** a. Describe the operation of an Astable multivibrator using 555 timer. (8)
- b. Calculate the values of LSB, MSB and full scale output for an 8-bit DAC for the 0 to 10V range. (6)
- c. What is a voltage regulator? State only name of the circuits that are used to make a regulated power supply. (2)

**PART (B)**

**Answer At least TWO questions. Each question carries 16 marks.**

- Q.6** a. Differentiate between positive logic and negative logic. (4)
- b. Perform the following conversions:  
(i)  $(110011011001)_2 = ( \quad )_{10}$  (ii)  $(268)_{10} = ( \quad )_{16}$   
(iii)  $(39.12)_{10} = ( \quad )_2$  (iv)  $(1054)_8 = ( \quad )_{10}$   
(v)  $(2040.125)_{10} = ( \quad )_{16}$  (vi)  $(1001101.1011)_2 = ( \quad )_8$  (6×2)
- Q.7** a. Why NAND and NOR gates are called universal gates? (6)
- b. Prove that the given identity  $Y = \overline{A + B}$  represents a NOR logic. (4)
- c. (i) Draw the logic circuit for the given identity  $Y = ABC + \overline{ABC} + B$   
(ii) Simplify the expression and draw a logic circuit for the same. (2×3)
- Q.8** a. What is Priority encoder? Draw & explain the truth table of decimal to BCD priority encoder. (8)

- b. Design a Full Adder Circuit consisting of three inputs A, B,  $C_{IN}$  and two outputs S,  $C_{OUT}$ . (8)

**Q.9**

- a. Write short notes on:-  
(i) NAND gate latch (ii) Clocked D FF (2×4)
- b. If data 1101 is fed into 4 bit Serial In / Serial Out Shift Register, show the status of register at various clock pulses. (6)
- c. State one advantage and one disadvantage of synchronous counter over asynchronous counter. (2)