

Q.2 a. Enlist the various advantages of IC over discrete component circuits.

Answer: 1.2 of Text Book I

b. Draw basic differential amplifier and discuss transfer characteristics of an ideal operational amplifier.

Answer: 2.4.1 & 2.4.2 of Text Book I

c. Design an amplifier with a gain of +5 using one OP-AMP

Answer: Page Number 49 of Text Book I

Q.3 a. State non-ideal DC characteristics of an op-amp. Explain any two of them in detail.

Answer: 3.2 of Text Book I

b. (i) Define Slew Rate of an op-amp

(ii) What causes the Slew Rate

(iii) How Slew Rate is measured

(iv) Can IC 741C be used for high frequency application?

Answer: 3.3.4 of Text Book I

Q.4 a. Draw the characteristics of an ideal comparator and that of a commercially available comparator. Also list different types of comparators.

Answer: Page Number 207 of Text Book

Q.5 a. Describe the operation of an Astable multivibrator using 555 timer.

Answer: 5.4 of Text Book I

b. Calculate the values of LSB, MSB and full scale output for an 8-bit DAC for the 0 to 10V range.

Answer:

(b) 8-bit DAC for 0 to 10. $(2 \times 3 = 6 \text{ M})$
 $\text{LSB} = \frac{1}{2} = 256$ For 10V range $\text{LSB} = \frac{10\text{V}}{256} = 39\text{mV}$
 $\text{MSB} = (\frac{1}{2}) \text{ Full Scale} = 5\text{V}.$
 $\text{Full Scale O/P} = (\text{Fullscale Voltage} - 1\text{LSB}) = 10\text{V} - 0.039\text{V}$

c. What is a voltage regulator? State only name of the circuits that are used to make a regulated power supply.

Answer:

Q:5 (c) A voltage regulator is an Electronic $(3/3)$ circuit that provides a stable dc voltage independent of the load current, temp. and ac line voltage variations. (2 M)
Four parts :- Reference voltage circuit, Error amplifier, series pass transistor, Feedback n/w.

- Q.6
- Differentiate between positive logic and negative logic.
 - Perform the following conversions:
 - $(110011011001)_2 = (\text{---})_{10}$
 - $(268)_{10} = (\text{---})_{16}$
 - $(39.12)_{10} = (\text{---})_2$
 - $(1054)_8 = (\text{---})_{10}$
 - $(2040.125)_{10} = (\text{---})_{16}$
 - $(1001101.1011)_2 = (\text{---})_8$

Answer:

Q:6 (a)

Positive logic		Negative logic
1) logic state 1 \equiv higher voltage level		Lower Voltage Level 2x2 = (4)
2) logic state 0 \equiv Lower voltage level		Higher voltage level.

(b) (i) $(110011011001)_2 = (\text{---})_{10}$ 6x2

$$\begin{array}{cccccccccccc}
 1 & 1 & 0 & 0 & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 1 \\
 / & / & / & / & / & / & / & / & / & / & / & / \\
 2048 & 1024 & 512 & 256 & 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1
 \end{array}
 = (3289)_{10}$$

(ii) $(268)_{10} = (\text{---})_{16}$

16	268
16	16
16	1
2	1

Reminder 12: C

0: 0
1: 1 ↑ 10C

$$(iii) (39.12)_{10} = (\text{---})_2$$

2	39	Remainder
2	19	1 (LSB)
2	9	1
2	4	0
2	2	0
	1	1

$$\begin{aligned} 0.12 \times 2 &= 0.24 & 0 \\ 0.24 \times 2 &= 0.48 & 0 \\ 0.48 \times 2 &= 0.96 & 0 \\ 0.96 \times 2 &= 1.92 & 1 \\ 0.92 \times 2 &= 1.84 & 1 \end{aligned}$$

$$(1001011.00011\dots)_2$$

$$(iv) (1054)_8 = (\text{---})_{10}$$

$$\begin{array}{cccc} 10 & 5 & 4 & \\ \hline 8^3 & 8^2 & 8^1 & 8^0 \end{array} = (556)_{10}$$

$$(v) (2040.125)_{10} = (7FB.2)_{16}$$

16	2040	Remainder
16	127	8
16	7	15 (F)
		7

$$.125 \times 16 = 2$$

$$(vi) (1001101.1011)_2 = (\text{---})_8$$

$$\begin{array}{cccccc} 001 & 001 & 101 & . & 101 & 100 \\ \downarrow & \downarrow & \downarrow & & \downarrow & \downarrow \\ 1 & 1 & 5 & & 5 & 4 \end{array} = (115.54)_8$$

Q.7 a. Why NAND and NOR gates are called universal gates?

Answer: 3.12 of Text Book II

b. Prove that the given identity $Y = \overline{A+B}$ represents a NOR logic.

c. (i) Draw the logic circuit for the given identity $Y = ABC + \overline{A}BC + B$

(ii) Simplify the expression and draw a logic circuit for the same.

Answer:

(b) $Y = \overline{A+B}$ - NOR Gate. or $\bar{Y} = A+B$

A	B	Y	\bar{Y}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0




(2x2 = 4m)



(c) $Y = ABC + \overline{A}BC + B$

(i) Logic circuit

(2m)

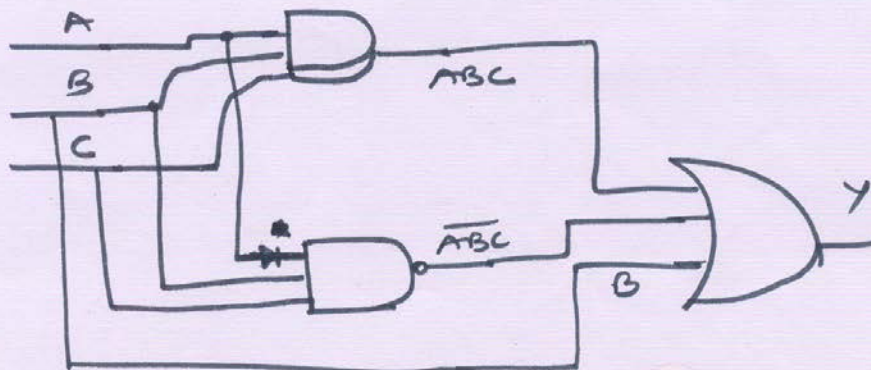

(ii) simplification.

$$Y = ABC + \overline{A}BC + B$$

$$= 1 + B$$

$$= 1$$

- Q.8** a. What is Priority encoder? Draw & explain the truth table of decimal to BCD priority encoder.

Answer: Page Number 593 of Text Book

- b. Design a Full Adder Circuit consisting of three inputs A, B, C_{IN} and two outputs S, C_{OUT} .

Answer: Page Number 320 of Text Book

- Q.9** a. Write short notes on:-
(i) NAND gate latch
(ii) Clocked D FF

Answer: 9.8 & 5.4 of Text Book

Text Books

1. Linear Integrated Circuits, Revised Second Edition, D Roy Choudhury, Shail B. Jain, New Age International Publishers.
2. Digital Systems – Principles and Applications, Ninth Edition, Ronald J Tocci, Neal S Widmer and Gregory L. Moss, Pearson Education, 2008.