

**DipIETE – ET/CS**

Time: 3 Hours

**DECEMBER 2013**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. A memory that requires refreshing is \_\_\_\_\_

- |          |               |
|----------|---------------|
| (A) ROM  | (B) SRAM      |
| (C) DRAM | (D) Flash RAM |

b. The hexadecimal representation of 177 is \_\_\_\_\_

- |         |        |
|---------|--------|
| (A) 112 | (B) B1 |
| (C) 111 | (D) 2D |

c. BCD code 11001011 represents the decimal number \_\_\_\_\_

- |         |         |
|---------|---------|
| (A) 190 | (B) 203 |
| (C) 52  | (D) 5   |

d. The sum of product of  $(x + y' + c)(x' + y' + c)$  is \_\_\_\_\_

- |               |                 |
|---------------|-----------------|
| (A) $y' + c$  | (B) $xy' + cx'$ |
| (C) $y' + xc$ | (D) $x'y + y'c$ |

e. Two RS flipflops connected sequentially with complementary clocks forms a \_\_\_\_\_

- |                            |                     |
|----------------------------|---------------------|
| (A) two bit shift register | (B) two bit counter |
| (C) JK flip flop           | (D) MS flip flop    |

f. A 8 bit synchronous counter using flip-flops each of propagation delay 12 nsec and gate delay of 8nsec, provides a transition delay of \_\_\_\_\_

- |            |             |
|------------|-------------|
| (A) 68nsec | (B) 104nsec |
| (C) 20nsec | (D) 48nsec  |

Code: DE58/DC58

Subject: LOGIC DESIGN

- g. A parallel binary adder can be made faster by
- (A) using serial adder configuration (B) gated input configuration  
(C) carry look ahead configuration (D) complementary addition system
- h. A three bit counter divides the clock by \_\_\_\_\_
- (A) 3 (B) 7  
(C) 8 (D) 2
- i. Johnson counter is realized using a \_\_\_\_\_
- (A) Ripple Counter (B) Serial Adder  
(C) Multiplexer (D) Shift Register
- j. Parallel to serial conversion requires \_\_\_\_\_
- (A) Counter (B) Multiplexer  
(C) Shift Register (D) Decoder

---

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

---

- Q.2** a. Perform the following conversions: (6)
- (i)  $(2496)_{10} = (?)_8$   
(ii)  $(CF3D)_{16} = (?)_{10}$   
(iii)  $(11011.0111)_2 = (?)_{10}$
- b. Draw the functional diagram of a digital computer and explain the function of each block. (6)
- c. Give examples of parallel and serial transmission in digital systems. (4)
- Q.3** a. What is the need to minimize a Boolean expression? What are the methods used to achieve these. (4)
- b. Minimize the following Boolean expressions and write the truth tables to show that the minimized expressions will produce the same output as the expanded expressions. (12)
- (i)  $F = m_0 + m_2 + m_5 + m_7 + m_8 + m_{10} + m_{13} + m_{15}$   
(ii)  $y = (A' + B)(A' + B + D)(C + D')$
- Q.4** a. Draw the logic diagram of eight bit serial in/parallel out shift register and explain its operation. (8)
- b. What is meant by multiplexer? List out its various applications. (4)

Code: DE58/DC58

Subject: LOGIC DESIGN

- c. Explain briefly with the help of waveforms, how propagation delay occurs in Ripple Counters? (4)
- Q.5** a. Distinguish between asynchronous and synchronous Flip Flops. Convert an asynchronous RS flip flop into synchronous latch. (6)
- b. Design a decade counter using JK Flip Flops and draw its timing diagram. (6)
- c. What is the need of Schmitt trigger devices, explain with waveforms. (4)
- Q.6** a. Build a Full Adder using two Half Adders and prove that the addition of two numbers results in subtraction when 2's complement is used. (8)
- b. If a single bit Full Adder takes 8sec for addition, calculate the total addition time taken to add two numbers having hundredth weight. Suggest a method of speeding up the addition. (8)
- Q.7** a. Design a seven segment decoder that is required to drive an active low seven segment display. (8)
- b. What are the advantages and disadvantages of a synchronous counter over an asynchronous counter? (4)
- c. How many AND gates are required to decode completely all of the states of a MOD-32 binary counter? What are the inputs to the gate that decodes for the count of 21? (4)
- Q.8** a. How will you read and write into a  $16 \times 4$  RAM? Draw a schematic of this RAM and explain the process. (8)
- b. Design a mod 7 synchronous counter and calculate its maximum frequency of operation if the flip flop delay time is 8nano sec. and gate delay time is 5nano sec. (8)
- Q.9** Explain the principle of the following: (4×4)
- (i) Magnitude Comparator
  - (ii) CPU and memory interface
  - (iii) Johnson Counter
  - (iv) DRAM