

Code: AE59

Subject: CIRCUIT THEORY

AMIETE - ET

Time: 3 Hours

JUNE 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


Q.1 Choose the correct or the best alternative in the following: (2 × 10)

- a. A  $100\Omega$  resistance is connected across a 10V battery. The energy consumed in 5 secs is

- (A) 3 Joules (B) 4 Joules  
(C) 5 Joules (D) 6 Joules

- b. The current  $I_{ab}$  in the circuit shown in Fig.1 is

- (A) 1A (B) 2A  
(C) 3A (D) 4A

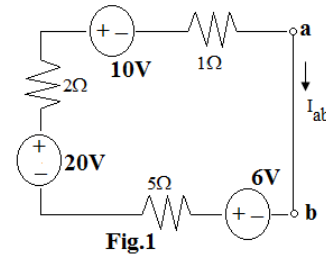

- c. The correct statement is \_\_\_\_\_

- (A)  $V_L = L \frac{di}{dt}$  and  $i_C = C \frac{dv}{dt}$  (B)  $i_L = L \frac{dv}{dt}$  and  $V_C = C \frac{di}{dt}$   
(C)  $V_L = L \frac{di}{dt}$  and  $i_L = C \frac{dv}{dt}$  (D)  $V_C = L \frac{dv}{dt}$  and  $i_C = C \frac{di}{dt}$

- d. Laplace transform of  $f(t) = e^{at} u(t)$  is

- (A)  $\frac{1}{s^2}$  (B)  $\frac{1}{s+a}$   
(C)  $\frac{1}{s-a}$  (D)  $\frac{1}{(s+a)^2}$

- e. The Quality factor of a purely resistive circuit is

- (A) 0 (B) 1  
(C) 1.5 (D) infinite

- f. The impedance of one port network  $Z(s) = \frac{15(s^3 + 2s^2 + 3s + 2)}{s^4 + 6s^3 + 8s^2}$  indicates

- (A) Double pole at origin (B) Double zeros at origin  
(C) Single pole at origin (D) Single zero at origin

g. The current  $i(t)$  corresponding to transform current  $I(s) = \frac{1}{s(s+1)}$  is

- (A)  $i(t) = (1 - e^{-t})u(t)$       (B)  $i(t) = (1 + e^{-t})u(t)$   
 (C)  $i(t) = e^t u(t)$       (D)  $i(t) = e^{-t} u(t)$

h. The Thevenin resistance as seen at  $ab$  of the circuit in Fig.2 is

- (A)  $5\Omega$       (B)  $8\Omega$   
 (C)  $10\Omega$       (D)  $12\Omega$

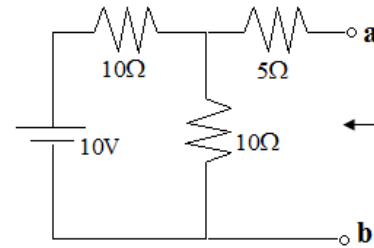


Fig.2

i. The duty cycle of a square wave is

- (A) 40%      (B) 50%  
 (C) 60%      (D) All of these

j. The minimum phase function has zeros of transmission on

- (A)  $j\omega$  axis only      (B)  $j\omega$  axis or in left half of  $s$ -plane  
 (C)  $j\omega$  axis or right half of  $s$ -plane      (D) in left half of  $s$ -plane only

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. A battery has an internal resistance of  $0.5\Omega$  and open circuit voltage of  $12V$ . What is power lost in the battery and terminal voltage on full load if a resistance of  $3\Omega$  is connected across the terminals of the battery? (4)
- b. In the Fig.3, find the current in the resistances using node analysis. (6)
- c. Find  $v_o$  using Kirchhoff's laws in the circuit as shown in Fig.4. Given that  $r_1 = 1000\Omega$ ,  $r_2 = 500\Omega$ ,  $r_3 = 50\Omega$ ,  $r_4 = 5\Omega$ ,  $\alpha = 0.5, \beta = 2$  and  $v_s = 10V$ . (6)

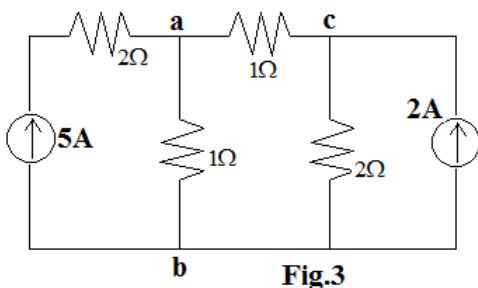


Fig.3

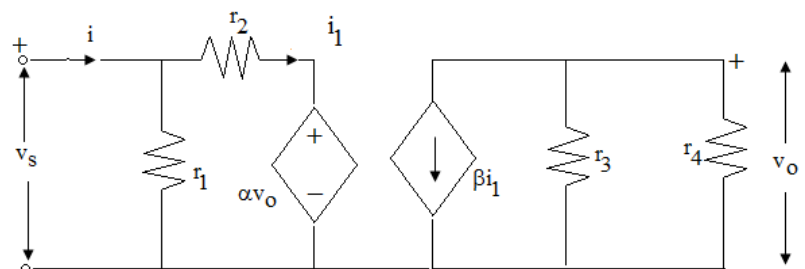


Fig.4

- Q.3** a. For the circuit given in Fig.5, switch K is closed at  $t = 0$ . Find the  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . (6)

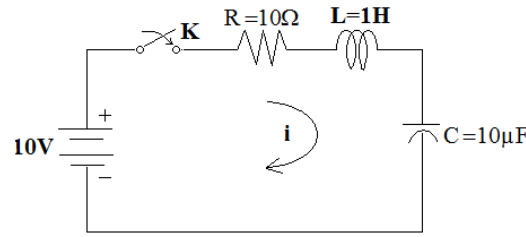


Fig.5

- b. Find the general solution of the equation  $2\frac{di}{dt} + i(t) = 2i(t)$  with initial condition at  $t = 0$ ,  $i = 5A$ . (4)
- c. A voltage of  $v = 200 \sin(314t - 30^\circ)$  is applied to a 50mH, 15Ω coil; calculate the current and the power factor for the arrangement. (6)
- Q.4** a. Using Laplace transform technique, find  $i_2$  at  $t = 0^+$  when switch k is closed at  $t = 0$  in Fig.6. (8)

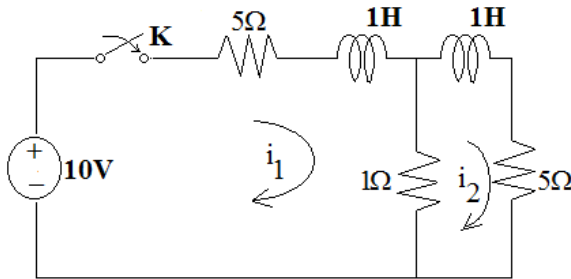


Fig.6

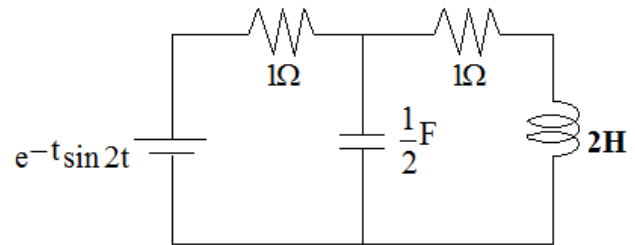


Fig.7

- Q.5** a. Determine  $Z(s)$  and  $I(s)$  for the network shown in Fig.7 using transform network. (8)
- b. Consider the network shown in Fig.8. Calculate  $i_1(t)$  using Thevenin's theorem. (8)

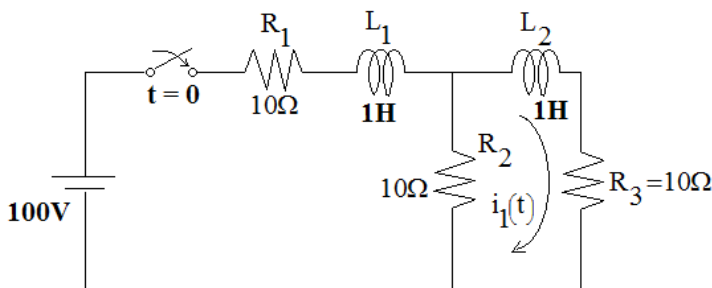


Fig.8

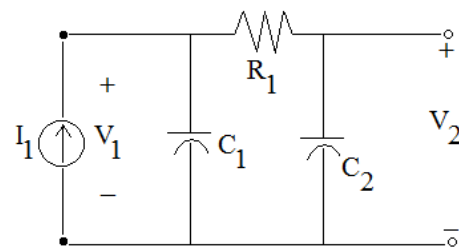


Fig.9

**Q.6** a. Compute the current gain  $\alpha_{12}(s)$  and driving point impedance  $Z_{12}(s)$  for the network shown in Fig.9 with  $C_1 = 1F$ ,  $R_1 = 1\Omega$  and  $C_2 = 2F$ . (8)

b. A network function is given by  $H(s) = \frac{2s}{(s+2)(s^2+2s+2)}$ . Obtain pole-zero diagram. (4)

c. Check the positive realness of the function  $F(s) = \frac{s^2+10s+4}{s+2}$ . (4)

**Q.7** a. Determine the Z-parameter of the network shown in Fig.10. (6)

b. The Z-parameter of a circuit are given by  $\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$ . Obtain the transmission line ABCD parameters. (4)

c. Establish the relation between Impedance parameters (Z) and hybrid parameters (h). (6)

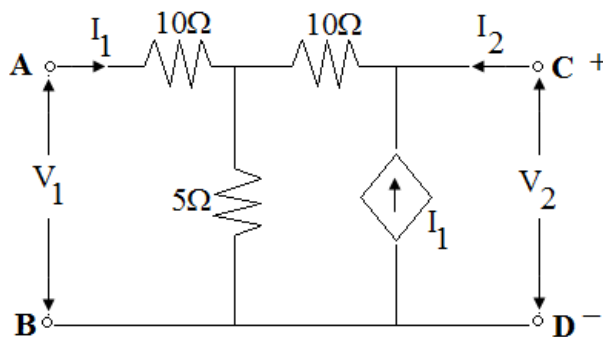


Fig.10

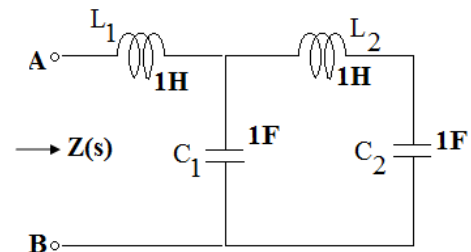


Fig.11

**Q.8** a. Obtain the driving point impedance of the given network across A-B shown in Fig.11 using Transform network. (8)

b. The driving point impedance of an LC network is  $Z(s) = \frac{10(s^2+4)(s^2+16)}{s(s^2+9)}$ . Obtain Foster form of network. (8)

**Q.9** a. What are the error criteria in any approximation problem in network theory? Derive amplitude approximation for maximally flat low pass filter approximation. (8)

b. Synthesize the voltage ratio  $\frac{V_2}{V_1} = \frac{s^2+1}{s^2+2s+1}$  as a constant resistance bridged-T network terminated in a  $1\Omega$  resistor. (8)