

DiplETE – ET

Time: 3 Hours

JUNE 2013

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED
IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER**

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The most commonly used transistor circuit configuration for power amplification is

- (A) CB (B) CC
(C) CE (D) CE, CB and CC

b. In a CE amplifier, if the emitter bypass capacitor is removed

- (A) Input resistance decreases (B) Output resistance increases
(C) Voltage gain decreases (D) Current gain increases

c. Which of the following amplifiers provides maximum efficiency

- (A) Class B amplifier (B) Class A amplifier
(C) Class AB amplifier (D) Class C amplifier

d. Which of the following is used for isolation in circuits

- (A) LED (B) Optocoupler
(C) Photo diode (D) Photo transistor

e. The slew rate of 741 C Op-Amp is

- (A) 1 V/ μ s (B) 0.5 V/ μ s
(C) 10 V/ μ s (D) 40 V/ μ s

f. The circuit shown in the Fig.1 below is

- (A) Clipper (B) Half-wave rectifier
(C) Peak detector (D) Sample & Hold circuit

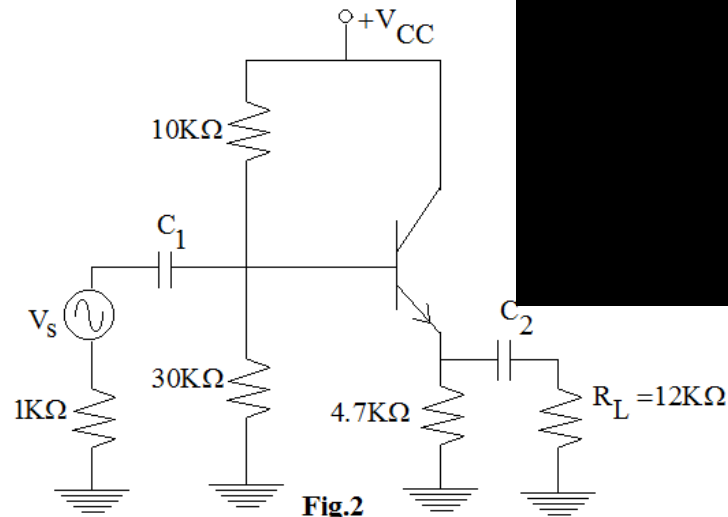


Fig.2

b. Compare the performance of CE, CC, and CB circuits. (8)

Q.4 a. Explain the drain characteristics of n-channel JFET with $V_{GS} = 0$ V. (8)

b. Explain the terms
 (i) Transconductance
 (ii) Drain Resistance
 (iii) Breakdown Voltage with respect to JFET (8)

Q.5 a. Explain, with a neat diagram, the working of a Class A transformer coupled power amplifier. (8)

b. Write a short note on LED and optocoupler. (8)

Q.6 a. Derive an expression for the gain of Non-Inverting Amplifier using op-amp. (8)

b. For the circuit shown in Fig.3 below, calculate
 (i) V_0 (ii) A_{CL}
 (iii) the load current i_L (iv) total current i_o (8)

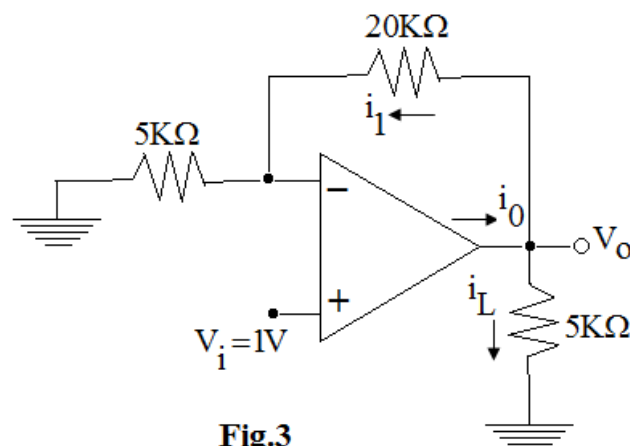


Fig.3

- Q.7** a. Draw the circuit of Inverting summing amplifier using op-amp and derive the expression for its output voltage. (8)
- b. Explain the working of the following circuits using op-amp:
(i) Peak Detector (ii) Clipper
- Q.8** a. Explain the working of a Schmitt Trigger using an op-amp. (8)
- b. Explain the working of 555 timer as monostable multivibrator. Also derive the expression of frequency of oscillation. (8)
- Q.9** a. Explain how a fixed voltage regulator can be used as a
(i) Current Source (ii) Adjustable Regulator (8)
- b. Explain the working of Counter type A/D Converter. (8)