

THE INSTITUTION OF ENGINEERS, SRI LANKA
IESL ENGINEERING COURSE PART I EXAMINATION - 2008

104 ELECTROTECHNIQUES

This paper consists of ten questions. Answer **any six (6)** questions.
 All questions carry equal marks.
 Time allowed : 3 hours

Electric space constant	ϵ_0	$= 8.854 \times 10^{-12} \text{ Fm}^{-1}$
Magnetic space constant	μ_0	$= 4\pi \times 10^{-7} \text{ Hm}^{-1}$
Gravitational constant	G	$= 6.672 \times 10^{-11} \text{ Nm}^2\text{kg}^{-2}$
Gravitational acceleration	g	$= 9.81 \text{ ms}^{-2}$
Electron rest mass	m_e	$= 9.11 \times 10^{-31} \text{ kg}$
Electron charge	e	$= 1.602 \times 10^{-19} \text{ C}$

Q1. (i) State Gauss' Law

(ii) There is a solid sphere of radius R , with uniform charge distribution. The total charge of the sphere is Q . Using Gauss' Law derive an expression for the Electric Field;

- a) Inside the sphere and
- b) Outside the sphere

Write all assumptions you make.

Q2. (i) State the formula for the Capacitance of a parallel-plate capacitor, and discuss briefly how a change in each value affects the capacitance.

(ii)

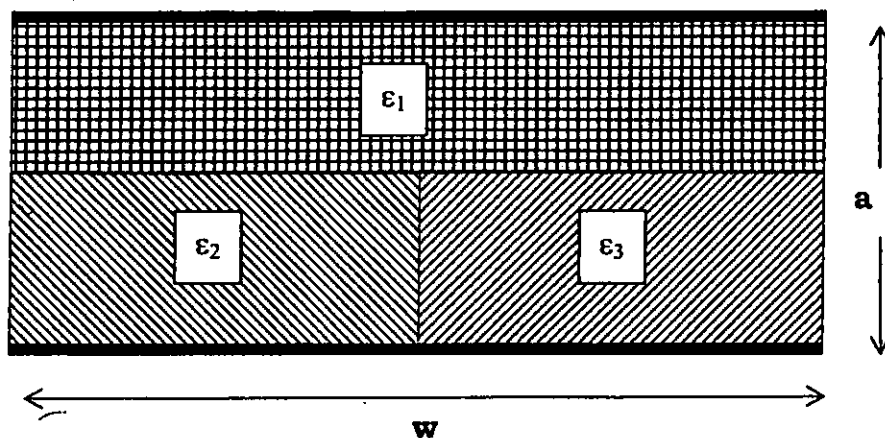


Figure Q2

Two rectangular conducting flat plates of length l and width w are kept at a distance a by filling the space between the two plates with three dielectrics as shown in **Figure Q2**. Half the space is filled with a dielectric ϵ_1 , the other half is filled in equal amount with ϵ_2 and ϵ_3 material as shown.

- If a voltage is to be applied across the two plates, write an expression for the total capacitance of the system in terms of l , w , a , ϵ_1 , ϵ_2 , and ϵ_3 .
- Calculate the total capacitance for values give below:
 $l = 20\text{cm}$ $w = 10\text{cm}$ $a = 8\text{mm}$
 relative dielectric constants $\epsilon_1 = 4$, $\epsilon_2 = 2$, $\epsilon_3 = 3$.

Q3. (i) State **the condition** for two elements to be connected in
 a) series; b) parallel; in an electronic circuit.

(ii) Twelve 1Ω resistors are connected into a cube as shown in **Figure Q3** below.

All resistors = 1 ohm

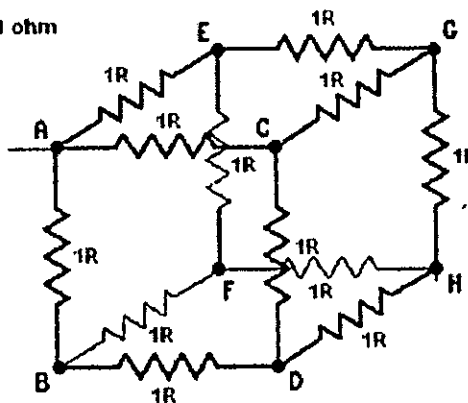


Figure Q3

Calculate the equivalent resistance of this cube, when measured between

- points **A** and **H**,
- points **A** and **B**.

Write all assumptions you make.

Q4. (i) Describe briefly the two Kirchhoff's Laws of electric circuits.

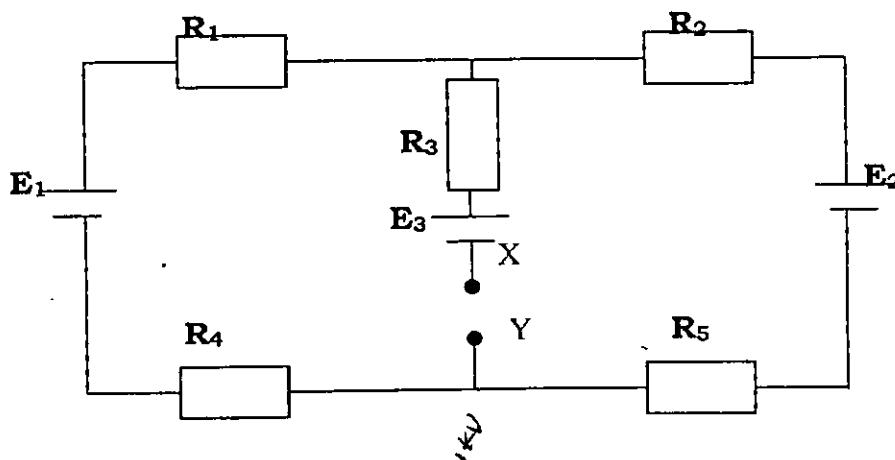


Figure Q4

(25)

- (ii) Calculate the potential difference between terminals X and Y in Fig. given that
 $R_1 = 12\Omega$; $R_2 = 22\Omega$; $R_3 = 36\Omega$; $R_4 = 20\Omega$; $R_5 = 46\Omega$; $E_1 = 12V$; $E_2 = 48V$
 and $E_3 = 24V$.

Q5. (i) Describe Ampère's Law.

- (ii) A coaxial cable consists of an inner solid conductor of radius a , and an outer concentric (pipe like) conductor of inner radius b_i and outer radius b_o . The inner conductor carries a current I in the opposite direction to the current flow of the outer conductor, which also carries the same I amount of current. Assume that the current density within a conductor is uniform. Calculate the magnetic field for the regions
 a) $r < a$; b) $a < r < b_i$; c) $b_i < r < b_o$; and d) $b_o < r$

Q6. (i) Describe Lenz's Law of induction.

- (ii) A thin metal strip is allowed to slide down frictionless parallel rails of negligible resistance. The rails are connected at the bottom end, and elevated at an angle θ above the horizontal. A uniform magnetic field B is directed vertically upward throughout the region. The strip has a mass m , and a resistance R . The minimum distance between the rails is d .

- a) Derive an expression for the terminal speed v_t of the strip in terms of m , B , θ , R , and d .
 b) Calculate v_t , given that $m = 35g$, $B = 1.5T$, $\theta = 30^\circ$, $R = 20\Omega$, and $d = 30cm$.

- Q7. (i) Describe briefly the behaviour of
 a) a capacitor
 b) an inductor in a sinusoidal circuit.

(ii)

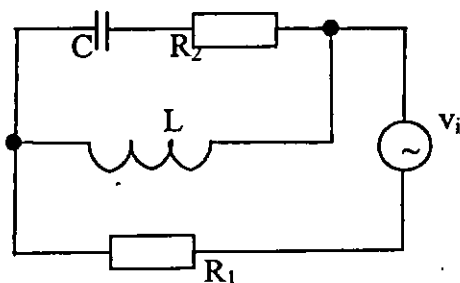


Figure Q7

- In the above circuit v_i is described as $v_i = 17 \sin(1000t)$ V. Given $R_1 = 500\Omega$, $R_2 = 3002\mu F$, $L = 400mH$, and $C = 2\mu F$;
 a) calculate the currents through all elements.
 b) Draw the phasor diagram for the circuit.

- Q8. (i) A resistor R , a capacitor C , and an inductor L are connected in series with one another. A power source of variable frequency is connected in series with this circuit. When the source frequency is set to the resonance frequency f_0 , a current I_0 flows from the source. The elements are then replaced by those of twice the value, $2R$, $2C$ and $2L$ respectively.
- What is the new resonance frequency in terms of f_0 ?
 - What is the new current drawn from the source at resonance in terms of I_0 ?
- (ii) A simple choke can be modelled as an ideal inductor connected in series with an ohmic resistor. A capacitor is connected in parallel to such a simple choke. Given $C = 20\mu\text{F}$; $L = 50\text{mH}$ and $R_L = 10\Omega$, calculate the resonance frequency for the circuit.
- Q9. (i) Real ammeters and voltmeters may present problems when measuring very large, or very small loads. Show, and describe briefly how best to connect an ammeter and a voltmeter to accurately measure
- Voltage across a very large load
 - Current through a very small load.
- (ii) A simple permanent-magnet galvanometer shows full-scale deflection at 100mV and 1mA . How can this be used to construct a metre able to measure up to
- 100V and
 - 20A
- Q10. (i) Devise a 2-input NOR gate, using only the minimum number of 2-input NAND gates.
- (ii) A simple display is to be constructed to help small children to identify prime numbers. Buttons carrying integers between 0 and 9 are given, so that only one button can be pressed at a time. The lamp lights up only when a button with a primary number is pressed. Use a Karnaugh-map to find a simplified logical expression for the above display.