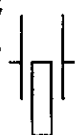


THE INSTITUTION OF ENGINEERS, SRI LANKA
IESL ENGINEERING COURSE PART I EXAMINATION-2010

104 ELECTROTECHNIQUES

This paper consists of ten questions. Answer **any six (6)** questions.
 All questions carry equal marks.
 Time allowed : 3 hours

Electric space constant	ϵ_0	$= 8.854 \times 10^{-12} \text{ Fm}^{-1}$
Magnetic space constant	μ_0	$= 4\pi \times 10^{-7} \text{ Hm}^{-1}$
Gravitational constant	G	$= 6.672 \times 10^{-11} \text{ Nm}^2\text{kg}^{-2}$
Gravitational acceleration	g	$= 9.81 \text{ ms}^{-2}$
Electron rest mass	m_e	$= 9.11 \times 10^{-31} \text{ kg}$
Electron charge	e	$= 1.602 \times 10^{-19} \text{ C}$

- Q1.** (i) State Gauss's Law
- (ii) A solid conducting sphere carrying charge q has radius a . It is inside a concentric hollow conducting sphere with inner radius b and outer radius c . The hollow sphere has no net charge
- (a) Derive expressions for the electric-field magnitude in terms of the distance r from the centre for the regions $r < a$, $a < r < b$, $b < r < c$, and $r > c$.
- (b) Graph the magnitude of the electric field as a function of r from $r = 0$ to $r = 2c$.
- (c) What is the charge on the inner surface of the hollow sphere?
- (d) What is the charge on the outer surface?
- (e) Sketch the field lines of the system within a spherical volume of radius $2c$.
- Q2.** (i) Describe the **behaviour** of two capacitors connected in series.
- (ii) A parallel-plate capacitor with only air between the plates is charged by connecting it to a battery. The capacitor is then disconnected from the battery, without any of the charge leaving the plates. The reading of a voltmeter is 45 V when placed across the capacitor. When a dielectric is inserted between the plates, completely filling the space, the voltmeter reads 11.5 V.
- 
- (a) What is the dielectric constant of this material?
- (b) What will the voltmeter read if the dielectric is now pulled partway out - parallel to the plates, so it fills only one-third of the space between the plates?
- Q3.** (i) The potential difference across the terminals of a battery is 8.4 V when there is a current of 1.50 A in the battery from the negative to the positive terminal. When the current is 3.50 A in the reverse direction, the potential difference becomes 9.4 V.
- (a) What is the internal resistance of the battery?
- (b) What is the emf of the battery?
- (ii) A 60 W, 120 V light bulb and a 200 W, 120 V light bulb are connected in series across a 240 V line. Assume that the resistance of each bulb does not vary with current. (A light bulb gives the power it dissipates when connected to the stated potential difference; that is, a 25 W, 120 V light bulb dissipates 25 W when connected to a 120 V line.)

- (c) Find the current through the bulbs.
- (d) Find the power dissipated in each bulb.
- (e) One bulb burns out very quickly. Which one? Why?

Q4. (i) Describe Coulomb's Law.

(ii) Two identical spheres are each attached to silk threads of length $L = 0.5$ m and hung from a common point. Each sphere has mass $m = 8$ g. The radius of each sphere is very small compared to the distance between the spheres, so they may be treated as point charges. One sphere is given positive charge q_1 , and the other a different positive charge q_2 ; this causes the spheres to separate so that when the spheres are in equilibrium, each thread makes an angle $\theta = 20^\circ$ with the vertical.

- (a) Determine the magnitude of the electrostatic force that acts on each sphere, and determine the tension in each thread.
- (b) Based on the information you have been given, what can you say about the magnitudes of q_1 and q_2 ?

A small wire is now connected between the spheres, allowing charge to be transferred from one sphere to the other until the two spheres have equal charges; the wire is then removed. Each thread now makes an angle of 30° with the vertical.

- (c) Determine the values of original charges.

Q5. (i) Describe Faraday's Law.

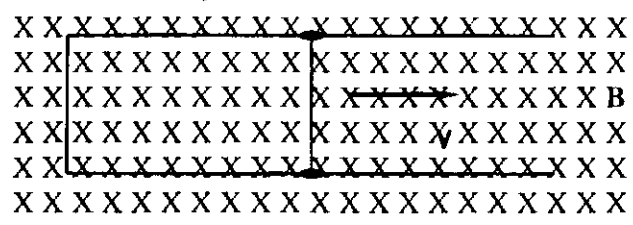



Figure Q5

(ii) A rectangular horizontal loop with width L and a slide wire with mass m are as shown in Fig. Q5. A uniform magnetic field \mathbf{B} is directed perpendicular to the plane of the loop into the plane of the figure. The slide wire is given an initial speed of v_0 and then released. There is no friction between the slide wire and the loop, and the resistance of the loop is negligible in comparison to the resistance R of the slide wire.

- (a) Obtain an expression for current I of the circuit while it is moving at speed v .
- (b) Obtain an expression for F , the magnitude of the force exerted on the wire while it is moving at that speed v .
- (b) What is the distance x that the wire moves before coming to rest?

Q6. (i) Describe the condition under which there is maximum power transfer to a load from an electric circuit.

(ii)

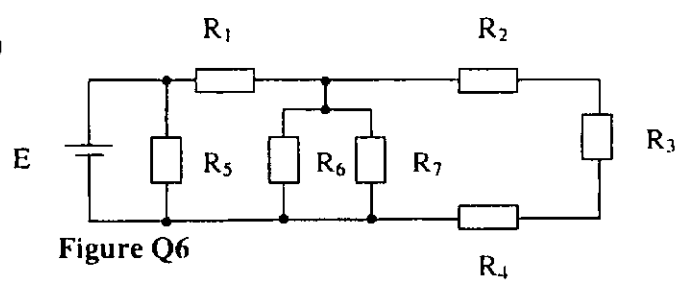

- $R_1 = 5 \Omega$
- $R_2 = 4 \Omega$
- $R_3 = 2 \Omega$
- $R_4 = 8 \Omega$
- $R_5 = 50 \Omega$
- $R_6 = 10 \Omega$
- $R_7 = 10 \Omega$
- $E = 20 \text{ V}$

Figure Q6


- (a) Calculate, using Thevenin's Theorem, the current flowing through R_3 .
- (b) The power dissipated from R_3 .

You are to replace R_3 with another resistor R_3' , so that maximum power can be drawn from it.

- (c) What is the suitable value for R_3' ?
- (d) How much is the power dissipated across R_3' ?

- Q7.** (i) Describe briefly the behaviour of
- a) a capacitor
 - b) an inductor
- in a sinusoidal circuit.

(ii)

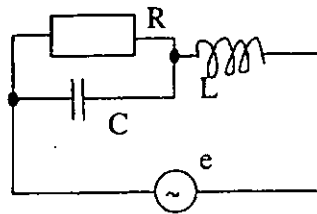

$R = 300 \Omega$
 $L = 500 \text{ mH},$
 $C = 2.5 \mu\text{F}$

Figure Q7 (For Q7 and Q8)

- (a) Given $e = 34 \sin 1000t \text{ V}$, calculate the currents through all the components.
- (b) Calculate i) the power dissipated from the circuit and ii) its power factor.
- (c) Draw a phasor diagram for the circuit.

- Q8.** (i) Describe the characteristic of a resonant circuit.

(ii) Now the above circuit (Fig. Q7) is set to its resonance situation, where the same components are used, and amplitude may be assumed unchanged at 34 V.

- (a) Calculate the currents through all the components.
- (b) Draw a phasor diagram for the circuit.

- Q9.** (i) Describe the phenomenon mutual inductance.

(ii) A solenoidal coil with 25 turns of wire is wound tightly around another coil with 300 turns. The inner solenoid is 25 cm long and has a diameter of 2 cm. At a certain time, the current in the inner solenoid is 0.12 A, and is increasing at a rate of $1.75 \times 10^3 \text{ A/s}$. For this time, calculate;

- (a) the average magnetic flux through each turn of the inner solenoid;
- (b) the mutual inductance of the two solenoids;
- (c) the emf induced in the outer solenoid by the changing current in the inner solenoid.

Q10. (i) Design a 2-input NOR gate, using only the minimum number of 2-input NAND gates.

(ii) A simple Boolean function is described as

$$F = \overline{A}BCD + A\overline{B}CD + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + ABCD$$

(a) Draw a truth table describing the function.

(b) Use a Karnaugh-map to find a simplified logical expression for the above function.