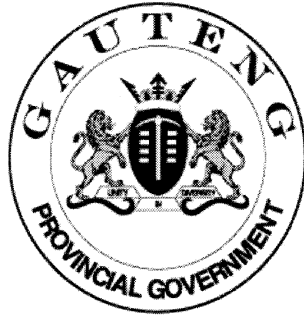


**SENIOR CERTIFICATE EXAMINATION
SENIORSERTIFIKAAT-EKSAMEN**



**OCTOBER / NOVEMBER
OKTOBER / NOVEMBER**

2004

ELECTRICIANS WORK

***ELEKTRISIËNS-
WERK***



703-2/0

**6 pages
6 bladsye**

ELECTRICIANS WORK SG



**COPYRIGHT RESERVED / KOPIEREG VOORBEHOU
APPROVED BY UMALUSI / GOEDGEKEUR DEUR UMALUSI**



GAUTENGSE DEPARTEMENT VAN ONDERWYS
SENIORSERTIFIKAAT-EKSAMEN

ELEKTRISIËNSWERK SG

TYD: 3 uur

PUNTE: 200

BENODIGHEDE:

- Tekeninstrumente en 'n goedgekeurde nieprogrammeerbare sakrekenaar.

INSTRUKSIES:

- Beantwoord AL die vrae.
- Trek 'n lyn dwarsoor die bladsy na beantwoording van elke vraag.
- Formules en berekeninge moet, waar van toepassing, getoon word.
- 'n Lys van formules word verskaf.

**VRAAG 1
ELEKTRIESE STROOMTEORIE**

- 1.1 'n Sekere spoel is oor 'n 120 V gs-toevoer verbind, en die stroomvloeï was 1,5 ampère. Dieselfde spoel is daarna oor 'n 220 V, 50 Hz ws-toevoer verbind en die stroom was 0,6 ampère. Bereken die induktansie van die spoel. (13)
- 1.2 Noem DRIE tipes belastings wat 'n nalopende arbeidsfaktor sal veroorsaak. (3)
- 1.3 Definieer die term **arbeidsfaktor**. (3)
- 1.4 Die onderstaande tabel toon die oombliklike waardes van 'n wisselstroom oor 'n halwe siklus:

Hoek in grade	0	30	60	90	120	150	180
Stroom in ampère	0	4	6	12	6	2	0

- 1.4.1 Teken 'n grafiek van hierdie waardes waar 40 mm gelyk is aan 30 grade op die X-as en 10 mm gelyk is aan 1 ampère op die Y-as. Verbind hierdie punte met reguit lyne en dui die middel-ordinate aan. (8)
- 1.4.2 Bepaal die vormfaktor. (9)

GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION

ELECTRICIANS WORK SG

TIME: 3 hours

MARKS: 200

REQUIREMENTS:

- Drawing instruments and an approved non-programmable calculator.

INSTRUCTIONS:

- Answer ALL the questions.
 - Draw a line after answering each question.
 - Formulae and calculations, where applicable, must be shown.
 - A list of formulae is provided.
-
-

**QUESTION 1
ELECTRICAL CURRENT THEORY**

- 1.1 When a certain coil was connected to a 120 d.c. supply, a current of 1,5 amperes was drawn. The same coil was then connected to a 220 V, 50 Hz supply and the current drawn was 0,6 amperes. Determine the inductance of the coil. (13)
- 1.2 Name THREE types of loads that will cause a lagging power factor. (3)
- 1.3 Define the term **power factor**. (3)
- 1.4 The table below shows the instantaneous values of an alternating current over half a cycle:

Angle in degrees	0	30	60	90	120	150	180
Current in amperes	0	4	6	12	6	2	0

- 1.4.1 Draw a graph of these values where 40 mm is equal to 30 degrees on the x-axis and 10 mm is equal to 1 ampere on the Y-axis. Join these values with straight lines and indicate the mid-ordinates. (8)
- 1.4.2 Determine the form factor. (9)

- 1.5 'n Seriekring bestaan uit 'n resistor van 25 ohm, 'n induktor van 0,3 henry en 'n kapasitor van 160 mikrofarad. As die toevoerspanning 100 V, 100 Hz is
- 1.5.1 bereken die stroom in die kring. (9)
- 1.5.2 bereken die fasehoek tussen die stroom en die spanning. (3)
- 1.5.3 bereken die drywingsfaktor. (2)
- 1.5.4 bereken die aktiewe stroom in die kring. (3)
- 1.5.5 bereken die totale drywing van die kring. (3)
- 1.5.6 Skets die fasordiagram met al die inligting aangedui (nie volgens skaal nie). (4)
- [60]**

VRAAG 2 INSTRUMENTE EN DRIEFASE-STELSELS

- 2.1 Teken 'n netjiese benoemde skets van 'n dinamometer-tipe wattmeter. (10)
- 2.2 Teken 'n kringdiagram om aan te toon hoe drie wattmeters gekoppel moet word om die totale drywing in 'n driefasige vierdraad-stelsel te meet. (8)
- 2.3 'n Driefasige delta-verbinde motor trek 30 A vanaf 'n 380V-toevoer teen 'n arbeidsfaktor van 0,9 nalopend.
- Bereken
- 2.3.1 die insetdrywing. (3)
- 2.3.2 die skyndrywing. (3)
- 2.3.3 die fasestroom van die motorwikkeling. (3)
- 2.3.4 die vollas-rendement van die motor, as die kraglewering as 12 kW aangegee word. (3)
- 2.4 Noem DRIE instrumente waarmee die arbeidsfaktor in 'n enkelfase-kring bepaal kan word. (3)
- 2.5 As die fasespanning van 'n driefase-ster-verbinde generator 220 V is, wat sal die lynspanning wees? (3)
- 2.6 'n Enkelfase-motor gebruik 'n stroom van 5 A wanneer dit aan 'n 220 V-toevoer verbind word. Die wattmeter wat in die stroombaan verbind is, lees 0,85 kW. Bereken die drywingsfaktor van die kring. (4)
- [40]**

- 1.5 A series circuit consists of a resistor of 25 ohms, an inductor of 0,3 henry and a capacitor of 160 micro-farads. The supply voltage is 100 V, 100 Hz.
- 1.5.1 Calculate the current in the circuit. (9)
- 1.5.2 Calculate the phase angle between the current and the voltage. (3)
- 1.5.3 Calculate the power factor. (2)
- 1.5.4 Calculate the active current in the circuit. (3)
- 1.5.5 Calculate the total power of the circuit. (3)
- 1.5.6 Draw (not to scale) a phasor diagram with all the information given. (4)
- [60]**

QUESTION 2
INSTRUMENTS AND THREE-PHASE SYSTEMS

- 2.1 Make a neat, labelled sketch of a dynamometer-type wattmeter. (10)
- 2.2 Draw a circuit diagram to illustrate how three wattmeters should be connected to measure the power in a three-phase four-wire system. (8)
- 2.3 A three-phase delta-connected motor draws 30 A from a 380 V supply at a power factor of 0,9 lagging.
- Calculate
- 2.3.1 the input power. (3)
- 2.3.2 the apparent power. (3)
- 2.3.3 the phase current of the motor winding. (3)
- 2.3.4 the full load efficiency of the motor if the output power is given as 12 kW. (3)
- 2.4 Name THREE instruments with which to determine the power factor of a single-phase circuit. (3)
- 2.5 If the phase voltage of a three-phase star-connected generator is 220 V, what will the line voltage be? (3)
- 2.6 A single-phase motor takes up a current of 5A when connected to 220 V supply. The wattmeter connected in the circuit reads 0,85 kW. Calculate the power factor of the circuit. (4)
- [40]**

**VRAAG 3
TRANSFORMATORS**

- 3.1 'n Eenfasige 140 kVA-transformator met 'n toevoer van 2 000 volt, 50 hertz het 'n uitset van 250 volt. Die sekondêre wikkeling het 100 windings. Bereken die
- 3.1.1 getal primêre windings. (3)
- 3.1.2 primêre stroom. (3)
- 3.2 'n Driefase-transformator het 400 primêre en 30 sekondêre windings. Die toevoerspanning is 3 300 volt. Bereken in elke geval die waarde van die sekondêre lynspanning wanneer die transformator verbind word in
- 3.2.1 ster-delta. (7)
- 3.2.2 delta-ster. (7)
- 3.3 Teken 'n netjiese, benoemde diagram om te wys hoe drie enkelfase-transformators aan 'n driefase-toevoer gekoppel kan word, met die primêre wikkeling in delta en die sekondêre wikkeling in ster gekonnekteer. (9)
- 3.4 Noem die verskillende toetse wat op 'n transformator uitgevoer kan word. (4)
- 3.5 Noem TWEE verliese wat in die ysterkern van transformators plaasvind. (2)
- [35]

**VRAAG 4
WISSELSTROOM-MOTORE**

- 4.1 Skets 'n netjiese benoemde diagram van 'n kapasitor-induksie-motor. (8)
- 4.2 Noem VIER nadele van sinchrone motors, wanneer dit met gewone induksie-motors vergelyk word. (8)
- 4.3 Skets 'n netjiese, benoemde kringdiagram van 'n driefase handbediende ster-delta-aansitter. (12)
- 4.4 'n Tweepool-driefase-induksiemotor word aan 'n 380 volt, 50 Hz-toevoer verbind. Die glijp van die motor is 3%. Bereken die rotorspoed. (7)
- [35]

QUESTION 3
TRANSFORMERS

- 3.1 A single-phase 140 kVA transformer with a supply of 2 000 volt, 50 hertz has an output of 250 volt. The secondary winding has 100 turns. Calculate the
- 3.1.1 number of primary turns. (3)
- 3.1.2 primary current. (3)
- 3.2 A three-phase transformer has 400 primary and 30 secondary turns. The supply voltage is 3 300 volts. Calculate, in each case, the value of the secondary line voltage when the transformer is connected in
- 3.2.1 star-delta. (7)
- 3.2.2 delta-star. (7)
- 3.3 Make a neat diagrammatic sketch to show how three single-phase transformers may be connected to a three-phase supply, with the primary side in delta and the secondary side in star connection. (9)
- 3.4 Name the different tests which can be carried out on a transformer. (4)
- 3.5 Name the TWO losses which occur in the iron core in transformers. (2)
- [35]**

QUESTION 4
ALTERNATING-CURRENT MOTORS

- 4.1 Draw a neat, labelled circuit diagram of a capacitor-induction motor. (8)
- 4.2 Name FOUR disadvantages of synchronous motors, when compared to ordinary induction motors. (8)
- 4.3 Draw a neat, labelled circuit diagram of a three-phase manual star-delta starter. (12)
- 4.4 A 2-pole, three-phase induction motor is connected to a 380 volt, 50 Hz supply. The slip of the motor is 3%. Calculate the rotor speed. (7)
- [35]**

VRAAG 5
ELEKTRONIKA EN VEILIGHEID

- 5.1 Wat is die kenmerke van 'n transistorkring in 'n gemeenskaplike kollektor-konfigurasie? (8)
- 5.2 Teken 'n kringdiagram van 'n transistor in 'n eenvoudige versterker-kring. Toon die inset- en uitsetgolf-vorms. (8)
- 5.3 Noem VIER voordele van halfgeleier-diodes, wanneer hulle vergelyk word met buisdiodes. (8)
- 5.4 Verduidelik hoe Vigs van een persoon na 'n ander oorgedra kan word. (6)

[30]

TOTAAL: 200

QUESTION 5
ELECTRONICS AND SAFETY

- 5.1 What are the characteristics of a transistor circuit in a common collector configuration? (8)
- 5.2 Draw a circuit diagram of a transistor in a simple amplifier circuit. Show the input and output waveforms. (8)
- 5.3 Name FOUR advantages of semiconductor diodes, when compared to tube diodes. (8)
- 5.4 Explain how Aids can be spread from one person to another. (6)
- [30]**

TOTAL: 200

FORMULA SHEET

FORMULEBLAD

$$Z = \sqrt{R^2 + (X_L \approx X_C)^2}$$

$$V_R = I_T \times R$$

$$I_T = \frac{V_T}{Z}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_L = I_T \times X_L$$

$$V_C = I_T \times X_C$$

$$I_T = \sqrt{I_R^2 + (I_C \approx I_L)^2}$$

$$I_R = \frac{V_R}{R};$$

$$I_L = \frac{V_L}{X_L};$$

$$I_C = \frac{V_C}{X_C};$$

$$\cos \theta = \frac{I_R}{I_T}$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

$$P = V \times I \times \cos \theta$$

$$\cos \theta = \frac{R}{Z}$$

$$\tan \theta = \frac{X_L - X_C}{R};$$

$$\cos \theta = \frac{P}{VA}$$

$$P = I^2 R$$

$$I_{act} = I \times \cos \theta$$

$$I_{react} = I \times \sin \theta$$

Star/ster

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} \times V_{ph}$$

Delta/delta

$$I_L = \sqrt{3} \times I_{ph}$$

$$V_L = V_{ph}$$

$$F = \frac{pN}{60}$$

$$S = \frac{N_s - N_R}{N_s} \times 100\%$$

$$N_R = \frac{f}{p} (1 - s)$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos \theta$$

$$S = \sqrt{3} \times V_L \times I_L;$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p} \text{ or / of } \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Rendement} = \frac{\text{Afvoer}}{\text{Invoer}}$$

END / EINDE