

**GAUTENG DEPARTMENT OF EDUCATION**  
**SENIOR CERTIFICATE EXAMINATION**

**ELECTRICIANS WORK SG**

**TIME: 3 hours**

**MARKS: 200**

---

---

**REQUIREMENTS:**

- Drawing instruments and an approved non-programmable calculator

**INSTRUCTIONS:**

- Answer ALL the questions.
  - Draw a line across the page in your answer book upon completion of each question.
  - Formulae and calculations, where applicable, must be shown.
  - A list of formulae is provided.
- 
- 

**QUESTION 1**  
**ELECTRICAL CURRENT THEORY**

- 1.1 An alternating voltage with the equation  $v = 60 \sin (314 t)$  is connected across a 45 ohm resistor.
- 1.1.1 Determine the current through the resistor as measured by an ammeter. (5)
- 1.1.2 Calculate the frequency of the alternating voltage. (3)
- 1.1.3 Calculate the instantaneous value of the voltage 3 milliseconds after it has been switched on. (6)
- 1.2 The instantaneous value of a current with a sinusoidal wave form is 5 amperes after 5 milliseconds. Calculate the maximum value which the current will reach if the period of the cycle is 20 milliseconds. (7)
- 1.3 Explain the meaning of the term impedance with regards to ac circuits. (3)

- 1.4 A series circuit consists of a resistor of 55 ohms, an inductor of 0,4 henry and a capacitor of 160 microfarad. If the supply voltage is 150 V / 100 Hz, calculate the
- 1.4.1 current in the circuit. (12)
  - 1.4.2 phase angle between the current and the voltage. (3)
  - 1.4.3 power factor. (2)
  - 1.4.4 active current in the circuit. (3)
  - 1.4.5 reactive current in the circuit. (3)
- 1.5 Name THREE disadvantages of a low power factor. (3)  
**[50]**

**QUESTION 2**  
**INSTRUMENTS**

- 2.1 Sketch a neat, labelled diagram of a single-phase induction-type wattmeter. The connections of the meter to the supply and the load must be clearly shown. (13)
- 2.2 Discuss the vibrating-reed frequency meter under the following headings:
- 2.2.1 Construction (3)
  - 2.2.2 Operation (4)  
**[20]**

**QUESTION 3**  
**THREE-PHASE ALTERNATING-CURRENT SYSTEMS**

- 3.1 Three pure resistances of 40 ohms each are connected to a balanced 380 V three-phase supply.
- Calculate the
- 3.1.1 phase voltage, current, line current and power when these resistances are connected in star. (10)
  - 3.1.2 phase voltage, current, line current and power when these resistances are connected in delta. (9)

- 3.2 A 200 kW three-phase, delta-connected motor is connected to a 500 V supply. The power factor is 0,9 and the efficiency is 90%.

Calculate the

- 3.2.1 line current of the motor. (8)
- 3.2.2 phase current of the motor. (3)
- [30]**

#### QUESTION 4 TRANSFORMERS

- 4.1 Name TWO functions of the Bucholz relay. (2)
- 4.2 A single-phase 120 kVA transformer with a supply of 2 000 volt / 50 hertz has an output of 400 volt. The secondary winding has 150 turns.

Calculate the

- 4.2.1 number of primary turns. (4)
- 4.2.2 primary current. (3)
- 4.2.3 secondary current. (3)
- 4.3 A three-phase transformer with 3 000 turns on the primary is connected in delta-star to a supply voltage of 6 000 V. The full load line current on the primary is 25 A when the secondary line voltage is 380 V and the power factor is 0,9.

Calculate the

- 4.3.1 secondary phase voltage. (4)
- 4.3.2 transformation (turns) ratio. (4)
- 4.3.3 number of secondary turns. (4)
- 4.3.4 primary phase current. (4)
- 4.4 State TWO losses that occur in transformers. (2)
- [30]**

**QUESTION 5  
ALTERNATING-CURRENT MOTORS**

- 5.1 Explain briefly the difference between synchronous speed and rotor speed. (4)
- 5.2 Name THREE tests that must be performed on the windings of a new electric motor before it is put into operation. (3)
- 5.3 A three-phase induction motor can supply a maximum power of 15 kW to a machine. Calculate the current value on which the overload unit must be set if a 7% overload is permitted. The supply voltage to the motor is 380 V, with a lagging power factor of 0,9. The efficiency of the motor is 95%. (10)
- 5.4 Draw a neat, labelled drawing of the starting circuit of a slipring-motor-starter. (15)
- 5.5 Name FOUR disadvantages of synchronous motors, when compared with ordinary induction motors. (4)
- 5.6 Mention the TWO factors which determine the speed of an induction-type alternating-current motor. (2)
- 5.7 Explain how the direction of a rotation can be changed in a three-phase motor. (2)
- [40]**

**QUESTION 6  
ELECTRONICS**

- 6.1 Draw a neat, labelled sketch of a cathode-ray tube. (9)
- 6.2 What are the characteristics of a transistor with a common-emitter configuration? (3)
- 6.3 Under which biasing conditions will the NPN transistor function correctly? (4)
- 6.4 What is the function of a Zener diode? (2)
- 6.5 How can maximum deflection on a cathode-ray tube be obtained? (2)
- [20]**

**QUESTION 7  
SAFETY**

- 7.1 Explain what you would do if you noticed that a learner in the workshop was being shocked by an electrical supply. (5)
- 7.2 State the FIVE basic causes of accidents. (5)
- [10]**

**TOTAL: 200**

**FORMULA SHEET**

**FORMULEBLAD**

$$Z = \sqrt{R^2 + (X_L \approx X_c)^2}$$

$$V_R = I_T \times R$$

$$I_T = \frac{V_T}{Z}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$V_L = I_T \times X_L$$

$$V_c = I_T \times X_c$$

$$I_T = \sqrt{I_R^2 + (I_c \approx I_L)^2} \quad I_R = \frac{V_R}{R}; \quad I_L = \frac{V_L}{X_L}; \quad I_c = \frac{V_c}{X_c}; \quad \text{Cos}\theta = \frac{I_R}{I_T}$$

$$X_L = 2\pi fL \quad X_c = \frac{1}{2\pi fC}$$

$$P = V \times I \times \text{Cos}\theta \quad \text{Cos}\theta = \frac{R}{Z} \quad \text{Tan}\theta = \frac{X_L - X_c}{R}; \quad \text{Cos}\theta = \frac{P}{VA}$$

$$P = I^2 R$$

$$I_{\text{act}} = I \times \text{cos}\theta$$

$$I_{\text{react}} = I \times \text{sin}\theta$$

Star/ster

Delta / delta

$$I_L = I_{\text{ph}}$$

$$I_L = \sqrt{3} \times I_{\text{ph}}$$

$$V_L = \sqrt{3} \times V_{\text{ph}}$$

$$V_L = V_{\text{ph}}$$

$$F = \frac{pN}{60} \quad S = \frac{N_s - N_R}{N_s} \times 100\% \quad N_R = \frac{f}{p} (1-s)$$

$$P = \sqrt{3} \times V_L \times I_L \times \text{cos}\theta$$

$$S = \sqrt{3} \times V_L \times I_L; \quad \frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p} \text{ or / of } \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Rendement} = \frac{\text{Afvoer}}{\text{Invoer}}$$

**END / EINDE**