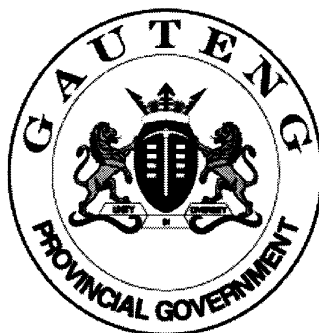


SENIOR CERTIFICATE EXAMINATION



FEBRUARY / MARCH

2007

ELECTRICIANS WORK

SG

703-2/0 E

ELECTRICIANS WORK SG



703 2 0E

SG

6 pages

X05



COPYRIGHT RESERVED
APPROVED BY UMALUSI



GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION

ELECTRICIANS WORK SG

TIME: 3 hours

MARKS: 200

REQUIREMENTS:

- Drawing instruments and an approved non-programmable calculator

INSTRUCTIONS:

- Answer ALL the questions.
- Draw a line across the page in your answer book upon completion of each question.
- Formulae and calculations, where applicable, must be shown.
- A list of formulae appears on the last page of the question paper.

**QUESTION 1
ELECTRICAL CURRENT THEORY**

- 1.1 A parallel circuit consists of a non-inductive resistance of 20 ohms, an inductor of 35 mH, and a capacitor of 180 microfarad. The supply voltage is 150 V / 50 Hz.

Calculate the

- 1.1.1 current through each component. (12)
- 1.1.2 total current. (3)
- 1.1.3 impedance. (3)
- 1.2 The following midordinate values are obtained from a graph which represents the instantaneous values of an alternating current over a half cycle.

Midordinate	i1	i2	i3	i4	i5	i6
Current in ampere	2	5	8	9	6	3

Use these midordinate values and calculate

- 1.2.1 the form factor. (10)

- 1.3 Of which TWO components does the current drawn from a supply consist? (2)
- 1.4 A series circuit consists of a resistor of 25 ohms, an inductor of 0,3 henry and a capacitor of 160 microfarad. If the supply voltage is 100 V / 100 Hz, calculate the
- 1.4.1 current in the circuit. (12)
- 1.4.2 phase angle between the current and the voltage. (3)
- 1.4.3 power factor. (2)
- 1.4.4 active current in the circuit. (3)
- [50]**

QUESTION 2

INSTRUMENTS

- 2.1 Draw a neat, labelled diagram of a power-factor meter and indicate how it is connected in a circuit. (10)
- 2.2 Explain the basic operating principle of a dynamometer type wattmeter. (8)
- 2.3 What type of meter will reflect the true power in a circuit? (1)
- 2.4 Why is an ammeter connected in series to a circuit? (1)
- [20]**

QUESTION 3

THREE-PHASE SYSTEMS

- 3.1 The full-load output of a 600 volt three-phase motor is 12 kW. If the input line current at full load is 20 amperes at a power factor of 0,9, what is the efficiency of the motor? (6)
- 3.2 A 200 kW three-phase, delta-connected motor is connected to a 500 V supply. The power factor is 0,9 and the efficiency is 90%.
- Calculate the
- 3.2.1 line current of the motor. (8)
- 3.2.2 phase current of the motor. (3)

- 3.3 A three-phase delta-connected motor draws 30 A from a 380 V supply at a power factor of 0,9 lagging.

Calculate the

- 3.3.1 input power. (3)
- 3.3.2 apparent power. (3)
- 3.3.3 phase current of the motor winding. (4)
- 3.3.4 full-load efficiency of the motor if the input power is given as 12 kW. (3)
- [30]**

QUESTION 4

TRANSFORMERS

- 4.1 What safety precaution must be taken when an ammeter is removed from the current transformer, and why is it necessary to take this precaution? (3)
- 4.2 State TWO advantages and TWO disadvantages of an auto-transformer. (4)
- 4.3 A three-phase transformer is connected in delta-star to a 22 kV line. The transformer has 6 400 primary windings and takes a full-load line current of 8 amperes on the same side. The secondary line voltage is 380 volts with a lagging power factor of 0,8.
- Calculate the
- 4.3.1 secondary phase voltage. (4)
- 4.3.2 transformation ratio. (4)
- 4.3.3 number of secondary windings. (3)
- 4.3.4 primary phase current. (3)
- 4.3.5 output power of the transformer. (3)
- 4.4 What is the function of a breather in a transformer? (4)
- 4.5 Name TWO tests which can be carried out on a transformer. (2)
- [30]**

**QUESTION 5
ALTERNATING-CURRENT MOTORS**

- 5.1 Draw a neat, labelled diagram of the starting circuit of the slip-ring induction motor. (15)
- 5.2 A four-pole, three-phase induction motor is connected to a 380 volt / 50 hertz supply. The slip of the motor is 5%.
- Calculate the
- 5.2.1 synchronous speed. (4)
- 5.2.2 rotor speed. (4)
- 5.3 Name FOUR examples of safety devices that could be included in the safety circuit of a motor starter. (4)
- 5.4 Draw a neat, labelled diagram of a shaded-pole induction motor. (9)
- 5.5 Which TWO factors determine the efficiency of a machine? (2)
- 5.6 Explain the term **rotor speed**. (2)
- [40]

**QUESTION 6
ELECTRONICS**

- 6.1 Name THREE advantages of semiconductor diodes, when compared with tube diodes. (3)
- 6.2 State TWO practical applications of an oscilloscope. (2)
- 6.3 Draw a neat, labelled circuit diagram of a 220/12 V power supply that makes use of a centre-tapped transformer with a secondary turn. (6)
- 6.4 Draw a labelled sketch of a cathode-ray tube. (9)
- [20]

**QUESTION 7
SAFETY**

- 7.1 State the FIVE basic causes of accidents. (5)
- 7.2 Explain how Aids can be spread from one person to another. (5)
- [10]

TOTAL: 200

FORMULA SHEET

FORMULEBLAD

$$Z = \sqrt{R^2 + (X_L \approx X_C)^2}$$

$$V_R = I_T \times R$$

$$I_T = \frac{V_T}{Z}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_L = I_T \times X_L$$

$$V_C = I_T \times X_C$$

$$I_T = \sqrt{I_R^2 + (I_C \approx I_L)^2}$$

$$I_R = \frac{V_R}{R};$$

$$I_L = \frac{V_L}{X_L};$$

$$I_C = \frac{V_C}{X_C};$$

$$\cos \theta = \frac{I_R}{I_T}$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

$$P = V \times I \times \cos \theta$$

$$\cos \theta = \frac{R}{Z}$$

$$\tan \theta = \frac{X_L - X_C}{R};$$

$$\cos \theta = \frac{P}{VA}$$

$$P = I^2 R$$

$$I_{act} = I \times \cos \theta$$

$$I_{react} = I \times \sin \theta$$

Star/ster

Delta / delta

$$I_L = I_{ph}$$

$$I_L = \sqrt{3} \times I_{ph}$$

$$V_L = \sqrt{3} \times V_{ph}$$

$$V_L = V_{ph}$$

$$F = \frac{pN}{60}$$

$$S = \frac{N_s - N_R}{N_s} \times 100\%$$

$$N_R = \frac{f}{p} (1-s)$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos \theta$$

$$S = \sqrt{3} \times V_L \times I_L;$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p} \text{ or / of } \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Rendement} = \frac{\text{Afvoer}}{\text{Invoer}}$$

END / EINDE