

GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION

ELECTRONICS SG

TIME: 3 hours

MARKS: 200

INSTRUCTIONS:

- Answer ALL the questions.
 - An approved pocket calculator may be used.
 - Answers must be clearly numbered.
 - Keep questions and subsections of a question together.
 - Sketches and diagrams must be large, neat and labelled.
 - A list of formulae, which may be used when applicable, is given on pages 6 to 9 of the question paper.
-

QUESTION 1
ELECTRIC CURRENT THEORY

- 1.1 A capacitor of 40 microfarads, an inductor of 0,1 henry and a resistor of 20 ohms are connected in series. An alternating current supply of 100 Volts / 100 hertz is connected to the circuit.

Calculate the:

- | | | |
|--------|--|-----|
| 1.1.1 | Inductive reactance | (3) |
| 1.1.2 | Capacitive reactance | (3) |
| 1.1.3 | Impedance | (4) |
| 1.1.4 | Current | (3) |
| 1.1.5 | Power factor | (3) |
| 1.1.6 | Phase angle | (3) |
| 1.1.7 | True power | (3) |
| 1.1.8 | Reactive power | (3) |
| 1.1.9 | Apparent power | (3) |
| 1.1.10 | Voltage drop across each component | (9) |
| 1.2 | Determine the Q-factor of the circuit in Question 1.1. | (3) |

[40]

QUESTION 2
THREE-PHASE ALTERNATING-CURRENT SYSTEMS

- 2.1 A three-phase 380 V star-connected motor has an output of 50 kW with a power factor of 0,85 and an efficiency of 90%. Calculate the following:
- 2.1.1 Current drawn at full load (4)
- 2.1.2 Apparent power (3)
- 2.1.3 Phase voltage (3)
- 2.2 Describe, with the aid of a neat, labelled sketch, how full-wave rectification is obtained in a three-phase AC-system. (10)
- [20]**

QUESTION 3
SEMICONDUCTORS

- 3.1 If the base current of a transistor is 20 μA when the emitter current is 6,4 mA, what is the collector current? (3)
- 3.2 Draw a correctly biased NPN transistor in block form.
Clearly indicate the following:
- Depletion region
 - Direction of movement of charge carriers
 - The majority carriers
 - ALL the biasing voltages and the conventional directions (10)
- 3.3 Draw a circuit diagram to demonstrate the operation of a silicon controlled rectifier (SCR). (5)
- [18]**

QUESTION 4
AMPLIFIERS

- 4.1 Draw a circuit diagram of a complete Resistor-capacitor (RC) coupled amplifier. Clearly label all resistors and capacitors on the circuit. (18)
- 4.2 Explain the purpose of the following components used in a transistor amplifier circuit:
- 4.2.1 Coupling capacitor (2)
- 4.2.2 Emitter bypass capacitor (2)
- 4.2.3 Emitter resistor (2)
- 4.3 Sketch a transistor amplifier that makes use of negative feedback. (6)
- [30]**

QUESTION 5
SWITCHING AND CONTROL CIRCUITS


- 5.1 Name the TWO methods by which a regulator circuit can be connected to a load. (2)
- 5.2 Draw an operating circuit of a simple Zener diode regulator. (6)
- 5.3 Draw a block diagram showing the four stages of a power supply circuit. Clearly label each stage. Include a simple circuit symbol in each block. (10)
- 5.4 Draw the voltage wave shape that will appear at each stage in Question 5.3. (10)
- 5.5 In point form, write down the operation of each stage in Question 5.3. (8)
- [36]**

QUESTION 6
OSCILLATORS

- 6.1 Draw a neat, labelled circuit diagram of an inductively coupled oscillator. (12)
- 6.2 Explain briefly the piezo-electrical effect with reference to crystals. (2)
- [14]**

QUESTION 7
COMPUTER PRINCIPLES

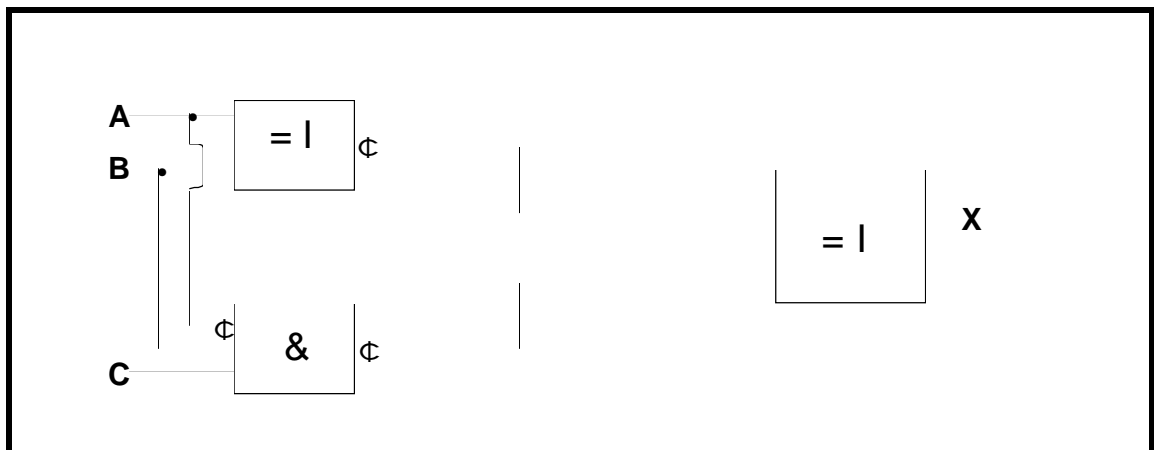- 7.1 Draw the Boolean equation, truth table and the electrical equivalent circuit of the two inputs OR gate. (10)
- 7.2 Prove by means of Boolean algebra that:
 $AB + BC + AC = BC + AC$ (7)
- 7.3 Write the Boolean expression for the following circuit diagram: (4)



[21]

QUESTION 8
ELECTRONIC APPARATUS

- 8.1 Draw a complete block diagram of an oscilloscope showing each main control circuit. (13)
- 8.2 Explain what is meant by: **Calibrate a scale.** (3)
[16]

QUESTION 9
OCCUPATIONAL SAFETY PRECAUTIONS

- 9.1 Name THREE rules applicable to the workshop in which you worked this year. (3)
- 9.2 Explain TWO ways in which Aids can be spread from one person to another. (2)
[5]

TOTAL: 200

INFORMATION SHEET / INLIGTINGSBLAD
ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE

$$I = \frac{V}{R} \text{ AMPS}$$

$$P = V \times I \text{ WATT}$$

$$t = \frac{1}{F} \text{ seconds / sekondes}$$

$$V_{\text{ave. / gem.}} = V_m \times 0,637$$

$$V_{\text{rms. / wgk.}} = V_m \times 0,707$$

STAR / *STER*

$$V_L = \sqrt{3} \times V_p$$

$$I_L = I_p$$

DELTA

$$I_L = \sqrt{3} \times I_p$$

$$V_L = V_p$$

$$X_C = \frac{1}{2 \times \pi \times F \times C}$$

$$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$$

$$X_L = 2 \times p \times F \times L$$

$$f_r = \frac{1}{2 \times p} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$Q = \frac{X_L}{R}$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$Q = \frac{X_C}{R}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_X = V_L - V_C$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_C = I_T \times X_C$$

$$V_L = I_T \times X_L$$

$$V_R = I_T \times R$$

$$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_X = V_C - V_L$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$I_T = \sqrt{I_R^2 + I_X^2}$$

$$Z = \sqrt{R^2 + X_X^2}$$

$$I_X = I_C - I_L$$

$$X_X = X_L - X_C$$

AMPLIFIERS / VERS TERKERS

$$I_e = I_c + I_b$$

$$V_{cc} = V_{Rc} + V_{ce}$$

$$I_c = \frac{V_{cc}}{Rc}$$

DECIBEL RATIOS / DESIBE LVERHOUDINGS

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

OPERATIONAL AMPLIFIERS / OPERASIO NELE VERS TERKERS

$$A_v = - \frac{R_F}{R_1}$$

$$V_{\text{OUT}} = A_v \times V_I$$

$$A_v = 1 + \frac{R_F}{R_1}$$

$$V_{\text{OUT}} = A_v \times V_I$$

$$V_{\text{OUT}} = \frac{1}{RC} \int V_I dt$$

$$V_{\text{OUT}} = - RC \frac{dv}{dt}$$

$$V_{\text{OUT}} = - \left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3} \right)$$

COMPUTER PRINCIPLES / REKE NAARBEGI NSELS

$$A.B = B.A$$

$$A + B = B + A$$

$$A.(B.C) = (A.B).C$$

$$A + (B + C) = (A + B) + C$$

$$A.(B + C) = AB + AC$$

$$A + (B.C) = (A + B) + (A + C)$$

$$A(A + B) = A$$

$$A + (AB) = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A.0 = 0$$

$$A.1 = A$$

$$A + A = A$$

$$A.A = 1$$

$$A.A = A$$

$$A.A = 0$$