

**GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION**

ELECTRONICS SG

FEB / MAR 2006

TIME: 3 hours

MARKS: 200

INSTRUCTIONS:

- Answer ALL the questions.
 - Sketches and diagrams must be large, neat and labelled.
 - All calculations must be shown.
 - Answers must be clearly numbered.
 - An approved pocket calculator may be used.
 - An information sheet may be found on pages 6 to 9.
-
-

**QUESTION 1
ELECTRICAL CURRENT THEORY**

- 1.1 A 240 V/50 Hz supply is connected to a series circuit. The series circuit has a pure resistance of 12 ohm, an inductance of 175 mH and a capacitance of 75 microfarad.

Calculate

- | | | |
|-------|----------------------------------|-----|
| 1.1.1 | the inductive reactance. | (3) |
| 1.1.2 | the capacitive reactance. | (3) |
| 1.1.3 | the impedance of the circuit. | (3) |
| 1.1.4 | the current flow in the circuit. | (3) |
| 1.1.5 | the phase angle. | (3) |
| 1.1.6 | the total power developed. | (3) |

- 1.2 A circuit comprises a non-inductive resistor of 45 ohm, an inductor of 0,3 henry and a capacitor of 150 micro-farad, all connected in parallel across a 250 V/50 Hz supply.

Calculate

- 1.2.1 the current through each component. (15)
1.2.2 the total current. (3)
1.2.3 the dynamic impedance. (3)
1.2.4 the phase angle. (3)
1.2.5 the Q factor. (3)
- 1.3 Draw a phasor diagram (not to scale, but in proportion). (7)
[52]

QUESTION 2 THREE-PHASE ALTERNATING-CURRENT SYSTEMS

- 2.1 Three pure resistances of 50 ohm each are connected in star to a 380 volt three-phase supply.

Calculate

- 2.1.1 the phase voltage. (3)
2.1.2 the phase current. (3)
2.1.3 the line current. (1)
- 2.2 Three pure resistances of 50 ohm each are connected in delta to a 380 volt three-phase supply.
- Calculate
- 2.2.1 the phase voltage. (1)
2.2.2 the phase current. (3)
2.2.3 the line current. (3)
[14]

QUESTION 3 SEMICONDUCTORS

- 3.1 Draw a neat, labelled circuit diagram of a transistor which is connected in the common-base configuration. Input and output waveforms must be shown. State the properties of the transistor when connected in this configuration. (10)
- 3.2 Show by means of a neatly labelled circuit how an SCR is connected to an alternating-current supply. Draw the output wave over the load and over the SCR in good relation to the trigger pulse. (8)
- 3.3 Briefly describe the difference in operation of PNP and NPN transistors. (6)
[24]

**QUESTION 4
AMPLIFIERS**

- 4.1 Draw a neatly labelled diagram of an RC-coupled amplifier. (17)
- 4.2 Sketch a neatly labelled curve of a load line for a common-emitter amplifier. Show all calculations. The following data is given:
- | | | | |
|-----------------|---|--------------|------|
| Load resistance | = | 3 k Ω | |
| Supply voltage | = | 15 volts | (11) |

[28]**QUESTION 5
SWITCHING AND CONTROL CIRCUITS**

- 5.1 Explain with the aid of a neatly labelled circuit diagram and a brief description how the speed of a DC motor can be controlled by using thyristors. (10)
- 5.2 Draw a neatly labelled circuit diagram of a bistable multivibrator. (10)
- 5.3 Explain by means of a diagram and waveforms how a 6 volt peak-to-peak wave is clamped to a positive DC level. (8)

[28]**QUESTION 6
OSCILLATORS**

Explain, with the aid of a neatly labelled circuit diagram, the operating principle of the crystal-controlled oscillator. **[10]**

**QUESTION 7
COMPUTER PRINCIPLES**

- 7.1 Sketch the symbol and indicate the truth table of the OR gate. (7)
- 7.2 Design a NOR-gate network for the following Boolean expression:
- $$X = (A + \overline{B})(C + D) \quad (6)$$
- 7.3 Prove by means of Boolean algebra that:
- $$(X + Y)(X + Z) = X + YZ \quad (6)$$
- 7.4 Design a combination circuit of logic gates to satisfy the following Boolean expression:
- $$X = \overline{AB} + CD.EF \quad (7)$$

- 7.5 Give the Boolean expression for the combination circuit in **Figure 7.5**. Write only the **answer** in your **answer book**. (6)

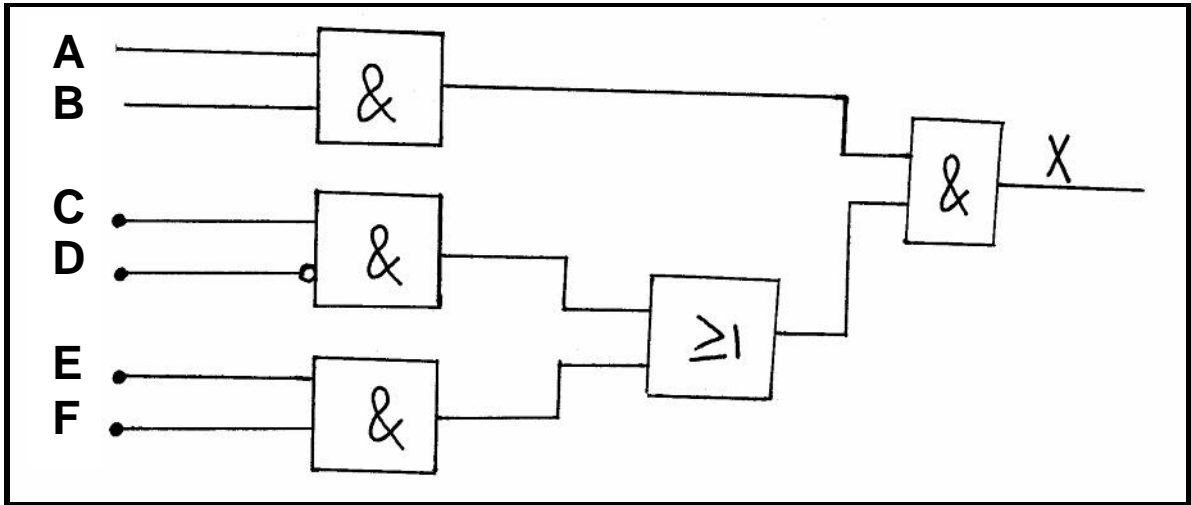


Figure 7.5

[32]

QUESTION 8
ELECTRONIC DEVICES

- Sketch a neatly labelled block diagram of an FM transmitter. [7]

QUESTION 9
SAFETY PRECAUTIONS

- 9.1 Explain what safety precautions you would institute in your workshop to prevent the spread of Aids. (2)
- 9.2 List THREE dangerous actions in the workshop. (3)

[5]

TOTAL: 200

INFORMATION SHEET / INLIGTINGSBLAD	
ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE	

$I = \frac{V}{R} \text{ AMPS}$	
--------------------------------	--

$P = V \times I \text{ WATT}$	
-------------------------------	--

$t = \frac{1}{F} \text{ seconds / sekondes}$	
--	--

$V_{\text{ave./gem.}} = V_m \times 0,637$	
---	--

$V_{\text{rms./wgk.}} = V_m \times 0,707$	
---	--

STAR / <i>STER</i>	
---------------------------	--

$V_L = \sqrt{3} \times V_P$	
-----------------------------	--

$I_L = I_P$	
-------------	--

DELTA	
--------------	--

$I_L = \sqrt{3} \times I_P$	
-----------------------------	--

$V_L = V_P$	
-------------	--

$X_C = \frac{1}{2 \times \pi \times F \times C}$	$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$	
--	---	--

$X_L = 2 \times p \times F \times L$	$f_r = \frac{1}{2 \times p} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$	
--------------------------------------	---	--

$V_T = \sqrt{V_R^2 + V_C^2}$	$Q = \frac{X_L}{R}$	
------------------------------	---------------------	--

$V_T = \sqrt{V_R^2 + V_L^2}$	$Q = \frac{X_C}{R}$	
------------------------------	---------------------	--

$V_T = \sqrt{V_R^2 + V_X^2}$	$Q = \frac{1}{R} \sqrt{L}$	
------------------------------	----------------------------	--

$V_X = V_L - V_C$	$\frac{V_1}{N_2} = \frac{N_1}{I_2} = \frac{I_1}{I_2}$	
-------------------	---	--

$V_C = I_T \times X_C$		
------------------------	--	--

$V_L = I_T \times X_L$	$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$	
------------------------	--	--

$V_R = I_T \times R$		
----------------------	--	--

MEASURING INSTRUMENTS / MEE TINSTRUMENTE

$V_T = \sqrt{V_R^2 + V_X^2}$	$Z = \sqrt{R^2 + X_C^2}$	
------------------------------	--------------------------	--

$V_X = V_C - V_L$	$Z = \sqrt{R^2 + X_L^2}$	
-------------------	--------------------------	--

$I_T = \sqrt{I_R^2 + I_X^2}$	$Z = \sqrt{R^2 + X_X^2}$	
------------------------------	--------------------------	--

$I_X = I_C - I_L$	$X_X = X_L - X_C$	
-------------------	-------------------	--

AMPLIFIERS / VERS TERKERS

$I_e = I_c + I_b$		
-------------------	--	--

$V_{cc} = V_{Rc} + V_{ce}$		
----------------------------	--	--

$I_c = \frac{V_{cc}}{Rc}$		
---------------------------	--	--

DECIBEL RATIOS / DESIBE LVERHOUDINGS

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

OPERATIONAL AMPLIFIERS / OPERASIO NELE VERS TERKERS

$$A_V = - \frac{R_F}{R_1}$$

$$V_{\text{OUT}} = A_V \times V_I$$

$$A_V = 1 + \frac{R_F}{R_1}$$

$$V_{\text{OUT}} = A_V \times V_I$$

$$V_{\text{OUT}} = \frac{1}{RC} \int V_I dt$$

$$V_{\text{OUT}} = - RC \frac{dv}{dt}$$

$$V_{\text{OUT}} = - \left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3} \right)$$

COMPUTER PRINCIPLES / REKE NAARBEGI NSELS

$$A.B = B.A$$
$$A + B = B + A$$

$$A.(B.C) = (A.B).C$$
$$A + (B + C) = (A + B) + C$$

$$A.(B + C) = AB + AC$$
$$A + (B.C) = (A + B) + (A + C)$$

$$A(A + B) = A$$
$$A + (AB) = A$$

$$A + 0 = A$$
$$A + 1 = 1$$
$$A.0 = 0$$
$$A.1 = A$$
$$A + \underline{A} = A$$
$$A + \overline{A} = 1$$
$$A.\underline{A} = A$$
$$A.\overline{A} = 0$$

INFORMATION SHEET / INLIGTINGSBLAD ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE	
---	--

$I = \frac{V}{R} \text{ AMPS}$	
--------------------------------	--

$P = V \times I \text{ WATT}$	
-------------------------------	--

$t = \frac{1}{F} \text{ seconds / sekondes}$	
--	--

$V_{\text{ave./gem.}} = V_m \times 0,637$	
---	--

$V_{\text{rms./wgk.}} = V_m \times 0,707$	
---	--

STAR / <i>STER</i>	
---------------------------	--

$V_L = \sqrt{3} \times V_P$	
-----------------------------	--

$I_L = I_P$	
-------------	--

DELTA	
--------------	--

$I_L = \sqrt{3} \times I_P$	
-----------------------------	--

$V_L = V_P$	
-------------	--

$X_C = \frac{1}{2 \times \pi \times F \times C}$	$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$	
--	---	--

$X_L = 2 \times p \times F \times L$	$f_r = \frac{1}{2 \times p} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$	
--------------------------------------	---	--

$V_T = \sqrt{V_R^2 + V_C^2}$	$Q = \frac{X_L}{R}$	
------------------------------	---------------------	--

$V_T = \sqrt{V_R^2 + V_L^2}$	$Q = \frac{X_C}{R}$	
------------------------------	---------------------	--

$V_T = \sqrt{V_R^2 + V_X^2}$	$Q = \frac{1}{R} \sqrt{L}$	
------------------------------	----------------------------	--

$V_X = V_L - V_C$	$\frac{V_1}{N_2} = \frac{N_1}{I_1} = \frac{I_2}{I_1}$
-------------------	---

$V_C = I_T \times X_C$	
------------------------	--

$V_L = I_T \times X_L$	$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$
------------------------	--

$V_R = I_T \times R$	
----------------------	--

MEASURING INSTRUMENTS / MEE TINSTRUMENTE

$V_T = \sqrt{V_R^2 + V_X^2}$	$Z = \sqrt{R^2 + X_C^2}$	
------------------------------	--------------------------	--

$V_X = V_C - V_L$	$Z = \sqrt{R^2 + X_L^2}$	
-------------------	--------------------------	--

$I_T = \sqrt{I_R^2 + I_X^2}$	$Z = \sqrt{R^2 + X_X^2}$	
------------------------------	--------------------------	--

$I_X = I_C - I_L$	$X_X = X_L - X_C$	
-------------------	-------------------	--

AMPLIFIERS / VERS TERKERS

$I_e = I_c + I_b$	
-------------------	--

$V_{cc} = V_{Rc} + V_{ce}$	
----------------------------	--

$I_c = \frac{V_{cc}}{Rc}$	
---------------------------	--

DECIBEL RATIOS / DESIBE LVERHOUDINGS

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

OPERATIONAL AMPLIFIERS / OPERASIO NELE VERS TERKERS

$$A_V = - \frac{R_F}{R_1}$$

$$V_{OUT} = A_V \times V_I$$

$$A_V = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = A_V \times V_I$$

$$V_{OUT} = \frac{1}{RC} \int V_I dt$$

$$V_{OUT} = - RC \frac{dv}{dt}$$

$$V_{OUT} = - (V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3})$$

COMPUTER PRINCIPLES / REKE NAARBEGI NSELS

$$A \cdot B = B \cdot A$$
$$A + B = B + A$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$
$$A + (B + C) = (A + B) + C$$

$$A \cdot (B + C) = AB + AC$$
$$A + (B \cdot C) = (A + B) + (A + C)$$

$$A(A + B) = A$$
$$A + (AB) = A$$

$$A + 0 = A$$
$$A + 1 = 1$$
$$A \cdot 0 = 0$$
$$A \cdot 1 = A$$
$$A + \bar{A} = 1$$
$$A + A = 1$$
$$A \cdot \bar{A} = 0$$
$$A \cdot A = A$$