

GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION

FEB / MAR 2006

TECHNIKA (ELECTRICAL) HG

TIME: 3 hours

MARKS: 300

REQUIREMENTS:

- Drawing instruments and an approved calculator

INSTRUCTIONS:

- Answer ALL the questions.
 - All the work including sketches and diagrams must be neat and legible.
 - Formulae and calculations must, where applicable, be indicated.
 - A list of formulae, which may be used where applicable, is provided on the last page of the question paper.
-
-

QUESTION 1
ELECTRICAL CURRENT THEORY

- 1.1 Name ONE method of improving a low inductive power factor. (2)
- 1.2 Explain what is meant by **resonant frequency** by referring to series circuits. (3)
- 1.3 Define the following terms regarding alternating voltage:
- 1.3.1 Frequency (2)
- 1.3.2 Period (2)
- 1.4 What determines the value of the current in a resonant series circuit? (2)
- 1.5 A coil with a resistance of 10 ohms, an inductance of 200 millihenrys and a capacitor of 100 microfarads is connected in series to a 250 V 50 Hz supply.
- Calculate the following:
- 1.5.1 Impedance of the circuit (9)
- 1.5.2 Power factor of the circuit (2)
- 1.5.3 Reactive component of the current (7)

- 1.6 The resistance component of a parallel resonant R, L and C circuit is 5 ohms. The circuit resonates at a frequency of 550 kHz if the capacitor is set at a capacitance of 500 pico-farads.

Calculate the following:

- 1.6.1 The Q factor of the circuit (5)
- 1.6.2 The current circulating between the coil and the capacitor if the supply current to the circuit is 50 micro-amperes. (4)
- 1.7 When a certain coil is connected to a 50 volt direct current supply, a current of 5 amperes is drawn and when the same coil is connected over a 140 volt - 60 Hz alternating current supply it draws a current of 7 amperes.

Calculate the following:

- 1.7.1 The value of the resistance of the coil (3)
- 1.7.2 The inductance of the coil (9)
- [50]**

QUESTION 2

SINGLE AND THREE-PHASE ALTERNATING-CURRENT SYSTEMS

- 2.1 Name the advantages of a three-phase alternating-current system over a single-phase alternating-current system. (3)
- 2.2 Explain what is meant by **apparent power**. (2)
- 2.3 Why is electricity, distributed by means of transmission lines at high voltage for example, 80 kilovolts? (2)
- 2.4 In a certain balanced, star-connected three-phase circuit with an inductive load, the line-to-line voltmeter reading is 380 volts, the ammeter reading 10 amps and the wattmeter reading 3 kilowatt.

Calculate the following:

- 2.4.1 The phase voltage (3)
- 2.4.2 The phase current (3)
- 2.4.3 The power factor of the load (3)
- 2.4.4 The phase impedance (3)
- 2.4.5 The phase resistance (3)

2.5 A single-phase installation is connected to a 500 V 50 Hz supply. The current in the circuit is 100 amperes and the power factor is 0,7 lagging.

Calculate the

- 2.5.1 active component of the current. (3)
 - 2.5.2 apparent power. (3)
 - 2.5.3 reactive component of power. (4)
 - 2.5.4 active component of power. (3)
- [35]**

QUESTION 3 TRANSFORMERS

- 3.1 Fully explain why the secondary windings of a current transformer may never be left open-circuited. (6)
- 3.2 Which TWO methods are generally used to cool transformers? (2)
- 3.3 Name ONE advantage of an auto transformer over that of a double-wound transformer. (2)
- 3.4 A star-connected three-phase alternator with a phase voltage of 6,6 kV is connected to a three-phase delta star transformer with a turns ratio of 50:1.

Calculate the

- 3.4.1 line voltage of the alternator. (3)
 - 3.4.2 primary line voltage of the transformer. (3)
 - 3.4.3 primary phase voltage of the transformer. (3)
 - 3.4.4 secondary phase voltage of the transformer. (3)
 - 3.4.5 secondary line voltage of the transformer. (3)
- [25]**

QUESTION 4
ALTERNATING CURRENT MOTORS

- 4.1 Name THREE factors that influence the speed of a squirrel-cage motor. (3)
- 4.2 Briefly describe TWO methods that are used in starters to limit the starting current of three-phase squirrel-cage motors. (4)
- 4.3 Describe fully the consequences of not including a NO-volt coil in a motor starter. (3)
- 4.4 Name the correct phase sequence for three-phase systems. (2)
- 4.5 A four-pole squirrel-cage induction motor is connected to a 380 V alternating current supply with a periodic time of 0,02 seconds. The motor slip is calculated to be 4%.
- Calculate the
- 4.5.1 supply frequency. (2)
- 4.5.2 rotor speed. (4)
- 4.6 A single-phase motor draws a current of 15 amperes with a power factor of 0,85 from a 380 volt supply.
- Calculate the
- 4.6.1 power of the motor. (3)
- 4.6.2 active component of the current. (3)
- 4.6.3 reactive component of the current. (4)
- [28]**

QUESTION 5
SEMICONDUCTORS

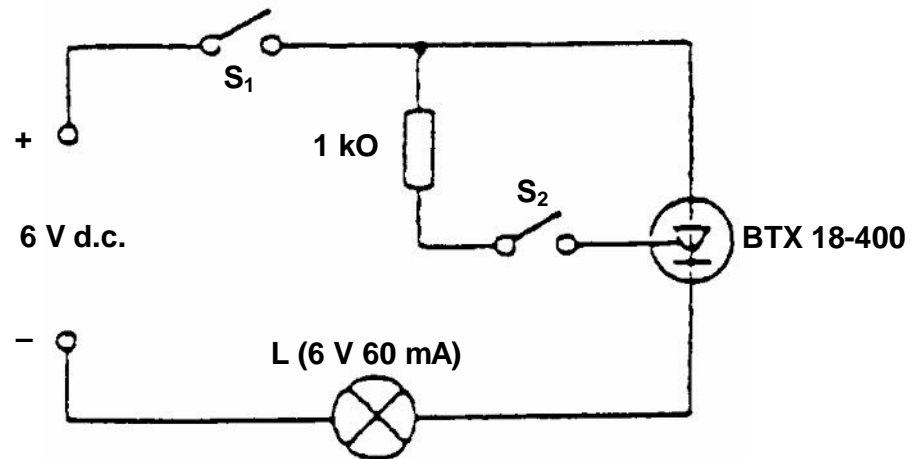


Figure 1

- 5.1 From the above circuit diagram explain, with reasons, what happens to the lamp when the following switching sequence takes place:
- 5.1.1 S₁ is closed, S₂ remains open, then (3)
 - 5.1.2 S₁ remains closed and S₂ is closed, then (3)
 - 5.1.3 S₁ remains closed and S₂ is opened. (3)
- 5.2 Draw the symbol and label the following electronic components:
- 5.2.1 PNP-Transistor (2)
 - 5.2.2 Triac (2)
- 5.3 Under which basic conditions can an PNP-transistor be switched on? Draw a diagram to prove your answer. (4)
- 5.4 Name TWO important forward-biased conditions for an SCR to function adequately. (4)
- 5.5 What is the difference between a **triac** and an **SCR**? (2)

[23]

**QUESTION 6
AMPLIFIERS**

6.1 Study the following circuit and answer the questions that follow.

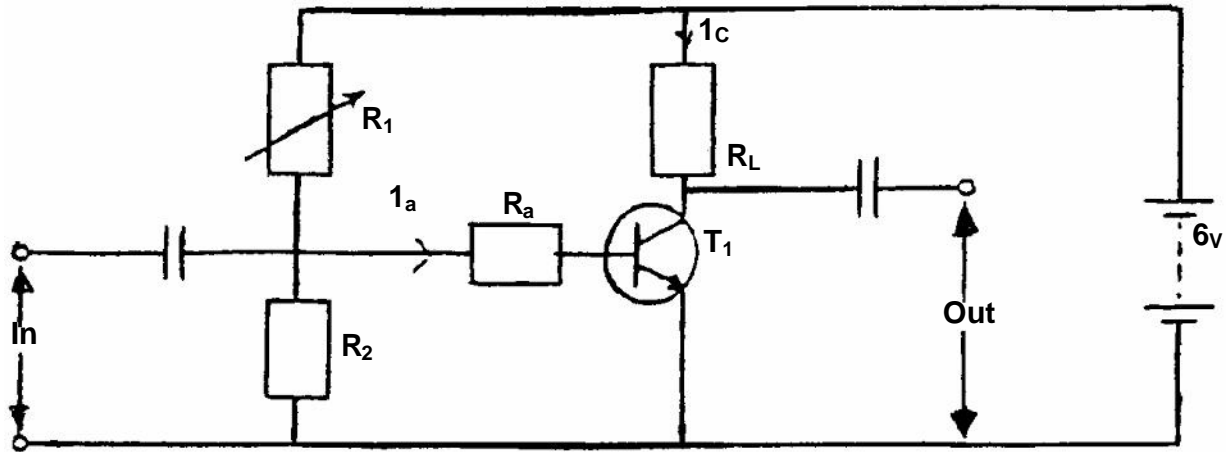


Figure 2

- 6.1.1 What is the voltage across
- (a) R_L and (2)
 - (b) T_1 when the transistor is off? (2)
- 6.1.2 (a) R_L and (2)
- (b) T_1 when the transistor is switched on fully? (2)
- 6.2 Name ONE advantage of negative feedback as applied to amplifiers. (2)
- 6.3 Sketch labelled frequency characteristic curves of a mutually coupled amplifier and a RC coupled amplifier in order to make a comparison between the two. (4)
- 6.4 Draw a diagram of a Darlington-pair amplifier with two NPN transistors. (4)

[18]

**QUESTION 7
SWITCHING AND CONTROL CIRCUITS**

- 7.1 Explain the term **regulated power supply**. (2)
- 7.2 With the aid of a diagram, explain the operation of a transistor series regulator when the input voltage shows a sudden increase. (10)
- 7.3 Explain, with the aid of a circuit diagram, how lamp dimming can be obtained in an AC circuit through the use of a triac. (6)
- [18]**

**QUESTION 8
OSCILLATORS**

- 8.1 What is the function of the crystal in the crystal-controlled Hartley oscillator circuit? (2)
- 8.2 What is **piëzo-electricity**? (2)
- 8.3

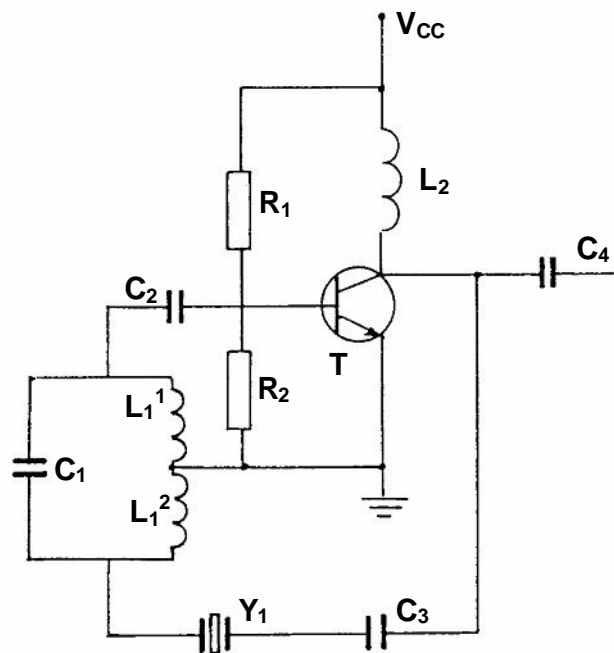


Figure 3

- 8.3.1 Identify the above circuit. (2)
- 8.3.2 Describe the function of R_1 and R_2 in the circuit. (4)
- 8.3.3 Identify the components which form the tank circuit. (2)
- 8.3.4 Identify Y_1 . (2)
- 8.3.5 Describe how the value of Y_1 is selected. (2)

[16]

b.o.

**QUESTION 9
OPERATIONAL AMPLIFIERS**

- 9.1 Sketch a diagram of a comparator circuit using an operational amplifier. Sketch typical output wave forms if the input is sinusoidal. (6)
- 9.2 Show, with the aid of a diagram, how an operational amplifier can be connected to operate as an a-stable multivibrator. (6)
- [12]**

**QUESTION 10
COMPUTER PRINCIPLES**

- 10.1 Prove with the aid of truth tables that
- $$A + B = A \cdot B \quad (6)$$
- 10.2 Simplify the following Boolean equation:
- $$X = (A \cdot B \cdot C) + (A \cdot B) \quad (5)$$
- 10.3 Sketch a block diagram of a full adder by using two half adders and an OR gate. Give the Boolean equation after each component. (8)
- 10.4 Draw a logic circuit of a clocked RS latch using NAND gates. (7)
- 10.5 The Technika (Electrical) educator is asked to design a lock for the school's pedestrian gate. This gate must only open under the following conditions:
- It must be daylight (morning) $A = 1$
 - and at least ONE of the following people must be present:
- B = 1 The headmaster of the school
 C = 1 The deputy headmaster
 D = 1 One of the heads of department
- 10.5.1 Draw a truth table to show all the possibilities. (6)
- 10.5.2 Give the Boolean equation from the truth table that will allow access to the school. (3)
- 10.5.3 Draw the logic circuit of this system. (5)
- [40]**

**QUESTION 11
MEASURING INSTRUMENTS**

11.1 Label the following block diagram of a capacitance measuring instrument. Write the letters **A** to **E** in your answer book and the appropriate label next to each.

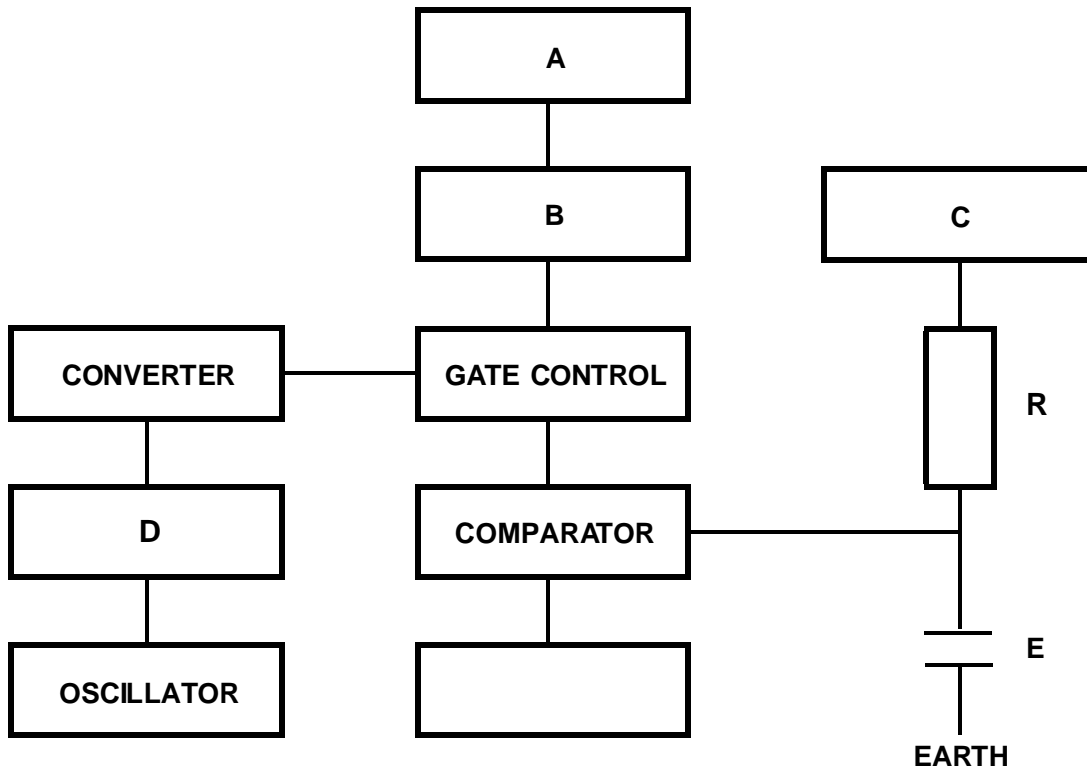


Figure 4

(5)

11.2 Draw a labelled circuit diagram to show how one wattmeter can be connected to measure the power in a balanced, star-connected load.

(6)

11.3 Name TWO uses of an ossilloscope.

(2)

[13]

**QUESTION 12
OCCUPATIONAL SAFETY**

- 12.1 Who is responsible for the prevention of occupational accidents? (2)
- 12.2 Your friend's hand is cut in the work centre. Describe what you will do to stop the bleeding, keeping the HI-virus in mind. (6)
[8]

**QUESTION 13
PRACTICAL**

- 13.1 Design a power supply that transforms 220 V alternating current to a stable 12 V direct current so that it can be used as a battery charger. Sketch the circuit diagram and show the following components. (N.B. Not a block diagram)
- Transformer
 - Main switch
 - Fuse
 - Diode Bridge
 - Filter Capacitor
 - Zener diode
- (10)
- 13.2 Show, by means of a sketch, how a diode can be tested with a multimeter. (4)
[14]

TOTAL: 300

FORMULES / FORMULAE

$$X_L = 2 \pi L F$$

$$X_C = \frac{1}{2 \pi F C}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$F_R = \frac{1}{2 \pi \sqrt{L C}}$$

$$F_R = \frac{1}{2 \pi} \sqrt{\frac{1}{L C} - \frac{R^2}{L^2}}$$

$$I_C = V \cdot \sqrt{\frac{C}{L}}$$

$$f = \frac{W}{2 \pi}$$

$$t = R \cdot C$$

Ster/Star

$$V_L = V_P \cdot \sqrt{3}$$

$$I_L = I_P$$

$$I_r = I \sin \Theta$$

$$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \Theta$$

$$\cos \Theta = \frac{P}{P_{\text{Skynbaar/Apparent}}}$$

$$\text{Rendement/Efficiency} = \frac{\text{Uitset/Output}}{\text{Inset/Input}}$$

$$N_s = \frac{f}{P}$$

$$\frac{N_P}{N_S} = \sqrt{\frac{Z_P}{Z_S}}$$

$$\beta = \frac{I_C}{I_B}$$

$$V_R = I R$$

$$V_L = L X_L$$

$$V_C = L X_C$$

$$Q = \frac{X_L}{R}$$

$$\cos \Theta = \frac{R}{Z}$$

$$f = \frac{1}{T}$$

$$I = \frac{V}{Z}$$

$$Z = \frac{L}{C \cdot R}$$

Delta

$$I_L = I_P \cdot \sqrt{3}$$

$$V_L = V_P$$

$$I_a = I \cos \Theta$$

$$\frac{N_P}{N_S} = \frac{V_P}{V_S} = \frac{I_S}{I_P}$$

$$N_r = N_s - S$$

$$S = \frac{N_s - N_r}{N_s}$$

$$I_E = I_B + I_C$$

$$I = \frac{V_{cc}}{R_L}$$

$$N = 10 \log \frac{P_2}{P_1}$$

$$Z = \frac{V}{I}$$

$$P = I \times V \times \cos \theta$$

$$I_{wgk} = I_{maks} \times 0,707$$

$$Q = \cos^{-1} \frac{V_R}{V_T}$$

$$P = I \times V$$

$$V_t^2 = V_R^2 + V_L^2$$

$$kVA = I \times V$$

$$N_s = \frac{f}{p}$$

END