

GAUTENG DEPARTMENT OF EDUCATION  
SENIOR CERTIFICATE EXAMINATION

TECHNIKA (ELECTRICAL) SG

TIME: 3 hours

MARKS: 200

---

---

**REQUIREMENTS:**

- An approved calculator and drawing instruments.

**INSTRUCTIONS:**

- Answer ALL the questions.
  - Sketches and diagrams should be neat and clear.
  - Formulae and calculations must be clear.
  - Formulae and calculations must be shown, where applicable.
  - A list of formulae, which must be used where applicable, is given on the last page of this examination paper.
- 
- 

**QUESTION 1**  
**ELECTRICAL CURRENT THEORY**

1.1 A circuit consists of a coil with a resistance of 40 Ohms and an inductance of 0,14 H, connected in series with a capacitor of 49 micro-Farads, across a source of 220 V, 60 Hz. Calculate the

- |       |  |     |
|-------|--|-----|
| 1.1.1 | impedance of the circuit.                                    | (9) |
| 1.1.2 | total current flow.  | (3) |
| 1.1.3 | phase angle of the current, relative to the applied voltage. | (4) |
| 1.1.4 | voltage drop across the coil.                                | (6) |

- 1.2 Calculate the Q factor of a series resonant RLC circuit, where  $R = 42 \Omega$  and  $L = 120 \mu\text{H}$ , with a supply frequency of 325 kHz. (6)

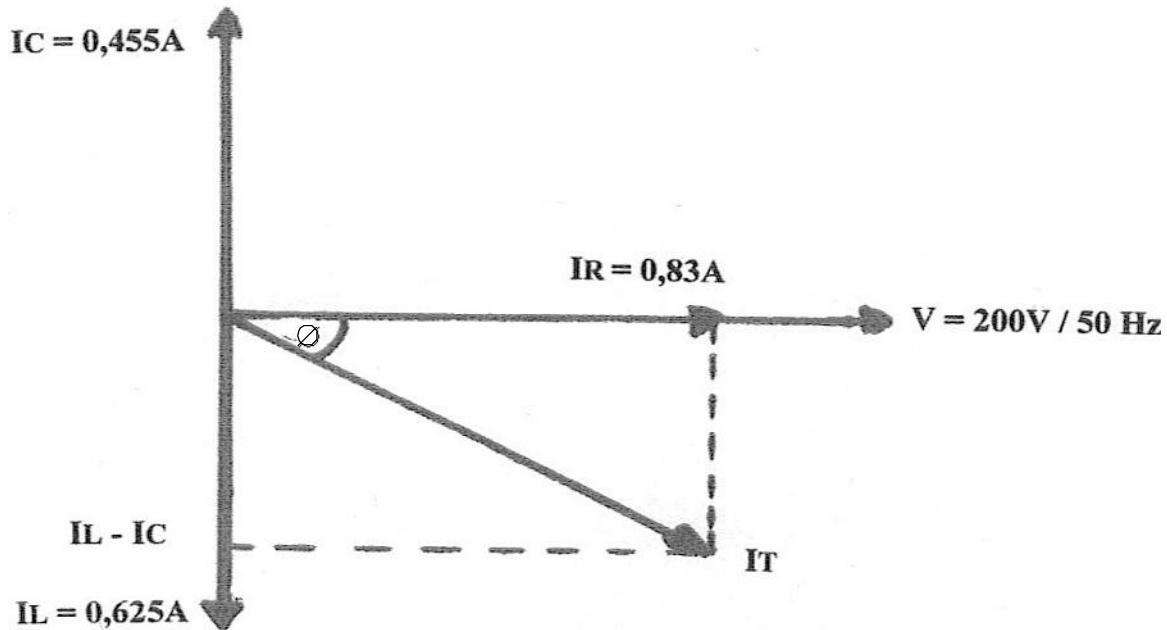


Figure 1.1

- 1.3 From the phasor diagram in **Figure 1.1** calculate:
- 1.3.1 The total current flow (3)
  - 1.3.2 The phase angle (4)
  - 1.3.3 The inductance of the coil in the circuit (6)
- 1.4 What effect will an increase in frequency have on the current flowing through an inductor in a parallel RLC circuit, with reference to the impedance of the circuit? (2)
- 1.5 In a parallel RLC circuit, when will the total current flow be equal to the current through the resistor? (2)
- [45]**

## QUESTION 2 SINGLE AND THREE-PHASE SYSTEMS

- 2.1 The meter readings in a certain single-phase system are:  
 $V = 250 \text{ V}$ ,  $I = 20 \text{ A}$  and power factor = 0,8 leading.
- 2.1.1 Calculate the apparent power of the circuit. (3)
  - 2.1.2 Calculate the effective power of the circuit. (3)
  - 2.1.3 Calculate the phase angle between the current and the voltage. (2)

- 2.2 State ONE advantage of a three-phase alternating current system when compared to that of a single-phase alternating current system. (2)  
[10]

### QUESTION 3 TRANSFORMERS

- 3.1 What is the purpose of silica gel in the breather of a transformer? (2)
- 3.2 Large transformers are used for the distribution of power. The transformers are immersed in a specific oil. Give ONE reason for the use of this specific oil in transformers. (2)
- 3.3 A three-phase alternator supplies a three-phase delta-star connected transformer with power. The alternator's line voltage and current is 11 kV and 5A. The transformer has 5000 primary windings. The secondary line voltage is 500 Volts with a lagging power factor of 0,6. Calculate the
- 3.3.1 secondary phase voltage. (2)
  - 3.3.2 transformation ratio. (3)
  - 3.3.3 number of secondary windings. (3)
  - 3.3.4 primary phase current. (2)
  - 3.3.5 secondary phase current. (3)
  - 3.3.6 output power. (3)
- [20]

### QUESTION 4 ALTERNATING CURRENT MOTORS

- 4.1 Briefly explain the difference between the synchronous speed and the rotor speed of an alternating current motor. (2)
- 4.2 The supply to a 50 kW three-phase motor is 380 Volts. Calculate the current that the motor will take from the line, if the efficiency of the motor is 80% at a power factor of 0,85. (6)
- 4.3 State TWO possible causes of overheating of an electric motor on load. (2)
- 4.4 Determine the slip, in percentage, of a four-pole three-phase induction motor. The supply to the motor is 500 Volts, 50 Hertz with a rotor speed of 1425 r/min. (6)
- 4.5 Draw a neat, labelled circuit diagram of a capacitor-starter motor. (4)
- 4.6 Give ONE use of the shaded-pole motor. (2)
- 4.7 What is the purpose of the second capacitor in the capacitor start-and-run motor? (3)  
[25]

**QUESTION 5  
SEMICONDUCTORS**

- 5.1 Draw the symbols of the following components:
- 5.1.1 NPN transistor (2)
  - 5.1.2 Diac (2)
- 5.2 Under which biasing conditions will a bipolar transistor (NPN) function correctly? (4)
- 5.3 Name ONE difference between a Zener diode and a junction diode. (2)
- [10]**

**QUESTION 6  
AMPLIFIERS**

- 6.1 Draw a neat, labelled circuit diagram of a push-pull amplifier. (8)
- 6.2 Which class of amplification is used in this push-pull amplifier? (2)
- 6.3 With the aid of a circuit diagram, explain how a single transistor can be used to amplify a sine wave. Show the input and output wave forms. (8)
- 6.4 State TWO disadvantages of a transformer-coupled amplifier. (2)
- [20]**

**QUESTION 7  
SWITCHING AND CONTROL CIRCUITS**

- 7.1 What does the term **regulated power supply** mean? (2)
- 7.2 Explain, with the aid of a labelled circuit diagram, how an SCR (Silicon Controlled Rectifier) can be used to control the speed of an electric motor. (10)
- 7.3 Name TWO safety precautions that should be kept in mind when working with power supplies. (2)
- 7.4 Name ONE method used to switch off an SCR. (2)
- 7.5 Draw a simple circuit of a Zener regulated power supply. (4)
- [20]**

**QUESTION 8  
OPERATIONAL AMPLIFIERS**

- 8.1 Sketch a neat, labelled circuit diagram of a differentiator circuit which makes use of an operational amplifier. Illustrate all relevant wave forms. **[10]**

**QUESTION 9  
OSCILLATORS**

- 9.1 Describe the following terms as applied to oscillators:
- 9.1.1 Positive feedback (2)
  - 9.1.2 Tank circuit (2)
  - 9.1.3 Piezo-electricity (2)
- 9.2 Explain the purpose of the crystal in a Hartley crystal-controlled oscillator. (2)
- 9.3 What is the purpose of an oscillator circuit in a capacitance meter? (2)
- [10]**

**QUESTION 10  
COMPUTER PRINCIPLES**

- 10.1 A learner is approached to design a circuit consisting of three switches, A, B and C, which will allow the current to flow under the following conditions:
- Switches A and C open and B closed
  - Switches B and C open and A closed
  - Switches A and C closed and B open
  - All three switches closed
- 10.1.1 Draw up a truth table for the circuit. (8)
- 10.1.2 Derive a logical expression for the circuit. (4)
- 10.2 Prove with the aid of truth tables that:
- $$A + B = A.B \quad (6)$$
- 10.3 Draw the symbol of a NAND gate. (2)
- [20]**

TECHNIKA (ELECTRICAL) SG	713-2/0 U	7
--------------------------	-----------	---

**QUESTION 11**  
**MEASURING INSTRUMENTS**

- 11.1 Draw a neat, labelled sketch of a power-factor meter. (6)
- 11.2 Name TWO uses of the oscilloscope. (2)
- 11.3 Give ONE method used to obtain deflection in a cathode ray tube. (2)
- [10]**

**TOTAL: 200**

## FORMULA SHEET/ FORMULELYS

$$X_L = 2 \pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$F_R = \frac{1}{2\pi \sqrt{LC}}$$

$$f = \frac{\omega}{2\pi}$$

$$t = R.C$$

Star/Ster

$$V_L = V_P \cdot \sqrt{3}$$

$$I_L = I_P$$

Delta

$$V_L = V_P$$

$$I_L = I_P \cdot \sqrt{3}$$

$$I_r = I \sin \theta$$

$$I_a = I \cos \theta$$

$$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \theta$$

$$\cos \theta = \frac{P}{P_{\text{apparaat / skynbaar}}}$$

$$\text{Efficiency / Rendement} = \frac{\text{Output / Uitset}}{\text{Input / Inset}}$$

$$N_s = \frac{f}{P}$$

$$\cos \theta = \frac{R}{Z}$$

$$Z = \frac{V}{I}$$

$$Z = \frac{L}{CR}$$

$$F_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$Q = \frac{X_L}{R}$$

$$f = \frac{1}{T}$$

$$VR = I.R$$

$$V_L = I.X_L$$

$$V_C = I.X_C$$

$$\frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{I_s}{I_p}$$

$$t = R.C$$

$$I_E = I_B + I_C$$

$$I_C = \frac{V_{CE}}{R_L}$$

$$S = \frac{N_s - N_r}{N_s}$$

$$\beta = \frac{I_C}{I_B}$$