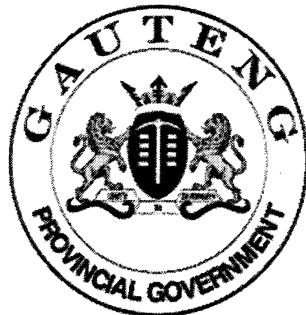


**SENIOR CERTIFICATE EXAMINATION**  
***SENIORSERTIFIKAAT-EKSAMEN***



**OCTOBER / NOVEMBER**  
***OKTOBER / NOVEMBER***

**2004**

**TECHNIKA (ELECTRONICS)**

***TECHNIKA (ELEKTRONIES)***

**SG**

**714-2/0**

**9 pages**  
**9 bladsye**

TECHNIKA ELECTRONICS SG



**COPYRIGHT RESERVED / KOPIEREG VOORBEHOU**  
**APPROVED BY UMALUSI / GOEDGEKEUR DEUR UMALUSI**



GAUTENGSE DEPARTEMENT VAN ONDERWYS  
SENIORSERTIFIKAAT-EKSAMEN

TECHNIKA (ELEKTRONIES) SG

TYD: 3 uur

PUNTE: 200

**INSTRUKSIES:**

- Beantwoord AL die vrae.
- Sketse en diagramme moet groot, netjies en benoem wees.
- Alle berekeninge moet getoon word.
- 'n Goedgekeurde sakrekenaar mag gebruik word.
- Antwoorde moet korrek genommer wees.
- 'n Formuleblad (bladsye 7-9) is aan die einde van die vraestel ingesluit.


**VRAAG 1  
ELEKTRIESE STROOMTEORIE**

1.1 **Figuur 1** is 'n tipiese RLC-kring met meters. Aanvaar dat die skakelaar gesluit is.

1.1.1 Bepaal die volgende:

- |     |                                |     |
|-----|--------------------------------|-----|
| (a) | Die stroomvloei in die kring   | (9) |
| (b) | Die spanning oor die spoel     | (3) |
| (c) | Die spanning oor die kapasitor | (3) |
| (d) | Die spanning oor die weerstand | (3) |
| (e) | Die fasehoek                   | (5) |
| (f) | $\cos \theta$                  | (3) |

1.1.2 Teken 'n volledig benoemde fasordiagram wat al die spannings en die fasehoek in die kring aantoon. (7)

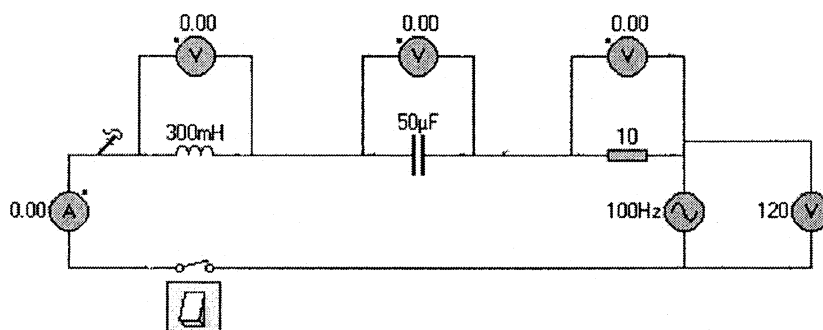

**Figuur 1  
RLC-kring**

GAUTENG DEPARTMENT OF EDUCATION  
SENIOR CERTIFICATE EXAMINATION

TECHNIKA (ELECTRONICS) SG

TIME: 3 hours

MARKS: 200

**INSTRUCTIONS:**

- Answer ALL the questions.
- Sketches and diagrams must be large, neat and labelled.
- All calculations must be shown.
- An approved pocket calculator may be used.
- Answers must be clearly numbered.
- Formulae sheets (pages 7-9) are enclosed at the end of the paper.


**QUESTION 1**  
**ELECTRIC CURRENT THEORY**

1.1 **Figure 1** is a typical RLC circuit with meters. Assume that the switch is closed.

1.1.1 Determine the following:

- |     |                                 |     |
|-----|---------------------------------|-----|
| (a) | The current in the circuit      | (9) |
| (b) | The voltage over the coil       | (3) |
| (c) | The voltage over the capacitor  | (3) |
| (d) | The voltage over the resistance | (3) |
| (e) | The phase angle                 | (5) |
| (f) | Cos $\theta$                    | (3) |

1.1.2 Sketch a fully labelled phasor diagram, showing all the voltages and the phase angle in the circuit. (7)

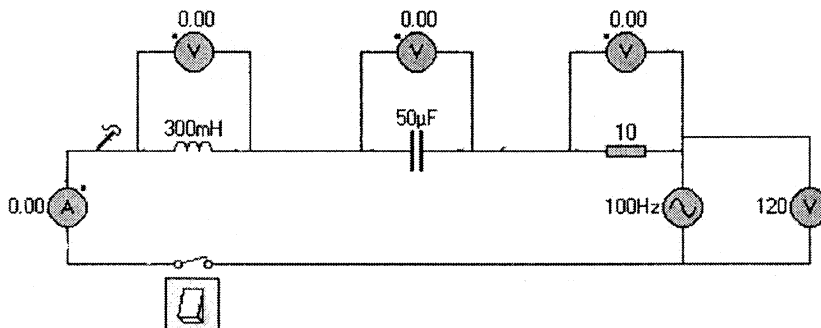


**Figure 1**  
**RLC Circuit**

- 1.2 Verduidelik kortliks hoe die waarde van die kapasitiewe reaktansie verander kan word. (4)
- 1.3 Teken 'n grafiek (nie volgens skaal nie) van die  $X_C$  en  $X_L$ -waardes om aan te toon wanneer die resonante frekwensie verkry word. (5)

[42]

## VRAAG 2 HALFGELEIER-TOESTELLE

- 2.1 Identifiseer die volgende elektroniese komponente met verwysing na die elektroniese kringdiagram in **Figuur 2**. Byvoorbeeld:  $R_{10}$  is 'n 680 000-ohm-resistor.

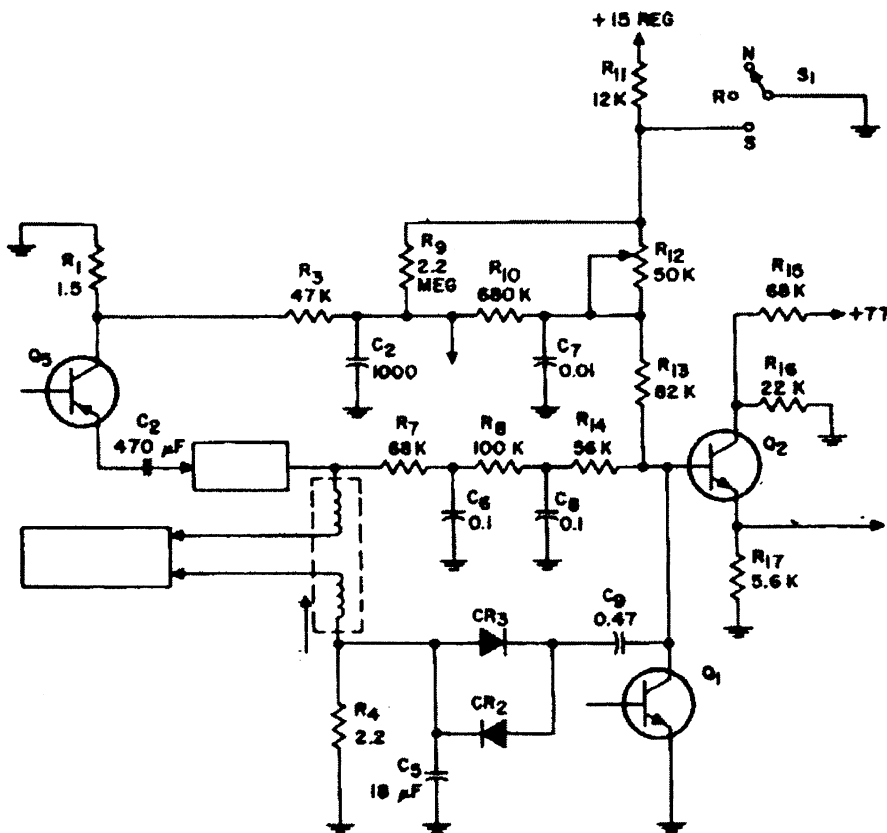

**Figuur 2**  
Vertikale voorversterker met insette

- 2.1.1  $R_{13}$  (3)
- 2.1.2  $Q_5$  (2)
- 2.1.3  $C_6$  (2)
- 2.1.4  $CR_2$  (2)
- 2.1.5  $Q_1$  (2)
- 2.2 Verduidelik kortliks hoe jy 'n diode sal toets met 'n analog-multimeter. (Teken die nodige diagramme.) (10)


1.2 Explain briefly how you will change the value of the capacitive reactance. (4)

1.3 Draw a graph (not to scale) of the  $X_L$  and  $X_C$  values showing at which point the resonant frequency will be active. (5)

[42]

**QUESTION 2**  
**SEMICONDUCTOR DEVICES**

2.1 Identify the following electronic components with reference to the electronic circuit diagram in **Figure 2**. For example:  $R_{10}$  is a 680 000 ohm resistor.

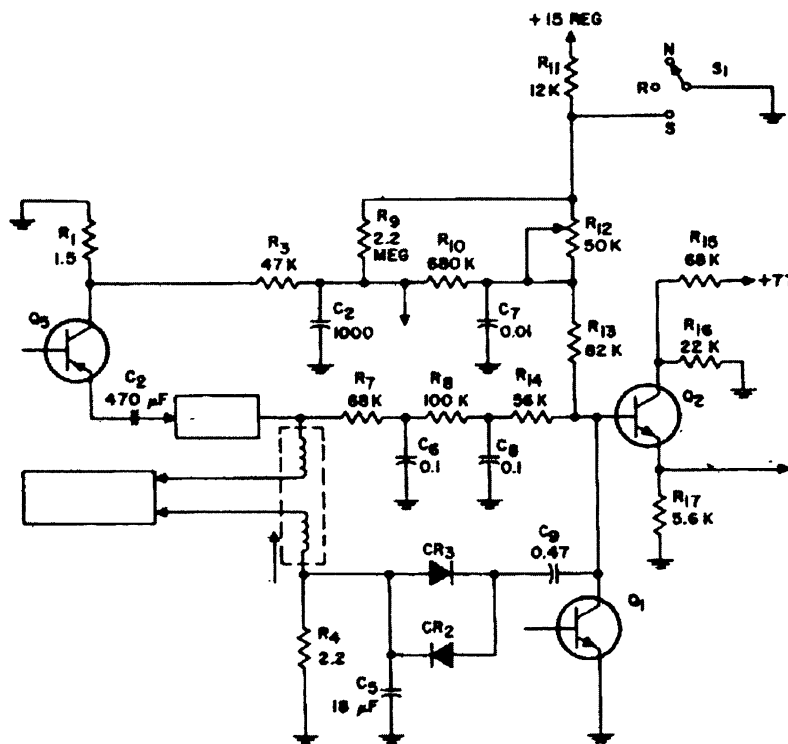

**Figure 2**  
**Vertical predriver with inputs**

2.1.1  $R_{13}$  (3)

2.1.2  $Q_5$  (2)

2.1.3  $C_6$  (2)

2.1.4  $CR_2$  (2)


2.1.5  $Q_1$  (2)

2.2 Explain briefly how you would test a diode by using an analogue multimeter. (Draw the necessary diagrams.) (10)

- 2.3 Maak netjiese, benoemde sketse om die basiese samestelling van die BSG te toon. Verduidelik die werkbeginsel van die BSG. (12)
- 2.4 Noem TWEE praktiese gebruike van 'n BSG. (2)  
[35]

### VRAAG 3 VERSTERKERS

- 3.1 Transistors word in verskillende stadiums met versterkers verbind om die vereiste versterking te verkry. Verduidelik aan die hand van 'n netjiese, benoemde diagram die basiese werkbeginsel van **óf** die resistor-kapasitor-gekoppelde versterker **óf** die transformator-gekoppelde versterker. (20)
- 3.2 Bereken die waardes vir en maak 'n netjiese benoemde skets van die laslyn vir die kring in **Figuur 3**. (10)

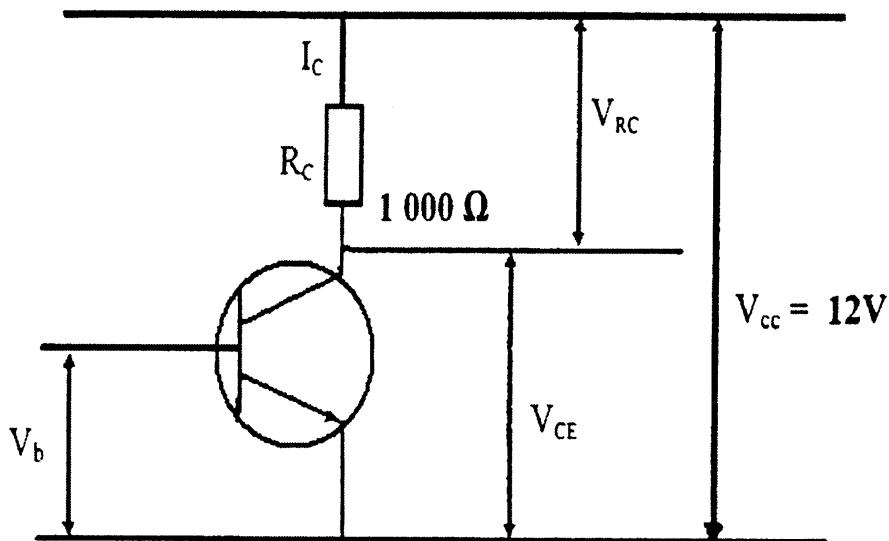

**Figuur 3**  
**Gemeenskaplike Emitterversterker**


- 3.3 Verduidelik kortliks wat jy onder die term **negatiewe terugvoering** verstaan met verwysing na versterkerkringe. (4)
- 3.4 Noem VYF kenmerke van 'n ideale operasionele versterker. (5)
- 3.5 Omskryf die volgende terme met verwysing na die operasionele versterker:
- 3.5.1 Gemeenskaplike modus (2)
- 3.5.2 Verskilmodus (2)

[43]

- 2.3 Draw neatly labelled sketches to show the basic composition of the SCR. Explain the principle of operation of the SCR. (12)
- 2.4 Name TWO practical uses of an SCR. (2)  
[35]

**QUESTION 3  
AMPLIFIERS**

- 3.1 Transistors are connected in different stages in amplifiers. This is done in order to obtain the required amplification. Explain with the aid of a neat, labelled diagram the principle of operation of **either** the RC coupled amplifier **or** the transformer-coupled amplifier. (20)
- 3.2 Calculate the values for and make a neat, labelled sketch of the load line for the circuit in **Figure 3**. (10)

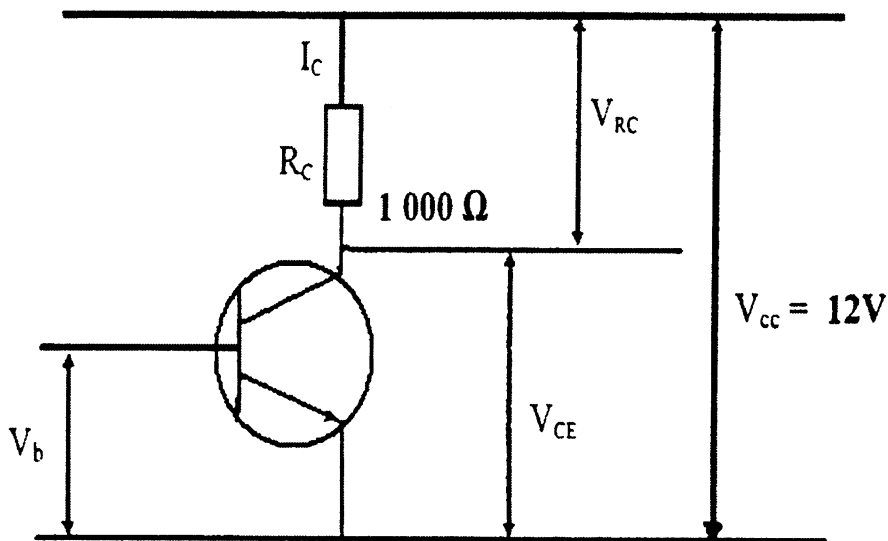

**Figure 3  
Common Emitter Amplifier**

- 3.3 Explain briefly what you understand by the term **negative feedback** with reference to amplifier circuits. (4)
- 3.4 State FIVE characteristics of an ideal operational amplifier. (5)
- 3.5 Explain the following terms with reference to the operational amplifier:
- 3.5.1 Common mode (2)
- 3.5.2 Differential mode (2)

[43]

**VRAAG 4  
SKAKEL- EN BEHEERKRINGE**

- 4.1 Teken 'n eenvoudige ligverdoefkring wat met 'n diak en 'n triak werk. Toon die in- en uitsetgolwe, asook die hekpuls. (10)
- 4.2 Teken 'n eenvoudige skets van 'n bistabiele multivibrator. (10)  
[20]

**VRAAG 5  
REKENAARBEGINSELS**

- 5.1 Illustreer die basiese werkbeginsel van die **OF-hek** aan die hand van 'n netjiese, benoemde simbool, 'n waarheidstabel en die ekwivalente kring, bestaande uit 'n battery, skakelaars en 'n lamp. (12)
- 5.2 Bewys met Boole-algebra dat die volgende stelling waar is.

$$A + B(A\bar{B}) = A$$


(10)  
[32]

**VRAAG 6  
INLIGTINGOORDRAG**

- 6.1 Teken 'n eenvoudige blokdiagram van 'n optiesevesel-telefoonstelsel. [15]

**VRAAG 7  
MEETINSTRUMENTE**

- 7.1 **Figuur 4** toon 'n gesigplaat van 'n ossilloskoop. Bepaal vanuit die golfvorm die volgende:
- 7.1.1 Die frekwensie (2)
- 7.1.2 Die gemiddelde waarde (2)
- 7.1.3 Die waarde wat 'n voltmeter sal vertoon, indien dit aan die kring verbind sal word (2)
- 7.1.4 Die effektiewe waarde (wgk) van die golf (2)

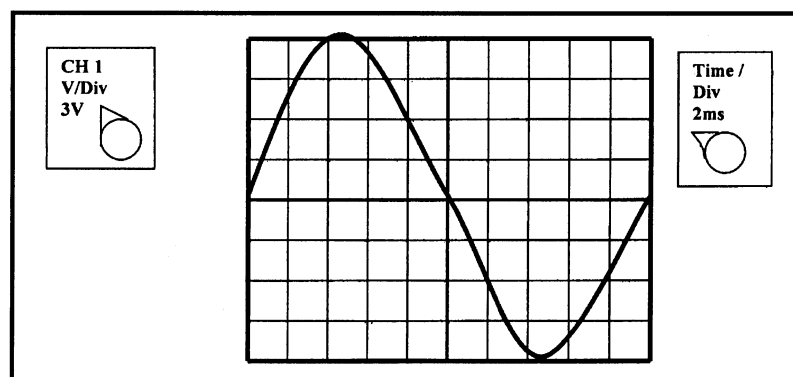

**Figuur 4  
Die ossilloskoop**

[8]



**QUESTION 4**  
**SWITCHING AND CONTROL CIRCUITS**

- 4.1 Draw a simple light dimmer circuit that uses a diac and a triac. The in and output waves as well as the gate pulse must be shown. (10)
- 4.2 Draw a simple sketch of a bistable multivibrator. (10)  
[20]

**QUESTION 5**  
**COMPUTER PRINCIPLES**

- 5.1 Illustrate the basic working principle of the **OR gate** by using a neat, labelled symbol, a truth table and the equivalent circuit consisting of a lamp, battery and switches. (12)
- 5.2 By using Boolean algebra, show that the following statement is true.

$$A + B(A.\bar{B}) = A$$


(10)  
[32]

**QUESTION 6**  
**INFORMATION TRANSFER**

- 6.1 Draw a simple block diagram showing a fibre-optic telephone system. [15]

**QUESTION 7**  
**MEASURING INSTRUMENTS**

- 7.1 **Figure 4** shows a faceplate of an oscilloscope. Determine from the waveform the following: (2)
- 7.1.1 The frequency (2)
- 7.1.2 The average value (2)
- 7.1.3 The value of the voltmeter if it is connected to the circuit. (2)
- 7.1.4 The effective value (RMS) of the wave (2)

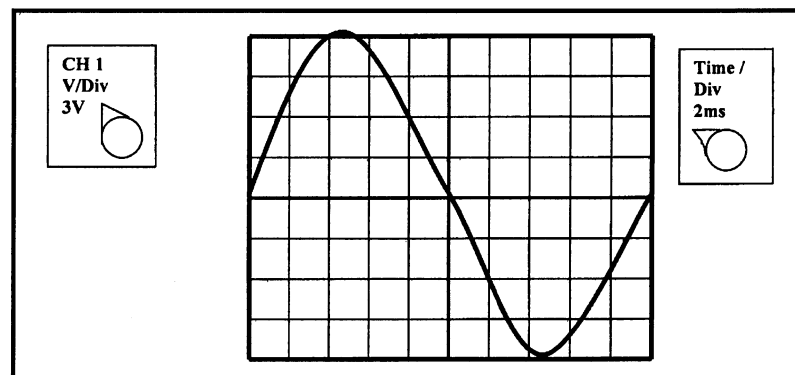

**Figure 4**  
**The Ossilloscope**

[8]

**VRAAG 8**  
**VEILIGHEIDSMATREËLS**

- 8.1 Noem EEN voorsorgmaatreeël wat getref moet word om te verhoed dat Vigs opgedoen word, indien daar 'n werkswinkelongeluk plaasvind. (3)
- 8.2 Verduidelik, in DRIE stappe, wat jy sal doen as jy opmerk dat 'n persoon wat elektriese skok opgedoen het, bewusteloos is. (6)
- 8.3 Noem VIER aspekte waaraan daar besondere aandag geskenk moet word wanneer draagbare elektriese kraggereedskap geïnspekteer word. (4)
- 8.4 Noem enige TWEE noodnommers in Suid-Afrika. (2)

(2)  
[15]

**TOTAAL: 200**

**QUESTION 8**  
**SAFETY PRECAUTIONS**

- 8.1 State ONE safety precaution that must be taken to prevent contracting Aids in the event of a workshop accident. (3)
- 8.2 Explain, in THREE steps, what your reaction would be if you noticed that a person who received an electrical shock is unconscious. (6)
- 8.3 State FOUR aspects that must be taken into consideration when inspecting portable electrical power tools. (4)
- 8.4 State any TWO emergency numbers in South Africa. (2)
- [15]**
- TOTAL: 200**



**INFORMATION SHEET / INLIGTINGSBLAD**

**ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE**

$$I = \frac{V}{R} \text{ AMPS}$$

$$P = V \times I \text{ WATT}$$

$$t = \frac{1}{F} \text{ seconds / sekondes}$$

$$V_{\text{ave. / gem.}} = V_m \times 0,637$$

$$V_{\text{rms. / wgk.}} = V_m \times 0,707$$

**STAR / STER**

$$V_L = \sqrt{3} \times V_P$$

$$I_L = I_P$$

**DELTA**

$$I_L = \sqrt{3} \times I_P$$

$$V_L = V_P$$

$$X_C = \frac{1}{2 \times \pi \times f \times C}$$

$$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$$

$$X_L = 2 \times \pi \times f \times L$$

$$f_r = \frac{1}{2 \times \pi} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$Q = \frac{X_L}{R}$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$Q = \frac{X_C}{R}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_X = V_L - V_C$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$



$$V_C = I_T \times X_C$$

$$V_L = I_T \times X_L$$

$$V_R = I_T \times R$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$V_X = V_C - V_L$$

$$I_T = \sqrt{I_R^2 + I_X^2}$$

$$I_X = I_C - I_L$$

$$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_X^2}$$

$$X_X = X_L - X_C$$

### **AMPLIFIERS / VERSTERKERS**

$$I_e = I_c + I_b$$

$$V_{cc} = V_{Rc} + V_{ce}$$

$$I_c = \frac{V_{cc}}{Rc}$$

### **DECIBEL RATIOS / DESIBELVERHOUDINGS**

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$





**OPERATIONAL AMPLIFIERS / OPERASIONELE VERSTERKERS**

$$A_v = -\frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_I$$

$$A_v = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_I$$

$$V_{OUT} = \frac{1}{RC} \int V_I dt$$

$$V_{OUT} = -RC \frac{dv}{dt}$$

$$V_{OUT} = -\left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3}\right)$$

**COMPUTER PRINCIPLES / REKENAARBEGINSELS**

$$A.B = B.A$$

$$A + B = B + A$$

$$A.(B.C) = (A.B).C$$

$$A + (B + C) = (A + B) + C$$

$$A.(B + C) = AB + AC$$

$$A + (B.C) = (A + B) + (A + C)$$

$$A(A + B) = A+B$$

$$A + (AB) = A.B$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A.0 = 0$$

$$A.1 = A$$

$$A + \underline{A} = A$$

$$A + A = 1$$

$$A.\underline{A} = A$$

$$A.A = 0$$