

GAUTENG DEPARTMENT OF EDUCATION  
SENIOR CERTIFICATE EXAMINATION

TECHNIKA (ELECTRONICS) SG

TIME: 3 hours

OCTOBER / NOVEMBER 2005  
OKTOBER / NOVEMBER 2005

MARKS: 200

INSTRUCTIONS:

- Answer ALL the questions.
- Sketches and diagrams must be large, neat and labelled.
- An approved calculator may be used.
- All calculations must be shown.
- Answers must be clearly numbered in accordance with the question paper.
- An information sheet is provided at the end of the paper.

QUESTION 1  
ELECTRIC CURRENT THEORY

- 1.1 Calculate, with reference to the circuit diagram in **Figure 1**, the
- 1.1.1 **capacitance** of the capacitor. (4)
- 1.1.2 **inductance** of the inductor. (4)
- 1.1.3 **total current** through the circuit. (7)
- 1.1.4 **voltage drop** across each component. (9)
- 1.1.5 power factor and phase angle of the circuit. (You need to sketch a fully labelled impedance triangle to support your answer.) (10)
- 1.2 Explain, by means of a fully labelled phasor diagram, the **voltage relationship** of the circuit in **Figure 1**. (6)


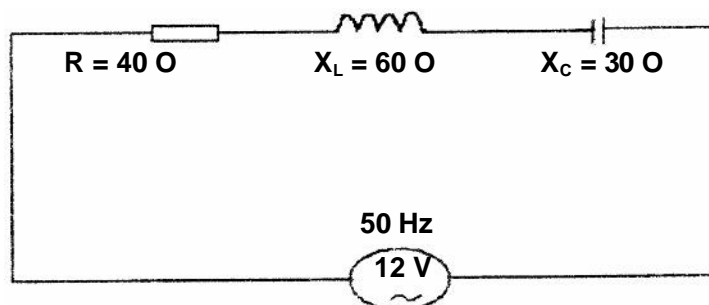


Figure 1  
RLC Circuit

[40]

**QUESTION 2**  
**SEMICONDUCTOR DEVICES**

2.1 Identify the following electronic components with reference to the electronic circuit diagram in **Figure 2**. For example: R3 is a 10 000 ohm resistor.

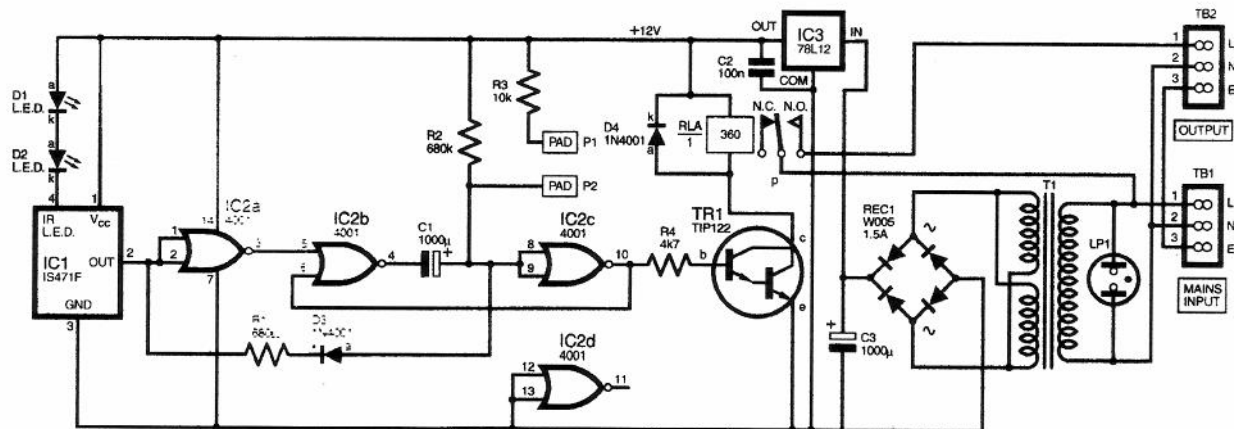


**Figure 2**

- 2.1.1 D 4 (2)
  - 2.1.2 TR 1 (3)
  - 2.1.3 REC 1 (1)
  - 2.1.4 IC2B (2)
  - 2.1.5 C 1 (2)
- 2.2 Explain briefly how you would test a transistor by using an analogue multimeter (Draw the necessary diagrams). (10)
- 2.3 Draw neat, labelled sketches to show the basic composition of the **unijunction transistor** (UJT). Also explain the basic working principle of the device. (Show the IV characteristics.) (12)
- 2.4 Name TWO practical uses of an **unijunction transistor** (UJT). (2)

[34]

**QUESTION 3  
AMPLIFIERS**

- 3.1 Transistors are connected in different stages in amplifiers. The reason for this is to get the needed amplification. Explain with the aid of a neat, labelled diagram and a brief description the operating principle of the **balanced amplifier** or the **radio frequency amplifier**. Choose ONE. (20)
- 3.2 Determine, by means of calculations and a neat, labelled sketch, the load line for the circuit shown in **Figure 3**. (10)

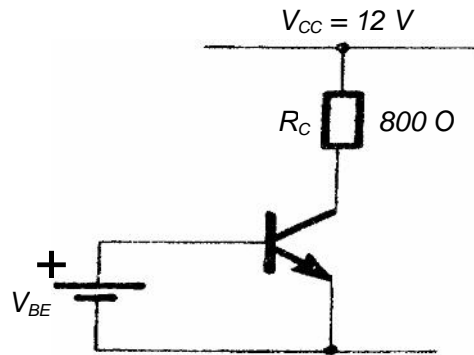

**Figure 3  
Common Emitter Amplifier**

- 3.3 Draw a labelled frequency response curve for each of the following circuits: (3)
- 3.3.1 Direct-coupled amplifier (3)
- 3.3.2 RC-coupled amplifier (5)
- 3.3.3 Transformer-coupled amplifier (5)
- [43]**

**QUESTION 4  
SWITCHING AND CONTROL CIRCUITS**

- 4.1 Draw a simple transistor **series voltage-regulator circuit**. (5)
- 4.2 Draw a simple sketch of a **bi-stable multivibrator** that makes use of an **operational amplifier**. (10)
- 4.3 Draw a neat, labelled sketch to indicate how speed control can be obtained in a DC motor by using a thyristor. (8)
- [23]**

**QUESTION 5**  
**COMPUTER PRINCIPLES**

5.1 Answer the following questions for EACH of the gates in Question 5.1.1 – 5.1.4.


- (a) Draw the **logic symbol**
- (b) Write the **Boolean equation** for each gate.
- (c) Draw the **truth table** for each by using binary 0's and 1's.

- 5.1.1 **NAND** gate (5)
- 5.1.2 **NOR** gate (5)
- 5.1.3 **AND** gate (5)
- 5.1.4 **OR** gate (5)

5.2 Answer the following questions for EACH of the circuits in Question 5.2.1 and 5.2.2.


- (a) Write down the **Boolean expression** for the input.
- (b) Create a **truth table** to explain the equation.

5.2.1

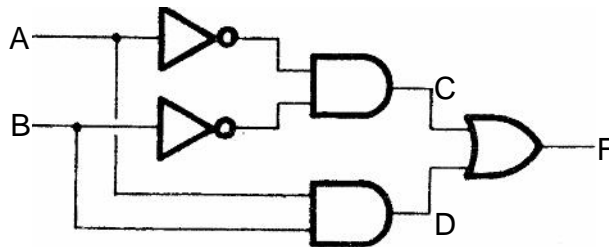

(8)

5.2.2

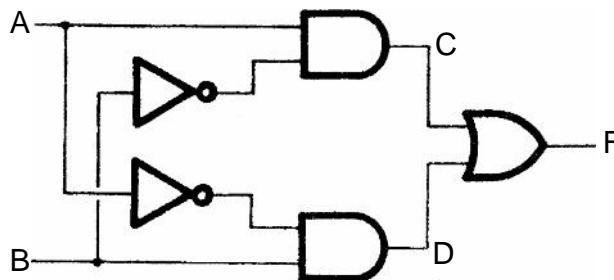

(8)  
[36]

<b>TECHNIKA (ELECTRONICS) SG</b> 714-2/0 K	<b>6</b>
---	----------

**QUESTION 6**  
**INFORMATION TRANSFER**

- 6.1 Draw a simple block diagram of an FM-radio transmitter. (7)  
[7]

**QUESTION 7**  
**SAFETY PRECAUTIONS**

- 7.1 State FOUR safety precautions that must be taken when working with an oscilloscope? (4)
- 7.2 Explain in THREE steps how you would act when somebody in the workshop sustained an injury and the wound is bleeding. (3)
- 7.3 Integrated circuits are very sensitive components. State THREE precautions that you would take when working with these components. (3)
- 7.4 State THREE safety precautions you would take before switching on the supply to a newly completed electrical project. (3)
- 7.5 Name FOUR safety measures that you would implement as workshop manager to guarantee the safety of the workers. (4)  
[17]

**TOTAL: 200**

INFORMATION SHEET / INLIGTINGSBLAD

ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE

$$I = \frac{V}{R} \text{ AMPS}$$

$$P = V \times I \text{ WATT}$$

$$t = \frac{1}{F} \text{ seconds / sekondes}$$

$$V_{\text{ave. / gem.}} = V_m \times 0,637$$

$$V_{\text{rms. / wgk.}} = V_m \times 0,707$$

STAR / STER

$$V_L = \sqrt{3} \times V_P$$

$$I_L = I_P$$

DELTA

$$I_L = \sqrt{3} \times I_P$$

$$V_L = V_P$$

$$X_C = \frac{1}{2 \times \pi \times F \times C}$$

$$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$$

$$X_L = 2 \times \pi \times F \times L$$

$$f_r = \frac{1}{2 \times \pi} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$Q = \frac{X_L}{R}$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$Q = \frac{X_C}{R}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_X = V_L - V_C$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_C = I_T \times X_C$$

$$V_L = I_T \times X_L$$

$$V_R = I_T \times R$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$V_X = V_C \approx V_L$$

$$I_T = \sqrt{I_R^2 + I_X^2}$$

$$I_X = I_C \approx I_L$$

$$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_X^2}$$

$$X_X = X_L \approx X_C$$

### AMPLIFIERS / VERSTERKERS

$$I_C + I_B$$

$$V_{CC} = V_{R_C} + V_{CE}$$

$$I_C = \frac{V_{CC}}{R_C}$$

### DECIBEL RATIOS / DESIBELVERHOUDINGS

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

OPERATIONAL AMPLIFIERS / OPERASIONELE VERSTERKERS

$$A_v = - \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_i$$

$$A_v = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_i$$

$$V_{OUT} = \frac{1}{RC} \int V_i \, dt$$

$$V_{OUT} = - RC \frac{dv}{dt}$$

$$V_{OUT} = - \left( V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3} \right)$$

COMPUTER PRINCIPLES / REKENAARBEGINSELS

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B + C) = AB + AC$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$A(A + B) = A$$

$$A + (AB) = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + \bar{A} = 1$$

$$A + A = A$$

$$A \cdot \bar{A} = 0$$

$$A \cdot A = A$$

END / EINDE