

**GAUTENG DEPARTMENT OF EDUCATION  
SENIOR CERTIFICATE EXAMINATION**

**TECHNIKA (ELECTRONICS) HG**

**TIME: 3 hours**

**MARKS: 300**

**INSTRUCTIONS:**

- Answer ALL the questions.
- Sketches and diagrams must be large, neat and labelled.
- All calculations must be shown.
- Answers must be clearly numbered.
- A formula sheet (pages 12 – 14) is provided at the end of the paper.

**QUESTION 1  
ELECTRIC CURRENT THEORY**

- 1.1 A series circuit consists of a coil with an inductance of 100 mH, a capacitor with a capacitance of 100  $\mu$ F and a resistor with a resistance of 100  $\Omega$ . The circuit is supplied from a 220 Volt / 50 Hz supply.

Calculate the


- |       |   |      |
|-------|---|------|
| 1.1.1 | inductive reactance.  | (3)  |
| 1.1.2 | capacitive reactance.   | (3)  |
| 1.1.3 | impedance.  | (3)  |
| 1.1.4 | phase angle. (First sketch a neat, labelled impedance diagram.) | (10) |
- 1.2 A series resonant circuit of a radio consists of a coil with an inductance of 400  $\mu$ H, a capacitor with a capacitance of 305,7 pF and a resistor with a resistance of 100  $\Omega$ . The input signal is 0,2V.
- Calculate the
- |       |                             |     |
|-------|-----------------------------|-----|
| 1.2.1 | resonant frequency.         | (3) |
| 1.2.2 | Q-Factor.                   | (3) |
| 1.2.3 | current value at resonance. | (4) |
- 1.3 Calculate the turns ratio required for an impedance matching transformer to satisfy the requirements of a loudspeaker with a 4  $\Omega$  voice coil. The transistor needs a 500  $\Omega$  load for maximum power transfer.

(4)  
**[33]**

**QUESTION 2**  
**SEMICONDUCTOR DEVICES**


2.1 Identify the following electronic components with reference to the electronic circuit diagram in **Figure 2.1** below. For example: R1 is a 1 MO resistor.

- 2.1.1 D2 (3)
- 2.1.2 S1 (2)
- 2.1.3 T2 (3)
- 2.1.4 BZ1 (1)
- 2.1.5 C5 (3)

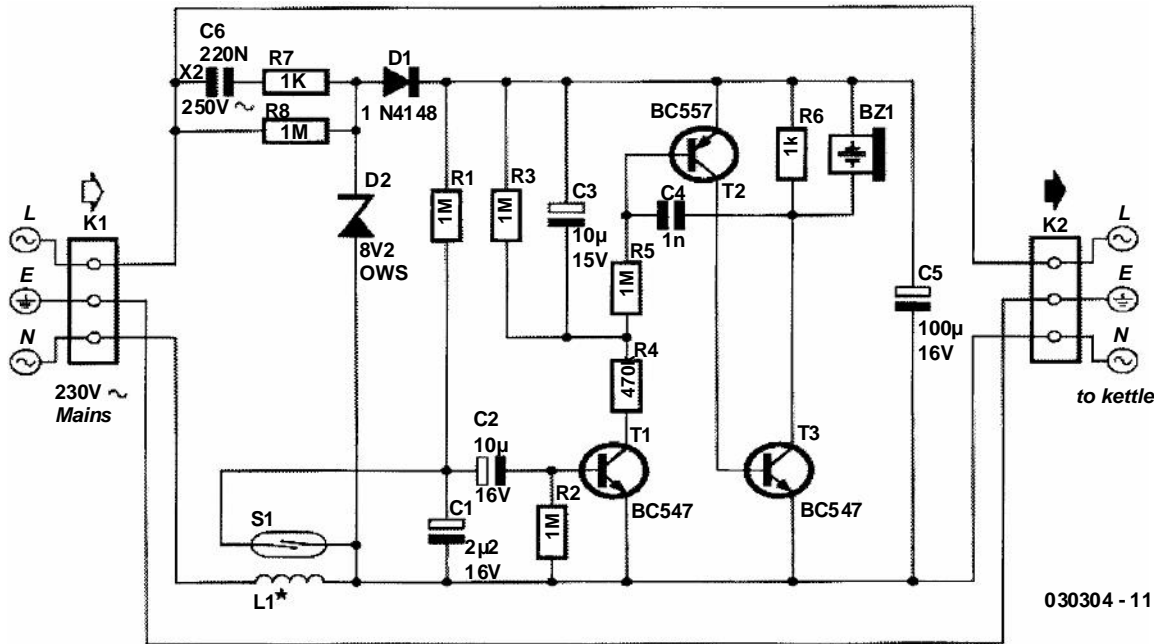

**Figure 2.1: Electronic circuit for a Whistling Kettle**

- 2.2 Refer to the electronic circuit in **Figure 2.2** and identify the transistor configuration. Explain by means of a brief description the basic operating principle and characteristics of this configuration. (11)

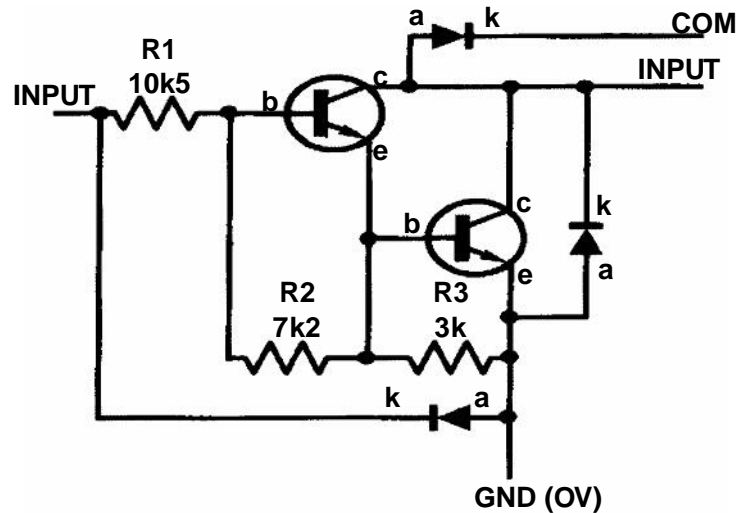


**Figure 2.2: Electronic Circuit**

- 2.3 The field effect transistor (FET) has been used since 1952 as a semiconductor device. Explain by means of neat, labelled sketches and brief descriptions, the basic **construction** and **functional** operation of a field effect transistor (FET). (12)
- 2.4 What major disadvantage of the diode bridge is overcome when filter capacitors are used in power supply units? (2)

[37]

### QUESTION 3 AMPLIFIERS

- 3.1 Design a dc bias circuit for the amplifier in **Figure 3.1**. The manufacturer's specifications state that the transistor has a current gain of 120, at a collector current of 10 mA, and a supply voltage of 12 Volt. (20)

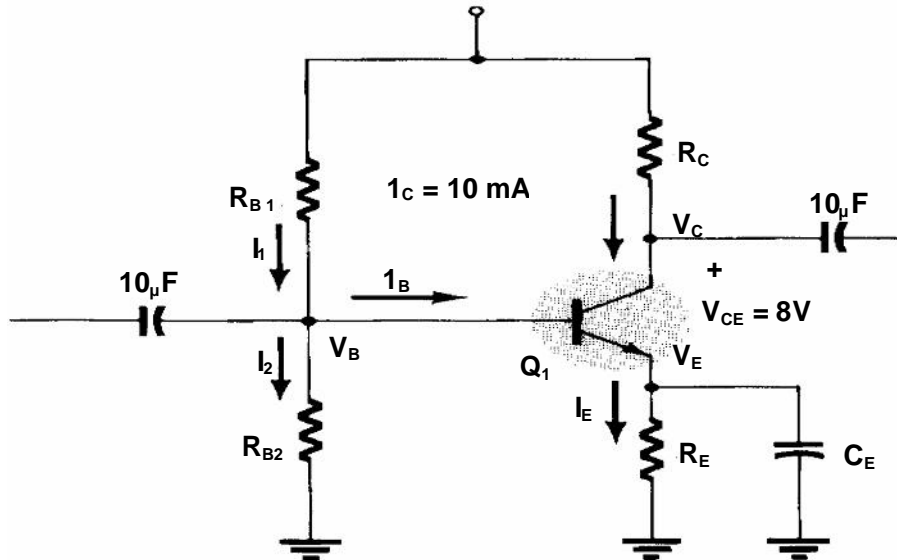


**Figure 3.1: Common-emitter amplifier**

- 3.2 A 741 operational amplifier is connected in the inverting mode. It amplifies a signal of 5 mV to 1 Volt. The input impedance is 1 MO.
- 3.2.1 Draw a neat, labelled diagram of the circuit. (10)
- 3.2.2 Determine the value of the feedback resistor by means of calculations. (7)
- 3.3 Calculate the dB increase in power if the input frequency to a certain filter increases from 10 kHz to 20 kHz and the output power rises from 50 mW to 100 mW. (4)

[41]

**QUESTION 4**  
**SWITCHING AND CONTROL CIRCUITS**

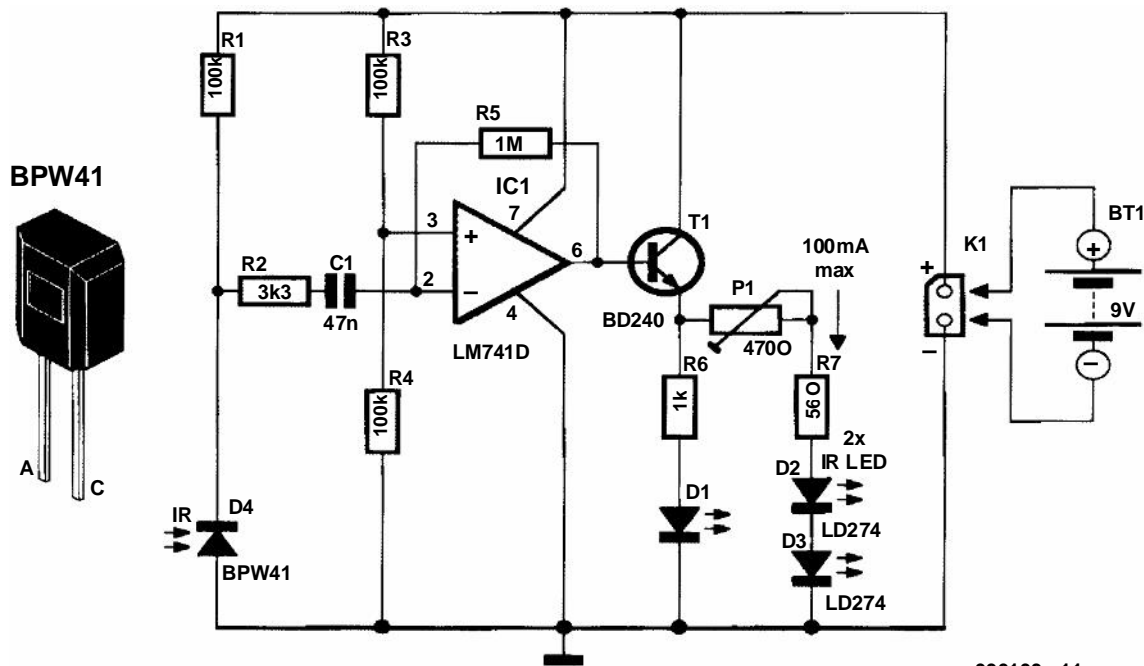- 4.1 Draw a neat, labelled circuit diagram of an astable multivibrator. You may use discrete components or operational amplifiers in your circuit. Relevant input and output waveforms should be indicated. (15)
- 4.2 The electronic circuit in **Figure 4.1** illustrates an Infra-red Control Extender used to extend the range of the available controller, receiving the Infra-red Signal (IR-signal) from your remote control and re-transmitting it, for example around a corner into another room. Explain the working principle of this circuit. (12)




030103 - 11

**Figure 4.1: Infra-red Control Extender**


4.3 Clippers and clampers are diode waveshaping circuits transmitting parts of waveforms and suppressing others to a predetermined value. Find the output voltage wave shape for the inputs shown in **Figure 4.2**. (Only sketch the output voltage wave shape in your answer book.)

4.3.1

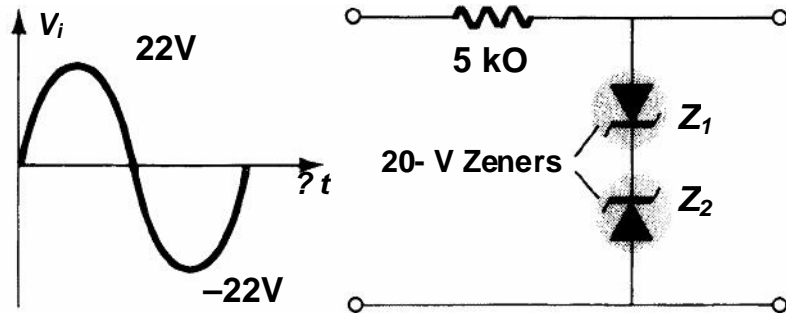

(4)

4.3.2

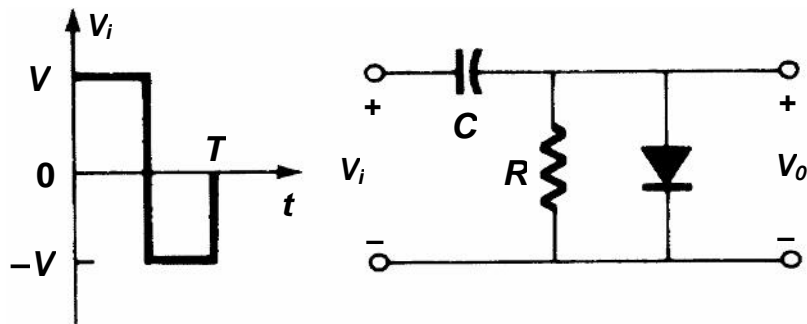

(4)

**Figure 4.2: Waveshaping circuits**

4.4 Explain the working principle of ANY electronic experiment OR model that you have built/designed this year. Take note that your explanation should include a neat, labelled circuit diagram or block diagram with a brief description. All wave forms, where applicable, should be included. Please note that the description should directly link to your circuit diagram. You are not allowed to replicate a question already covered in this question paper.

(15)  
[50]

**QUESTION 5  
OSCILLATORS**

5.1 Draw a neat, labelled circuit diagram of the crystal controlled Colpitts Oscillator.

(10)

5.2 Explain the **piezoelectric effect** with reference to the quartz crystal.

(4)

5.3 Draw a neat, labelled graph to illustrate the effect resonant frequency has on the impedance of a crystal.

(4)  
[18]

**QUESTION 6**  
**COMPUTER PRINCIPLES**

- 6.1 Design a NOR gate network for the following Boolean expression (A, B, C and D are direct gate inputs.):

$$F = (A.B) + (C.D) \quad (7)$$


- 6.2 Observe the following Boolean expression and complete the questions below:

$$F = (A.B)' + (A' + B)'$$

- 6.2.1 Simplify the Boolean expression above. (4)
- 6.2.2 Draw a logic gate circuit for the simplified circuit. (3)
- 6.3 You have been contracted by a leading electronics company to design a logic system that will satisfy the following needs:

An electric light is to be controlled by three switches. The light is to be ON whenever switches **A** and **B** are in the same position; when **A** and **B** are in different positions, the light is to be controlled by switch **C**.

- 6.3.1 Draw up a truth table for this situation. (8)
- 6.3.2 Represent the light function **F** in terms of **A**, **B** and **C**. (4)
- 6.3.3 Simplify the function and design a practical logic circuit. (4)
- 6.4 Refer to **Figure 6.1** and draw a truth table that will satisfy the possible solution of this logic circuit. (9)

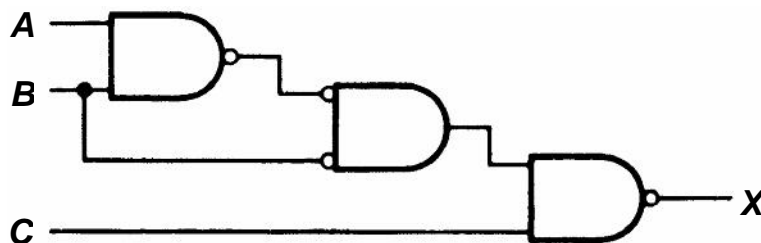

**Figure 6.1: Logic circuit**

- 6.5 Illustrate by means of a neat, labelled logic circuit and a Boolean expression, the Full Adder with SUM and CARRY. (16)

[55]

**QUESTION 7**  
**INFORMATION TRANSFER**

- 7.1 All frequencies above the range of human hearing (>20kHz) are called radio frequencies (RF). These frequencies fall into frequency bands, each with different uses. Refer to **Table 7.1** and complete the table. Write each answer in your answer book next to the appropriate number. (6)

BAND	TERM	USES
7.1.1	Low Frequency (LF)	Long-distance communication
300 kHz – 3 MHz	7.1.2	Medium-wave broadcasting
3 MHz – 30 MHz	High Frequency (HF)	7.1.3
30 MHz – 300 MHz	Very High Frequency (VHF)	7.1.4
7.1.5	Ultra High Frequency (UHF)	TV bands, M-Net, e.tv
Above 3 GHz	7.1.6	Radar, Satellite communication, Fibre optic


**Table 7.1**

- 7.2 Name TWO advantages of fibre optic systems. (2)
- 7.3 Explain by means of a neat, labelled block diagram the basic working principle of a typical fibre-optic communication system. (12)
- 7.4 Explain the purpose of the repeater with reference to Question 7.3. (5)
- 7.5 Name the major causes of signal losses in fibre optic cables. (8)
- [33]**




**QUESTION 8**  
**MEASURING INSTRUMENTS**

- 8.1 Explain the working principle of a digital voltmeter by means of a neat, labelled block diagram. (10)
- 8.2 Examine **Figure 8.1** and determine the reading of the multimeter if the range switch is on X 1M. (2)

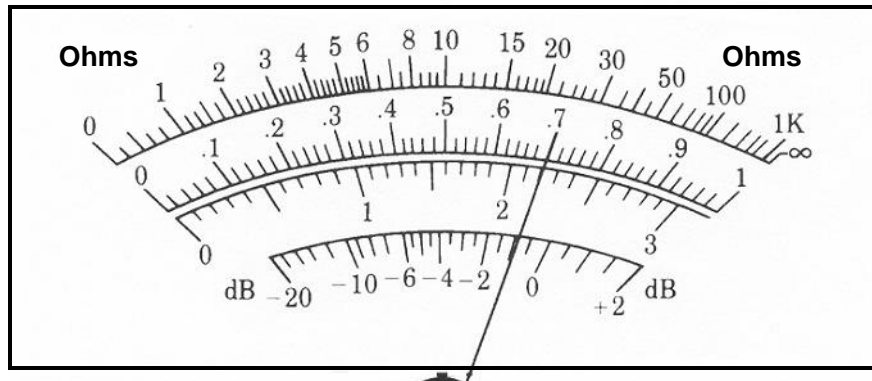

**Figure: 8.1 Multimeter reading**

- 8.3 Examine the sine waveform in **Figure 8.2** and
  - 8.3.1 determine the peak-to-peak voltage of the wave if the Volts/Division switch is on 2 mV/Division. (3)
  - 8.3.2 determine the frequency if the Time/Division switch of the oscilloscope is set at 50µsec/Div. (6)

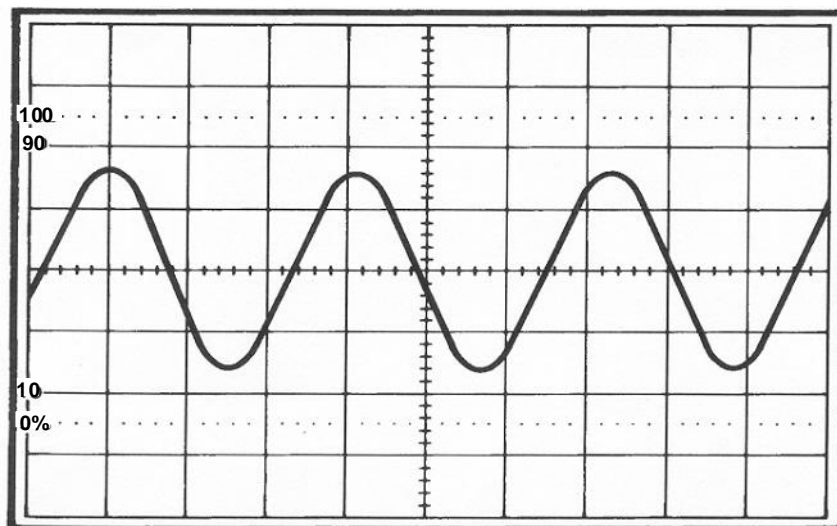


**Figure 8.2: Waveform**

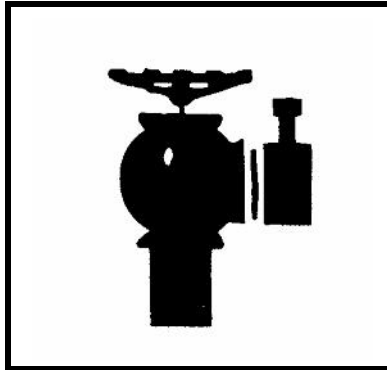[21]

**QUESTION 9**  
**SAFETY PRECAUTIONS**

- 9.1 Name FOUR housekeeping rules that you have applied in your workshop this year. (4)
- 9.2 Identify the following safety sign: (1)



- 9.3 Answer the following questions. Only write TRUE or FALSE next to the appropriate question in your answer book.
- 9.3.1 You will not be given a life insurance policy if you tested positive with HIV. (1)
- 9.3.2 It is a criminal offence if you do not disclose your HIV status to your sexual partner. (1)
- 9.3.3 You will be excluded from employment if you are HIV positive. (1)
- 9.4 Name ONE law that will protect your rights in the workplace. (1)
- 9.5 Explain the term **window period** with reference to HIV/Aids testing. (3)

[12]

**TOTAL: 300**

**INFORMATION SHEET / INLIGTINGSBLAD**

**ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE**

$$I = \frac{V}{R} \text{ AMPS}$$

$$P = V \times I \text{ WATT}$$

$$t = \frac{1}{F} \text{ seconds / sekondes}$$

$$V_{\text{ave./gem.}} = V_m \times 0,637$$

$$V_{\text{rms./wgk.}} = V_m \times 0,707$$

$$X_C = \frac{1}{2 \times \pi \times f \times C}$$

$$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$$

$$X_L = 2 \times \pi \times f \times L$$

$$f_r = \frac{1}{2 \times \pi} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$Q = \frac{X_L}{R}$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$Q = \frac{X_C}{R}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_X = V_L - V_C$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_C = I_T \times X_C$$

$$V_L = I_T \times X_L$$

$$V_R = I_T \times R$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$V_X = V_C - V_L$$

$$I_T = \sqrt{I_R^2 + I_X^2}$$

$$I_X = I_C - I_L$$

$$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_X^2}$$

$$X_X = X_L - X_C$$

### **AMPLIFIERS / VERS TERKERS**

$$I_e = I_c + I_b$$

$$V_{cc} = V_{Rc} + V_{ce}$$

$$I_c = \frac{V_{cc}}{Rc}$$

$$V_e \cong \frac{1}{10} V_{cc}$$

### **DECIBEL RATIOS / DESIBE L-VERHOUDINGS**

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

**OPERATIONAL AMPLIFIERS / OPERASIO NELE VERS TERKERS**

$$A_v = - \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_I$$

$$A_v = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_I$$

$$V_{OUT} = \frac{1}{RC} \int V_I dt$$

$$V_{OUT} = - RC \frac{dv}{dt}$$

$$V_{OUT} = - \left( V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3} \right)$$

**COMPUTER PRINCIPLES / REKE NAARBE GINSELS**

$$A.B = B.A$$

$$A + B = B + A$$

$$A.(B.C) = (A.B).C$$

$$A + (B + C) = (A + B) + C$$

$$A.(B + C) = AB + AC$$

$$A + (B.C) = (A + B).(A + C)$$

$$A(A + B) = A$$

$$A + (AB) = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A.0 = 0$$

$$A.1 = A$$

$$A + \underline{A} = A$$

$$A + A = 1$$

$$A.\underline{A} = A$$

$$A.A = 0$$

**END / EINDE**