

GAUTENG DEPARTMENT OF EDUCATION
SENIOR CERTIFICATE EXAMINATION

FEB / MAR 2006

TECHNIKA (ELECTRONICS) SG

TIME: 3 hours

MARKS: 200

INSTRUCTIONS:

- Answer ALL the questions.
- Sketches and diagrams must be large, neat and labelled.
- An approved calculator may be used.
- All calculations must be shown.
- Answers must be clearly numbered in accordance with the question paper.
- An information sheet is provided at the end of the paper.

QUESTION 1
ELECTRIC CURRENT THEORY

1.1 Study the parallel circuit in **Figure 1** and calculate the following:

- 1.1.1 The reactance of each component (4)
 1.1.2 The current which will flow through each branch (6)
 1.1.3 The total supply current (3)
 1.1.4 The total circuit impedance (3)

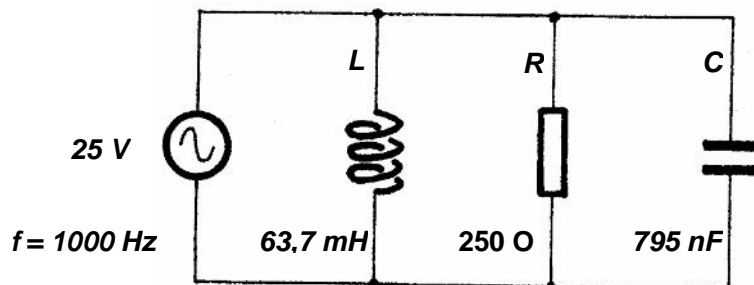


Figure 1
RLC Circuit

1.2 A series RLC-tuned circuit has a resonant frequency of 95 MHz and a bandwidth of 200 kHz. If the capacitor is a 2,5 pF and the wire used to wind the coil has zero resistance, calculate the

- 1.2.1 Q-factor of the circuit. (3)
 1.2.2 size of the necessary coil. (5)
 1.2.3 resistance of the circuit. (3)

[27]

**QUESTION 2
SEMICONDUCTOR DEVICES**

- 2.1 The “Darlington pair” transistor is a widely implemented device in power electronics such as car amplifiers and Hi-Fi systems. Explain, by means of a neat, labelled sketch and a brief description, the basic construction and functional operation of a Darlington transistor (Darlington pair). (12)
- 2.2 With the aid of sketches and a brief explanation, describe any project you did this year regarding semiconductor devices. (10)
- 2.3 Using your knowledge of semiconductors, draw the circuit symbol for each of the following:
- 2.3.1 NPN-transistor (2)
 - 2.3.2 FET-transistor (2)
 - 2.3.3 SCR (Silicon-controlled rectifier) (2)
 - 2.3.4 UJT transistor (2)
- [30]**

**QUESTION 3
AMPLIFIERS**

- 3.1 Transistors are connected in different stages in amplifiers to get the necessary amplification. Explain with the aid of a neat, labelled sketch and a brief description the working principle of the **balanced coupled amplifier** OR the **resistor-capacitor coupled amplifier**. (20)
- 3.2 Show, by means of neatly labelled **graphs**, the difference between the **Class B** and **Class C amplifiers**. The position of the static working point (the Q- point) and all in- and output wave forms must be shown on each graph. (10)
- 3.3 Explain briefly what is understood by **bandwidth** with regards to amplifiers. (4)
- [34]**

**QUESTION 4
SWITCHING AND CONTROL CIRCUITS**

- 4.1 Identify the following circuits and write brief notes to explain the working principle of each:

4.1.1

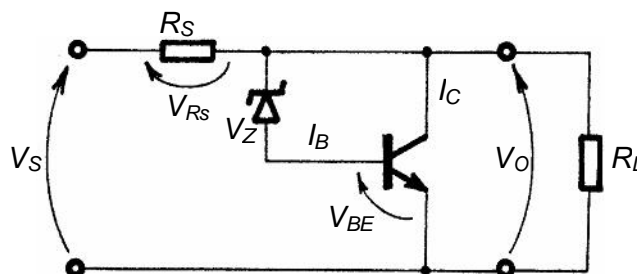


Figure 2

(6)

4.1.2

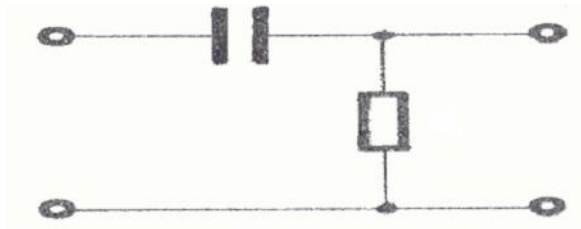


Figure 3

(6)

4.1.3

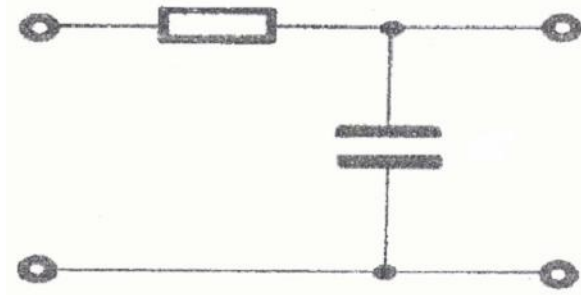


Figure 4

(6)

4.1.4

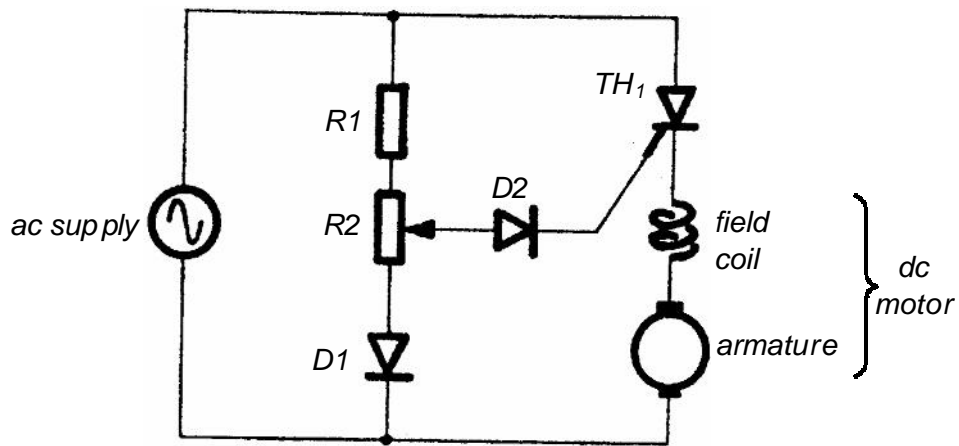


Figure 5

(6)

[24]

**QUESTION 5
COMPUTER PRINCIPLES**

5.1 For each of the following circuits (5.1.1 – 5.1.4):

- (a) Write the Boolean expression for the input.
- (b) Create a truth table to explain the equation.

5.1.1

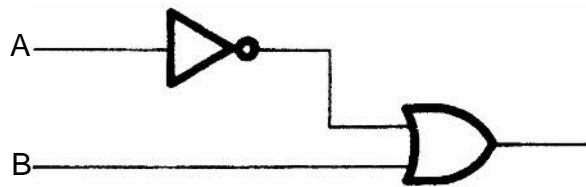


Figure 6

(7)

5.1.2

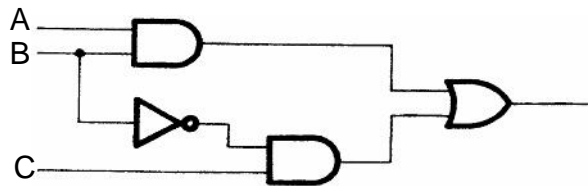


Figure 7

(13)

5.1.3

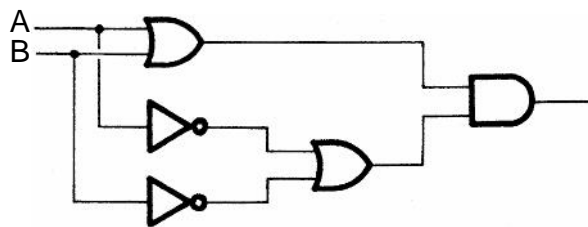


Figure 8

(13)

5.1.4

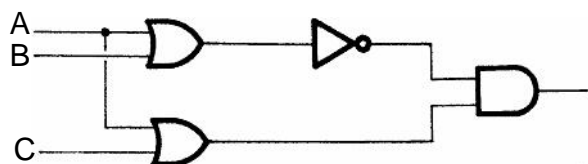


Figure 9

(10)

[43]

P.T.O.

TECHNIKA (ELECTRONICS) SG 714-2/0 L	6
--	---

QUESTION 6
MEASURING INSTRUMENTS

- 6.1 Draw a neat, labelled block diagram to explain the working principle of an oscilloscope. (15)
- 6.2 State THREE uses of a multimeter. (3)
- 6.3 Draw a neat, labelled block diagram explaining the working principle of a digital multimeter. (6)
- [24]**

QUESTION 7
SAFETY PRECAUTIONS

- 7.1 What is the difference between an **unsafe act** and an **unsafe condition**? (3)
- 7.2 State FOUR unsafe acts. (4)
- 7.3 State FOUR unsafe conditions. (4)
- 7.4 Why should direct pressure be applied to a gushing wound? (5)
- 7.5 State TWO safety measures, which must be adhered to when working with a multimeter. (2)
- [18]**

TOTAL: 200

INFORMATION SHEET / INLIGTINGSBLAD

ELECTRIC CURRENT THEORY / ELEKTRIESE STROOMTEORIE

$$I = \frac{V}{R} \text{ AMPS}$$

$$P = V \times I \text{ WATT}$$

$$t = \frac{1}{F} \text{ seconds / sekondes}$$

$$V_{\text{ave. / gem.}} = V_m \times 0,637$$

$$V_{\text{rms. / wgk.}} = V_m \times 0,707$$

STAR / STER

$$V_L = \sqrt{3} \times V_P$$

$$I_L = I_P$$

DELTA

$$I_L = \sqrt{3} \times I_P$$

$$V_L = V_P$$

$$X_C = \frac{1}{2 \times \pi \times F \times C}$$

$$f_r = \frac{1}{2 \times \pi \times \sqrt{LC}}$$

$$X_L = 2 \times \pi \times F \times L$$

$$f_r = \frac{1}{2 \times \pi} \times \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$Q = \frac{X_L}{R}$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$Q = \frac{X_C}{R}$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_X = V_L - V_C$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_C = I_T \times X_C$$

$$V_L = I_T \times X_L$$

$$V_R = I_T \times R$$

$$V_T = \sqrt{V_R^2 + V_X^2}$$

$$V_X = V_C \approx V_L$$

$$I_T = \sqrt{I_R^2 + I_X^2}$$

$$I_X = I_C \approx I_L$$

$$\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_X^2}$$

$$X_X = X_L \approx X_C$$

AMPLIFIERS / VERSTERKERS

$$I_C + I_B$$

$$V_{CC} = V_{R_C} + V_{CE}$$

$$I_C = \frac{V_{CC}}{R_C}$$

DECIBEL RATIOS / DESIBELVERHOUDINGS

$$G_I = 20 \text{ LOG } \frac{I_2}{I_1}$$

$$G_V = 20 \text{ LOG } \frac{V_2}{V_1}$$

$$G_P = 10 \text{ LOG } \frac{P_2}{P_1}$$

OPERATIONAL AMPLIFIERS / OPERASIONEL E VERSTERKERS

$$A_v = - \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_i$$

$$A_v = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = A_v \times V_i$$

$$V_{OUT} = \frac{1}{RC} \int V_i dt$$

$$V_{OUT} = - RC \frac{dv}{dt}$$

$$V_{OUT} = - \left(V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + V_3 \frac{R_F}{R_3} \right)$$

COMPUTER PRINCIPLES / REKENAARBEGINSELS

$$A.B = B.A$$

$$A + B = B + A$$

$$A.(B.C) = (A.B).C$$

$$A + (B + C) = (A + B) + C$$

$$A.(B + C) = AB + AC$$

$$A + (B.C) = (A + B) . (A + C)$$

$$A(A + B) = A$$

$$A + (AB) = A$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A.0 = 0$$

$$A.1 = A$$

$$A + \underline{A} = A$$

$$A + A = 1$$

$$A.\underline{A} = A$$

$$A.\underline{\underline{A}} = 0$$

END / EINDE