

# **X025/201**

---

NATIONAL  
QUALIFICATIONS  
2007

MONDAY, 4 JUNE  
9.00 AM – 11.30 AM

ELECTRONIC AND  
ELECTRICAL  
FUNDAMENTALS  
INTERMEDIATE 2

100 marks are allocated to this paper.

Answer **all** questions in Section A (50 marks).

Answer **two** questions from Section B (25 marks each).

A Datasheet is provided for questions 5 and 8.

In all your answers to questions requiring calculations, all working **must** be shown.



## Section A

Attempt all the questions in this section (50 marks)

1. Convert the following numbers.

- |                            |              |            |
|----------------------------|--------------|------------|
| (a) Binary to decimal      | $11001011_2$ | 2          |
| (b) Decimal to hexadecimal | $96_{10}$    | 2          |
| (c) Hexadecimal to binary  | $E5_{16}$    | 2          |
|                            |              | <b>(6)</b> |

2. The diagrams in Figure Q2 show input and output waveforms to and from electronic circuits labelled **X** and **Y**.

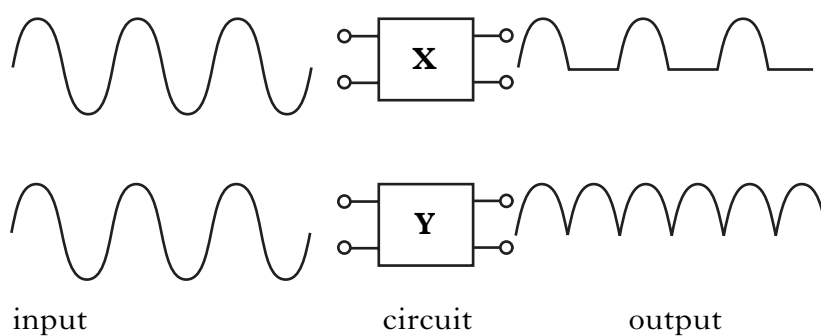


Figure Q2

State the full name for each type of circuit for:

- |                        |            |
|------------------------|------------|
| (a) circuit <b>X</b> ; | 2          |
| (b) circuit <b>Y</b> . | 2          |
|                        | <b>(4)</b> |

3. With reference to Figures Q3 (a) and (b), identify the following circuit symbols.

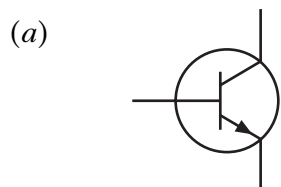


Figure Q3(a)

1



Figure Q3(b)

1

**(2)**

4.

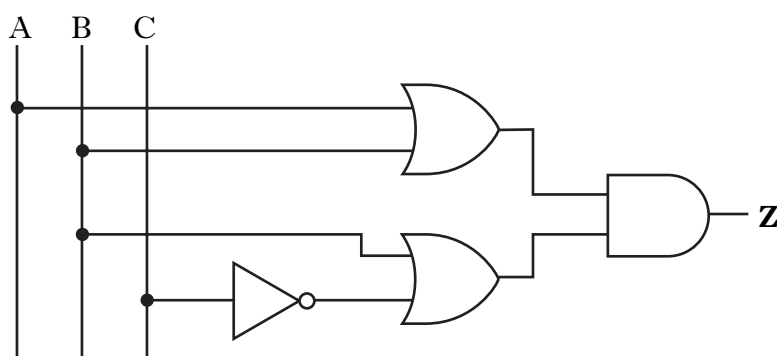


Figure Q4

For the circuit shown in Figure Q4:

- determine the Boolean expression for output **Z**;
- draw the truth table for the circuit;
- determine the circuit output **Z** when a fault condition causes input B to be permanently high.

2

4

2

**(8)**

5. Referring to Figure Q5 and using the supplied datasheet:

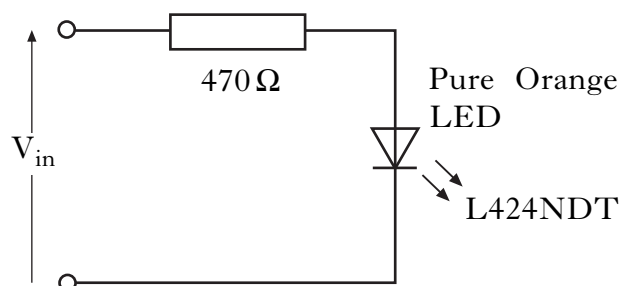


Figure Q5

- determine the maximum current the diode can handle;
- determine the typical forward voltage drop;
- calculate the maximum value of input voltage that can be applied.

1

1

3

**(5)****[Turn over]**

6. The coil B shown in Figure Q6 moves at a constant speed of  $5 \text{ m s}^{-1}$  through a magnetic field with a flux density of  $0.8 \text{ T}$ . The maximum induced voltage is  $6.8$  volts.

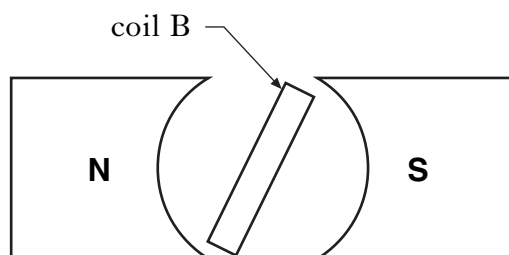


Figure Q6

- (a) Calculate the effective length of the coil. 2
- (b) State the **two** angles relative to the magnetic field where the maximum instantaneous voltage will occur. 2
- (4)**

7.

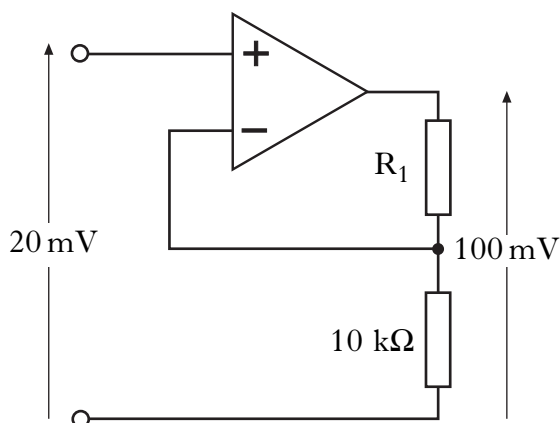


Figure Q7

With reference to the circuit shown in Figure Q7:

- (a) identify the circuit configuration; 1
- (b) calculate the circuit gain; 1
- (c) determine the value of resistor  $R_1$ ; 2
- (d) if the input voltage increases to  $25 \text{ mV}$ , determine the value of a resistor to replace  $R_1$ , to maintain the same value of output voltage. 2
- (6)**

8.

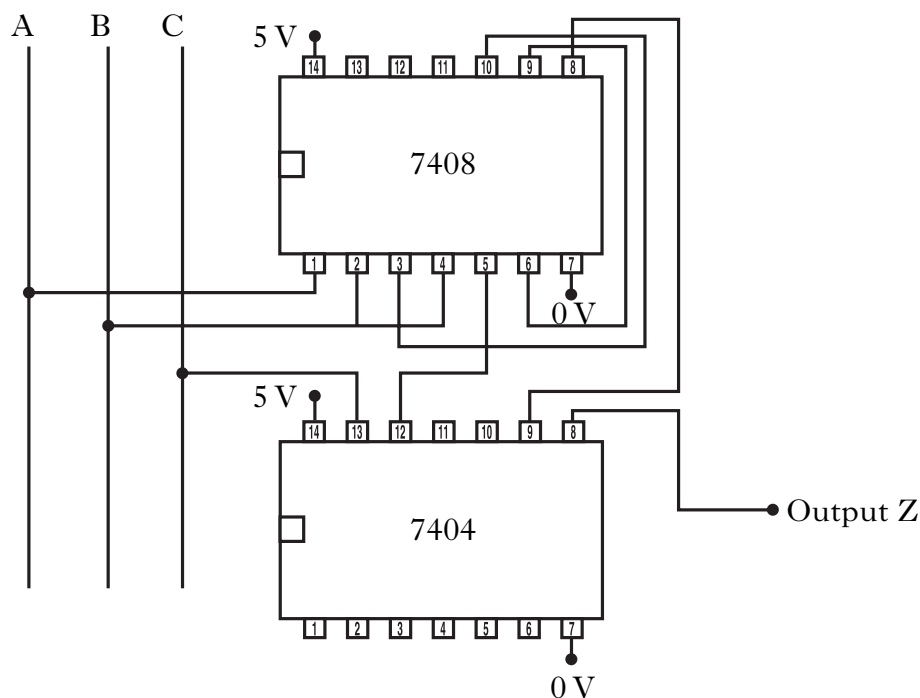


Figure Q8

Figure Q8 shows a logic circuit. With reference to the data sheet:

- draw the logic diagram; 3
  - draw the truth table for the circuit; 4
  - a fault condition causes input 9 on the 7408 to be permanently low. State the effect on the circuit output Z and **justify** your answer. 2
- (9)**

9.

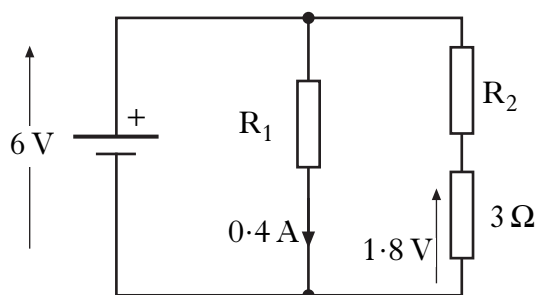


Figure Q9

For the circuit shown in Figure Q9, determine:

- the resistance of the resistor  $R_1$ ; 1
  - the current through the  $3\ \Omega$  resistor; 1
  - the resistance of the resistor  $R_2$ ; 2
  - the total circuit resistance. 2
- (6)**

**[BLANK PAGE]**

## Section B

Attempt any TWO questions in this section (50 marks).  
Each question is worth 25 marks.

10. (a) Identify the following circuit symbols:



(b) Under test conditions a diode was found to exhibit the following characteristics.

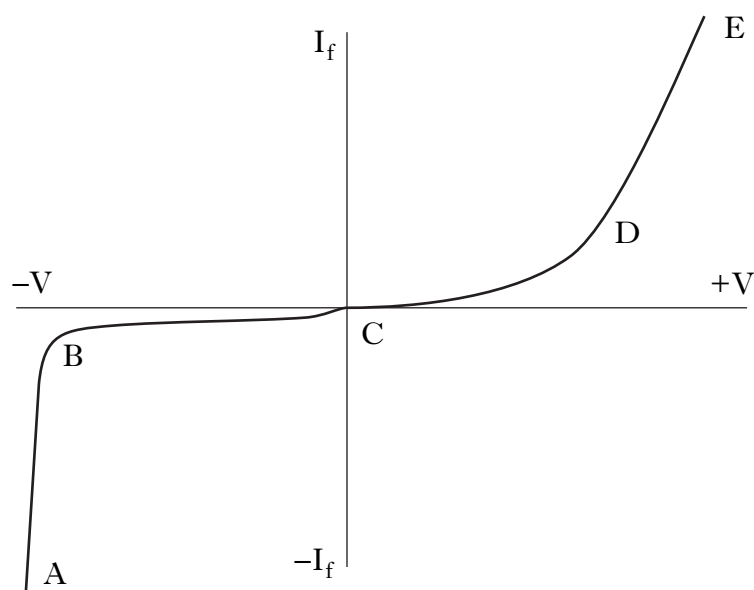


Figure Q10(b)

Identify with the use of the letters A to E on the characteristic Figure Q10(b) where the following begins:

- (i) reverse breakdown; 1  
(ii) forward conduction. 1

## 10. (continued)

- (c) Identify the type of semiconductor device that would most likely produce the characteristic shown in Figure Q10(c) under test conditions.

2

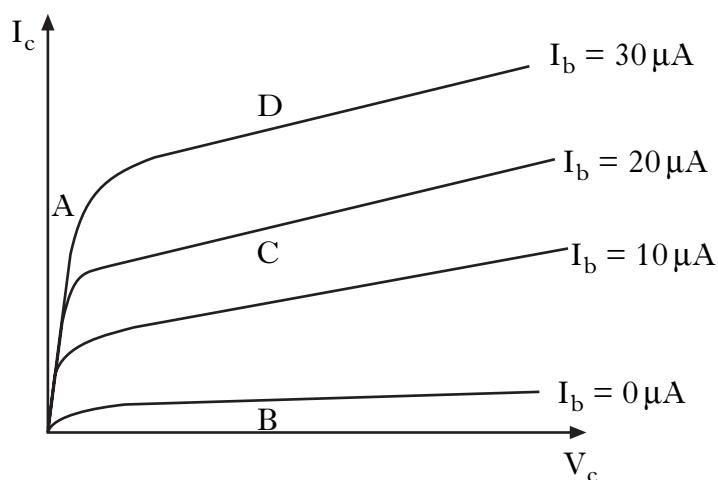


Figure Q10(c)

- (d) For the characteristics shown in Figure Q10(c) identify the areas where the device is acting as:

(i) a switch in the OFF position;

1

(ii) a current control device;

1

(iii) a switch in the ON position.

1

- (e) Identify the circuit shown in Figure Q10(e)(i) and identify the terminals labelled 1, 2 and 3.

2,3

(i)

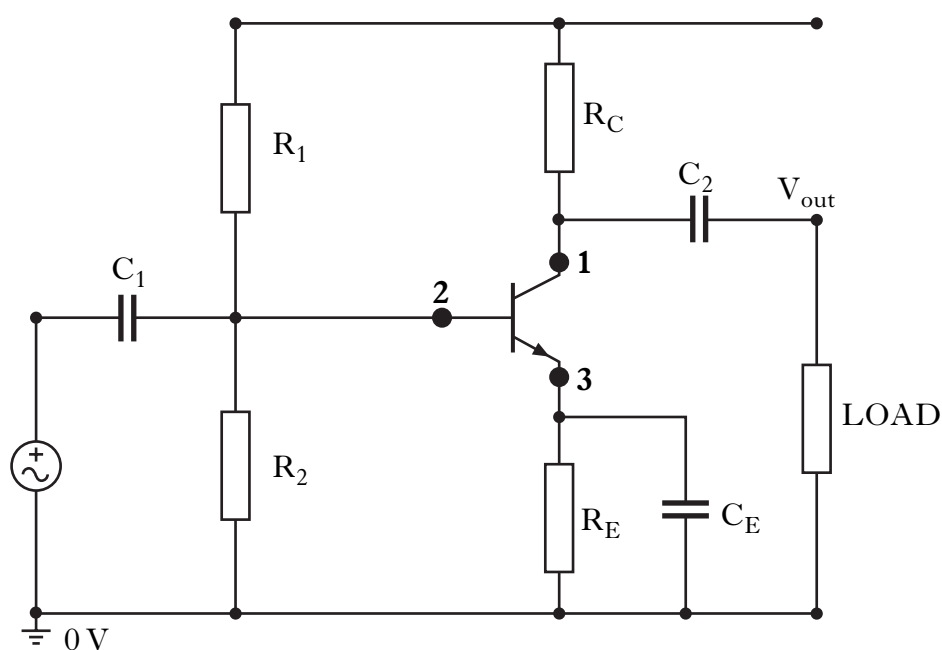


Figure Q10(e)(i)



## 10. (e) (continued)

- (ii) Identify the circuit shown in Figure Q10(e)(ii) and identify the terminals 1, 2 and 3.

2,3

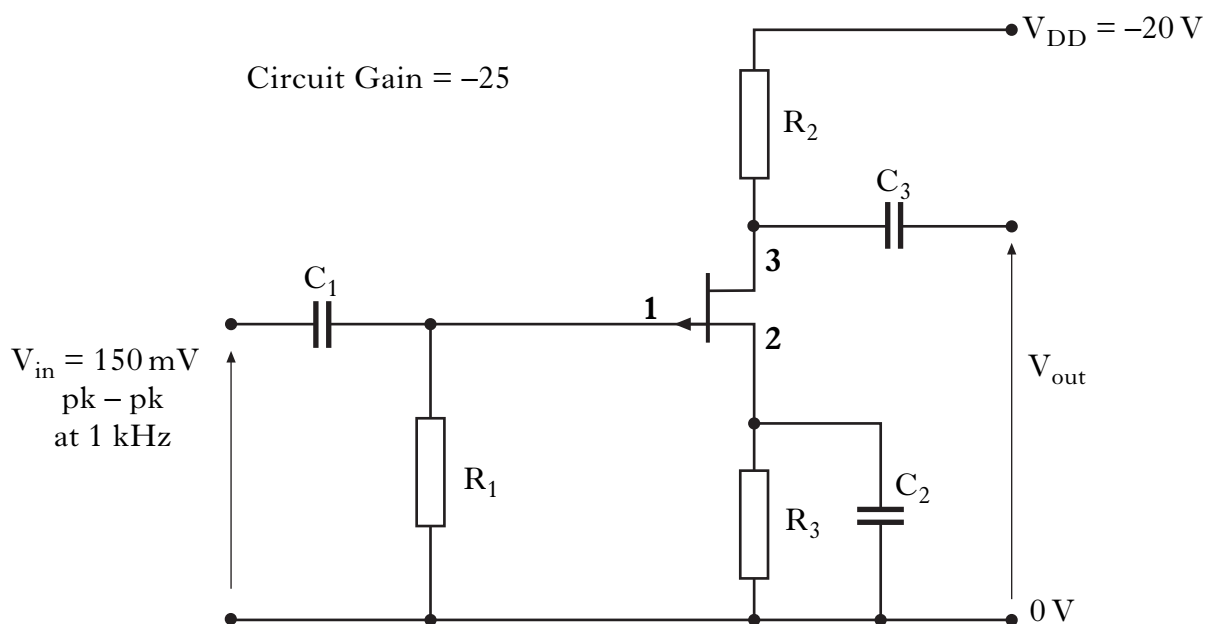


Figure Q10(e)(ii)

- (iii) For the circuit shown in Figure Q10(e)(ii), determine the pk - pk output voltage.

2

- (f) Identify the circuit shown in Figure 10(f) and state **one** application.

2

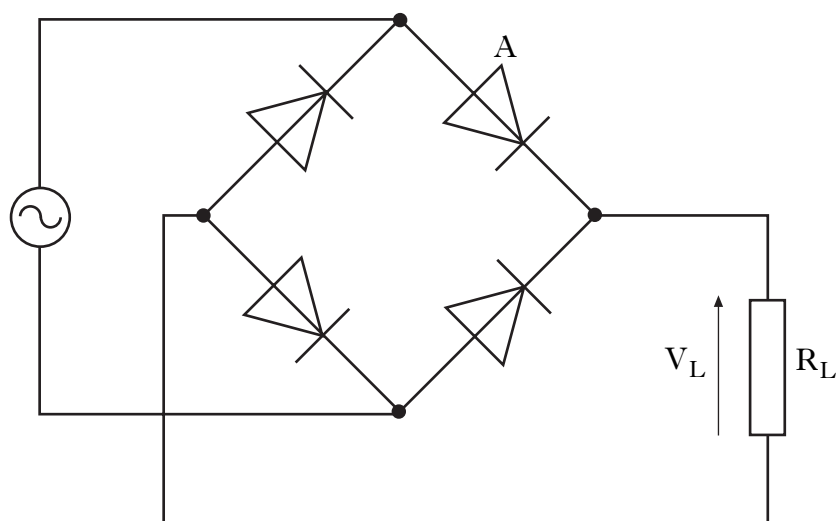


Figure Q10(f)

(25)

[Turn over

11. (a)

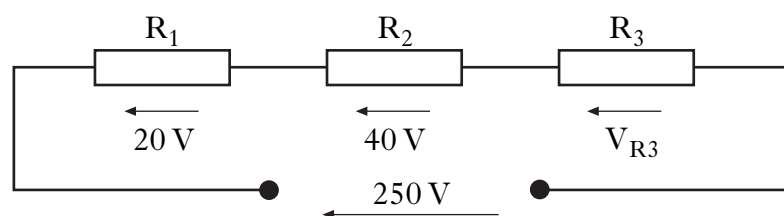


Figure Q11(a)

For the circuit shown in Figure Q11(a), determine the voltage drop  $V_{R3}$ .

1

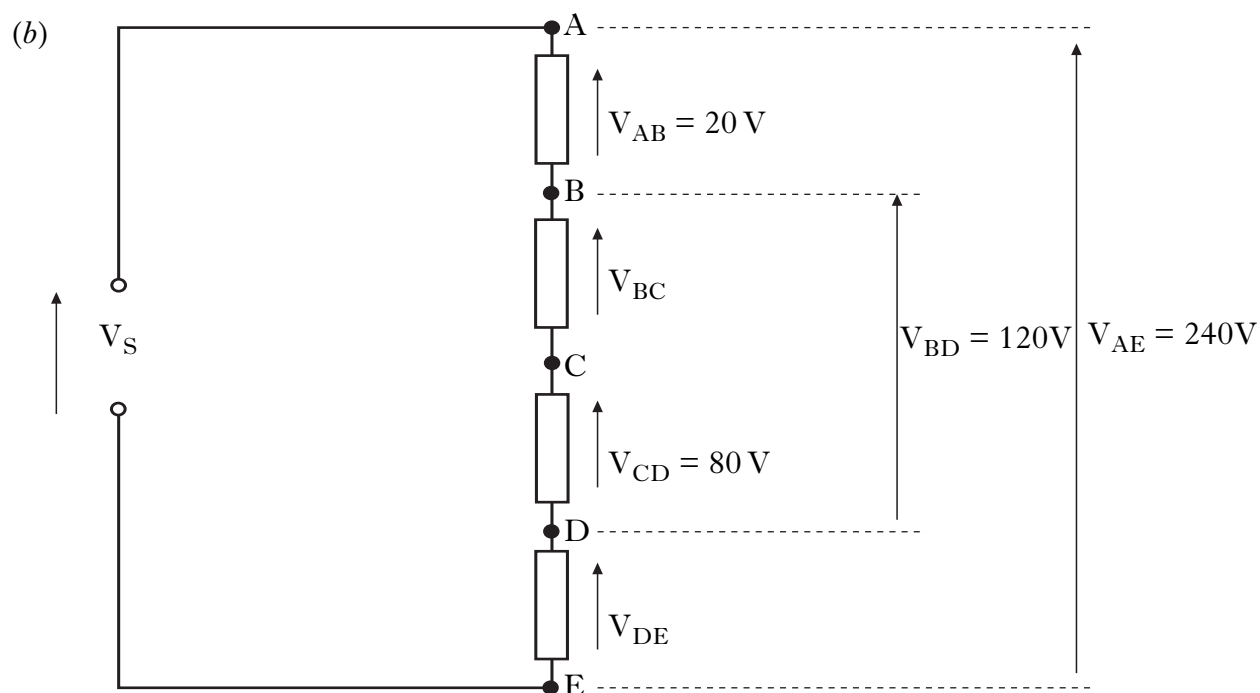


Figure Q11(b)

For the circuit shown in Figure Q11(b), determine the voltage drops:

(i)  $V_S$ ;

1

(ii)  $V_{BC}$ ;

1

(iii)  $V_{DE}$ .

1

(c)

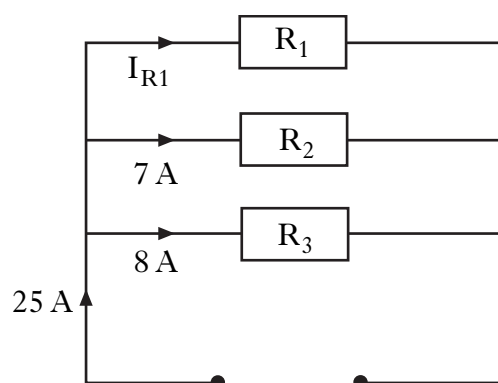


Figure Q11(c)

For the circuit shown in Figure Q11(c), determine the current  $I_{R1}$ .

1

## 11. (continued)

(d)

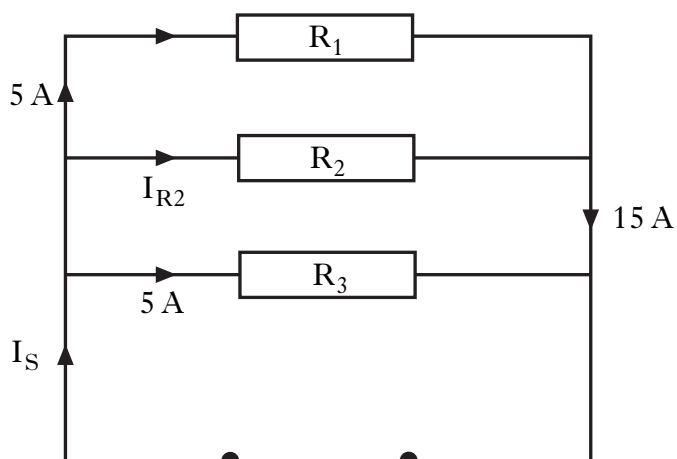


Figure Q11(d)

For the circuit shown in Figure Q11(d), determine:

- |                |          |
|----------------|----------|
| (i) $I_{R2}$ ; | <b>1</b> |
| (ii) $I_S$ .   | <b>1</b> |
- (e) A domestic heating system consists of four storage heaters,  $R_1$  to  $R_4$ , each with a 3 kW element. The circuit diagram, Figure Q11(e) shows how the heaters are connected.

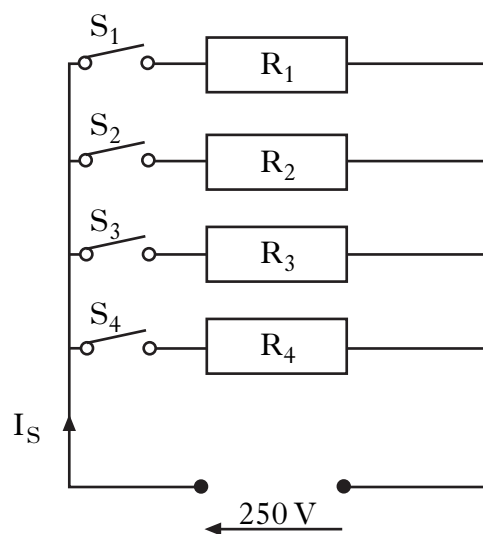


Figure Q11(e)

Assuming that all the switches,  $S_1$  to  $S_4$ , are closed, calculate:

- |  |          |
|--|----------|
| (i) the current in each heater element;            | <b>1</b> |
| (ii) the current taken from the supply;            | <b>1</b> |
| (iii) the resistance of each heater element;       | <b>2</b> |
| (iv) the total resistance of the circuit;          | <b>2</b> |
| (v) the total power dissipated in the circuit;     | <b>2</b> |
| (vi) the total energy (in kWh) consumed in 2 days. | <b>2</b> |

**11. (continued)**

- (f) The current produced by a generator can be determined by the formula

$$i = 250 \sin \theta \text{ amperes}$$

Determine:

- |   |             |
|---|-------------|
| (i) the maximum value of the current;   | <b>1</b>    |
| (ii) the value of the current generated when the angle between the generator's coil and the magnetic field is $60^\circ$ ;                            | <b>2</b>    |
| (iii) the rms value of the current.   | <b>1</b>    |
| <br>(g) A conductor of length 10 m and carrying a current of 10 A is placed in a magnetic field of 0.10 T.  |             |
| (i) Calculate the force on the conductor.   | <b>1</b>    |
| (ii) Calculate the force on the conductor when the magnetic field is increased to 0.4 T.  | <b>1</b>    |
| (iii) State what will happen to the force on the conductor if both the current in the conductor and the magnetic field are reversed at the same time. | <b>2</b>    |
|   | <b>(25)</b> |

12. (a) Add the following binary numbers:

(i)  $0111_2$  and  $0101_2$

2

(ii)  $1000_2$  and  $0110_2$

2

(b) For the following truth table:

A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

(i) identify the logic gate;

1

(ii) draw the BS symbol;

1

(iii) state the Boolean expression.

1

(c) Draw the logic diagrams for the following expressions using ANSI symbols.

(i)  $A.\overline{B}.C + \overline{A}.B.C + \overline{B}.\overline{C} = Z$

4

(ii)  $(\overline{P+Q+R}).(P+Q+\overline{R}).(P+\overline{Q}+R) = Z$

4

**[Turn over**

## 12. (continued)

(d) Construct the truth tables for the circuit in Figures Q12(d)(i) and Q12(d)(ii).

Determine from the truth tables which single logic gate could replace each circuit.

(i)

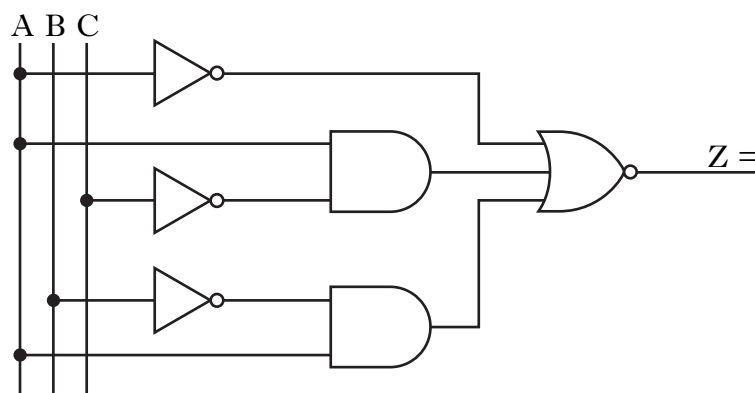


Figure Q12(d)(i)

5

(ii)

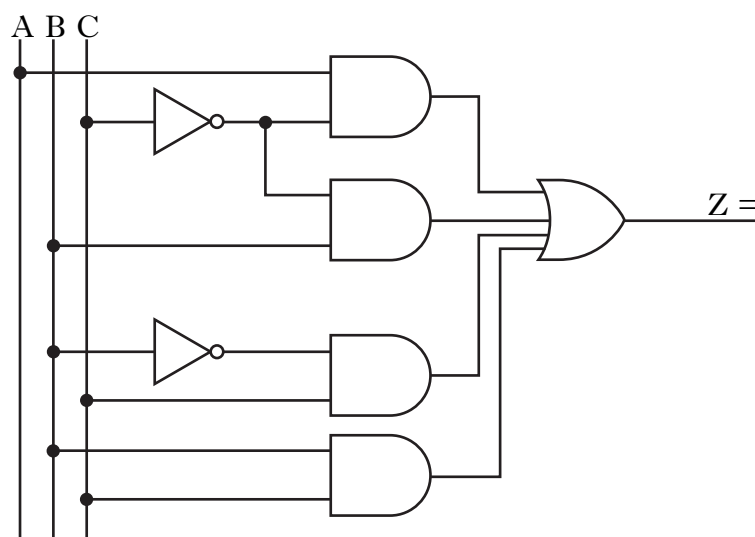


Figure Q12(d)(ii)

5  
(25)

[END OF QUESTION PAPER]

**[BLANK PAGE]**

**[BLANK PAGE]**



**X025/202**

---

NATIONAL  
QUALIFICATIONS  
2007

MONDAY, 4 JUNE  
9.00 AM – 11.30 AM

ELECTRONIC AND  
ELECTRICAL  
FUNDAMENTALS  
INTERMEDIATE 2  
Datasheets for Q5 and Q8




## Datasheet for Question 5


### LEDs

Diode Type	Part No	$I_F$ mA (max)	$V_F$ V (typ)	$V_R$ V (max)	Intensity @ 10 mA mcd		View Angle (deg)	Peak wavelength (nm)
					min	max		
Red	L424HDT	25	2	5	0.5	3.2	100	700
H E red	L424IDT	30	2	5	3.2	12.5	100	625
Pure orange	L424NDT	30	2	5	3.2	12.5	100	610
Green	L424GDT	25	2.2	5	1.3	8	100	565
Yellow	L424YDT	30	2.1	5	1.3	8	100	590

## Datasheet for Question 8

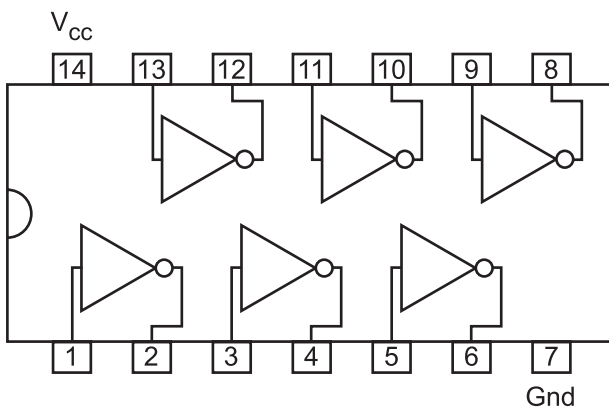

7404

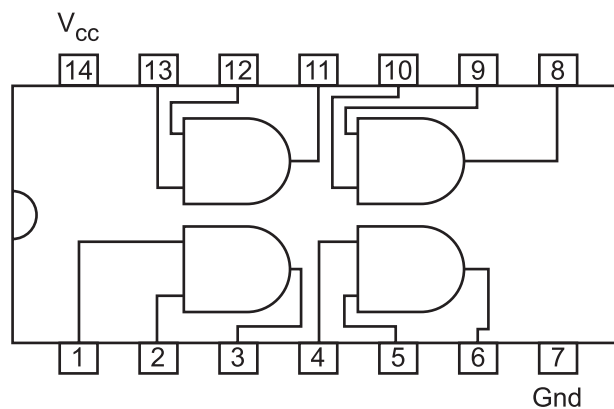

7408

[END OF DATASHEETS]