

--	--	--	--	--	--

	KU	RNA
Total Marks		

**4040/401**

NATIONAL  
QUALIFICATIONS  
2007

MONDAY, 30 APRIL  
1.00 PM – 2.15 PM

TECHNOLOGICAL  
STUDIES  
STANDARD GRADE  
General Level

**Fill in these boxes and read what is printed below.**

Full name of centre

Town

Forename(s)

Surname

Date of birth

Day Month Year

--	--	--	--	--	--	--	--

Scottish candidate number


--	--	--	--	--	--	--	--	--	--

Number of seat


- 1 Answer all the questions.
- 2 Read every question carefully before you answer.
- 3 Write your answers in the spaces provided.
- 4 Do **not** write in the margins.
- 5 Do **not** sketch in ink.
- 6 All dimensions are given in millimetres.
- 7 **Show all working and units where appropriate.**
- 8 Reference should be made to the Standard Grade and Intermediate 2 Data Booklet (2006 edition) which is provided.
- 9 Before leaving the examination room you must give this book to the invigilator. If you do not, you may lose all the marks for this paper.



[4040/401]

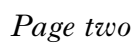


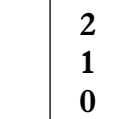- (b) **Draw** the Universal System Diagram.



3  
2  
1  
0

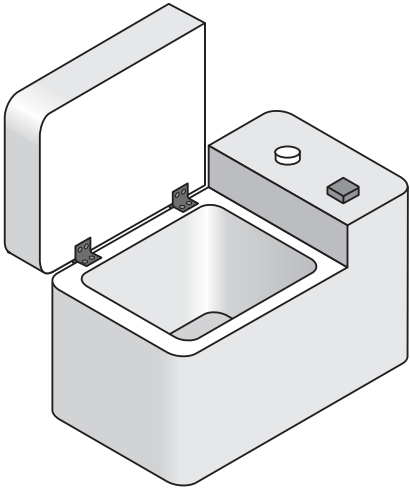2. A model of a bread making machine is operated by a microcontroller.




The sequence of operations for the breadmaker is shown below:

- the sequence begins when the start switch is pressed and the lid closed;
- the mixer motor runs for 10 seconds then stops;
- the heater switches on for 20 seconds then switches off;
- the sequence is reset.

Input Connection	Pin	Output Connection
	7	
	6	Heater
	5	Mixer motor
	4	
	3	
Lid sensor	2	
Start switch	1	
	0	

[Turn over

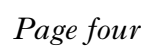(a) Complete the flowchart by adding the correct symbols and instructions. You should refer to the sequence and Data Booklet when answering this question.



2. (continued)

(b) With reference to the microcontroller connections and flowchart, complete the PBASIC program.

init:	let dirs = %11110000	_____
	let pins = 0	<i>'switch all pins off</i>
main:	if pin 1 = 0 then main	<i>'test pin 1</i>
label:	_____	<i>'test pin 2</i>
	high 5	<i>'switch on mixer motor</i>
	pause 10000	<i>'10 second delay</i>
	_____	<i>'switch off mixer motor, switch on heater</i>
	_____	<i>'20 second delay</i>
	low 6	<i>'switch off heater</i>
	_____	<i>'reset program</i>

(c) State the name of the microcontroller parts for each of the following functions.

(i) Function *Permanent memory where a program or data is stored*

Full name \_\_\_\_\_


(ii) Function *Temporary working memory of the microcontroller*

Full name \_\_\_\_\_

[Turn over

A diagram showing a side view of a vehicle door. A dashed line indicates the swing path of the door handle, which is shown in an open position. The handle is a vertical bar with a horizontal grip. The door is open, and the handle is in a vertical position, indicating it is in the 'open' position.

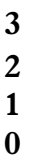(a) Complete the piping of the pneumatic circuit below.



Valve (A)	Valve (B)	Door position (open or closed)
0	0	
0	1	
1	0	
1	1	open

3. (continued)


The air supply between Valve (C) and Valve (D) is shown by a dashed line.

(c) State the name given to this type of air supply.

\_\_\_\_\_

(d) State the name of the pneumatic symbols.

(i)  \_\_\_\_\_

(ii)  \_\_\_\_\_

(e) State the **full name** of Valve (D).


\_\_\_\_\_

(f) State the name given to the **position** of the **piston** when the door is closed.

\_\_\_\_\_

(g) Calculate the air pressure to move the piston with a force of 800 N in the direction shown when the piston has an area of  $425 \text{ mm}^2$ .


Area =  $425 \text{ mm}^2$

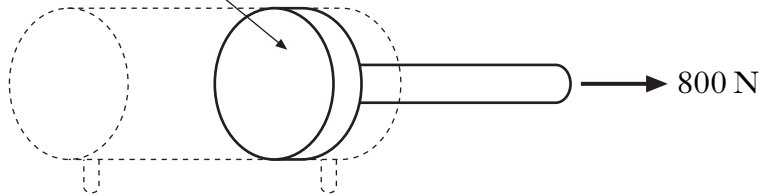

[Turn over

KU	RNA
1 0	
1 0	
1 0	
3 2 1 0	
1 0	
	2 1 0

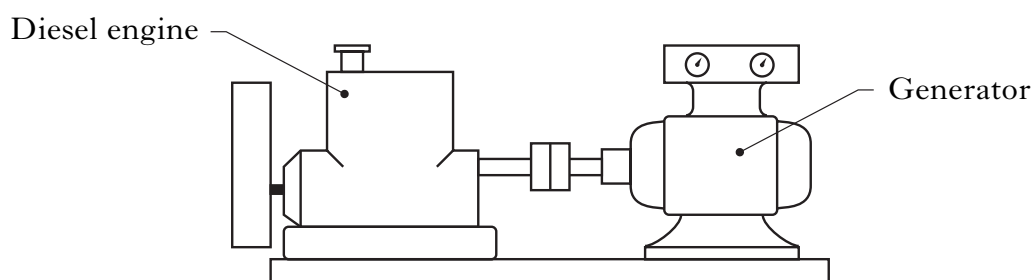
4. A diesel engine is used to drive a generator.



(a) Complete the diagram below by inserting the **main** input and output **energy**.



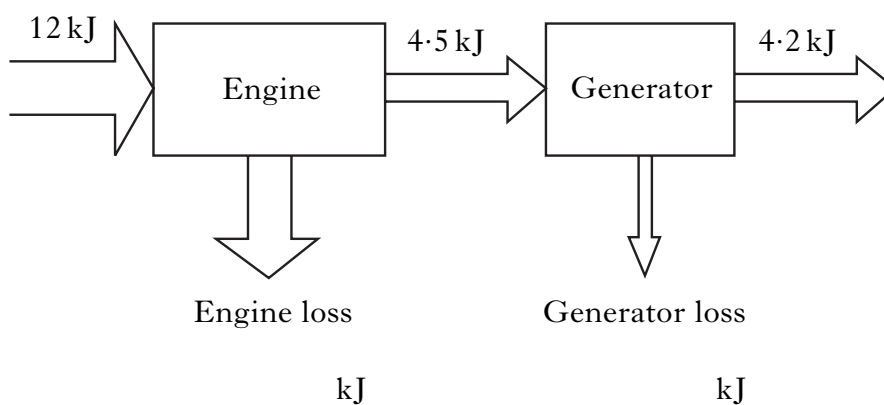(b) Calculate and complete the energy audit below.



(c) Complete the following sentence by using the list of phrases given.

*greater than*

*less than*


*equal to*

“The efficiency of all machines will be \_\_\_\_\_ 100% because the input energy is always \_\_\_\_\_ the output energy.






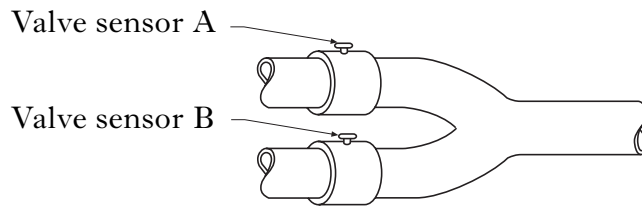5. An oil refinery process requires that just a single valve, X or Y, is open at any given time.



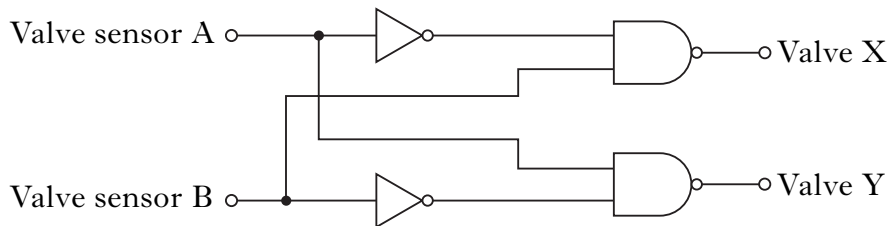Part of the logic circuit is shown below.



- (a) Using the Data Booklet, state the **full name** of the ICs required to construct the logic circuit.


**IC 1** Reference number – 7404

Full name \_\_\_\_\_

**IC 2** Reference number – 7400

Full name \_\_\_\_\_

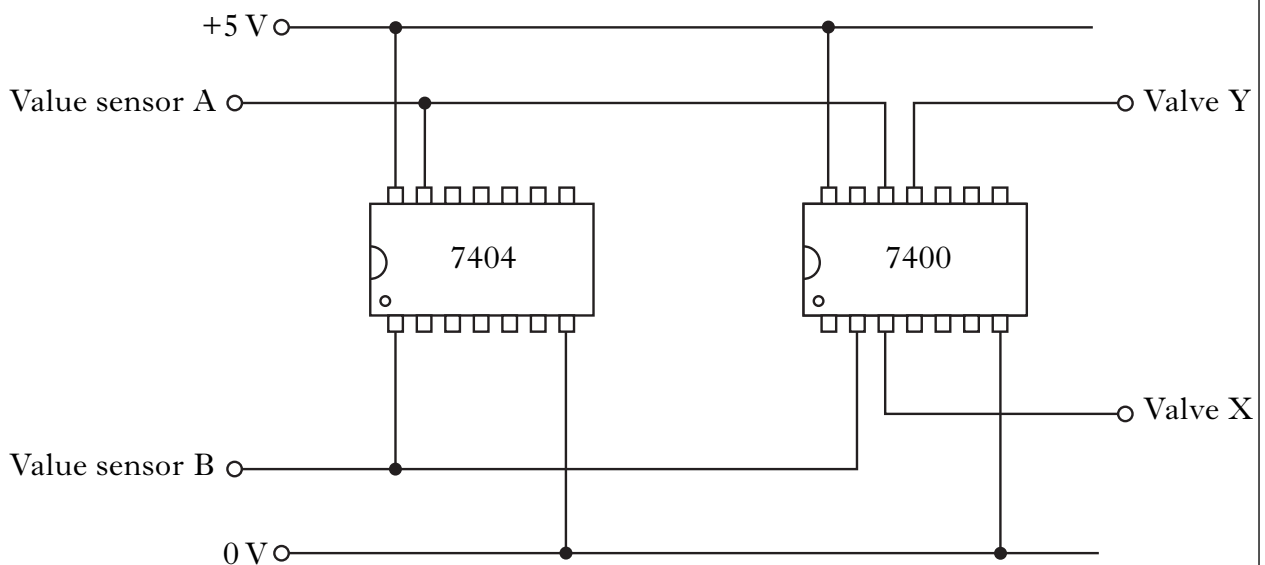- (b) Complete the wiring diagram below for the logic circuit.



2  
1  
0

5. (continued)

(c) A truth table for a logic gate is shown below.

C	D	Z
0	0	1
0	1	0
1	0	0
1	1	0

(i) State the name of the logic gate that the truth table represents.


\_\_\_\_\_

(ii) Sketch the logic symbol for this gate.

KU	RNA
1	
0	
2	
1	
0	

[Turn over

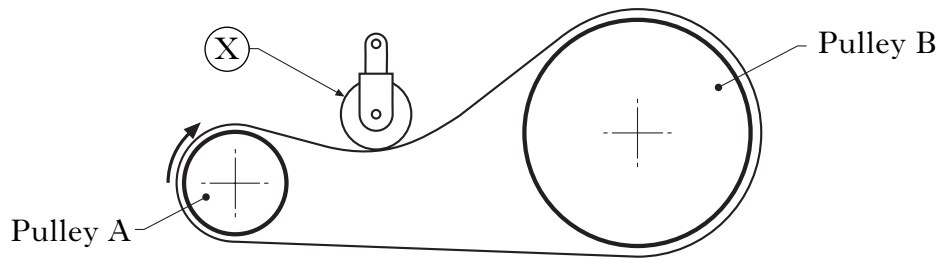6. An air compressor on a heavy goods vehicle is driven by a belt.



- (a) State the name of device (X) in the sketch above.

\_\_\_\_\_

Pulleys can rotate either **clockwise** or **anti-clockwise**.

Pulley A rotates clockwise, as shown in the diagram above.

- (b) State the direction of rotation of device (X) .

\_\_\_\_\_

Three different types of belts are shown below.

- (c) State the name of each belt.



- (i) \_\_\_\_\_ (ii) \_\_\_\_\_ (iii) \_\_\_\_\_

Friction is the resistance of one surface to move over another.

- (d) State **two** methods of **reducing** friction.


1 \_\_\_\_\_

2 \_\_\_\_\_

KU	RNA
1 0	1 0
3 2 1 0	2 1 0

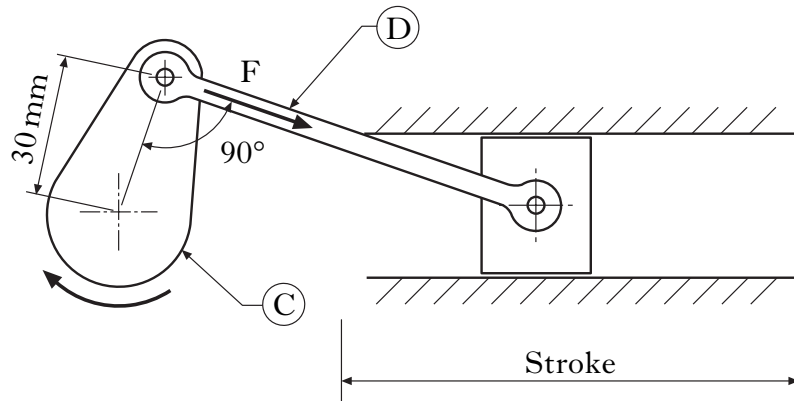6. (continued)

The mechanism shown below is used in the compressor.



(e) State the names of parts (C) and (D).

(C) \_\_\_\_\_ (D) \_\_\_\_\_


(f) Determine the length of **stroke** for the above mechanism.

\_\_\_\_\_


Part (C) has a radius of 30 mm and, as it rotates, the force **F** in part (D) is 250 N in the position shown.

(g) Calculate the torque.

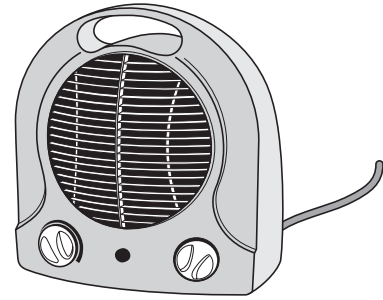7. A heater has variable temperature control.



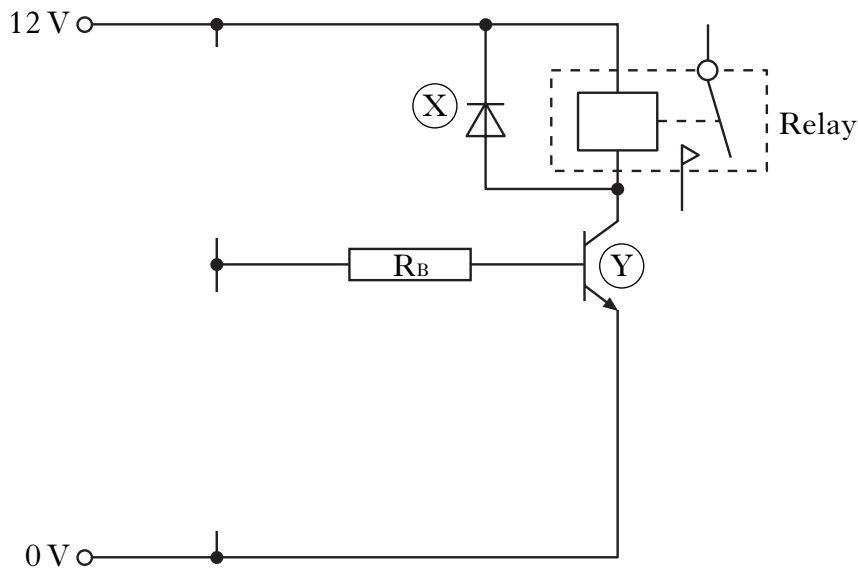An incomplete electronic circuit for the heater control is shown.



(a) (i) Complete the circuit above by inserting the symbol for a variable resistor and a thermistor to form a **cold sensor**.

(ii) State the name of the components (X) and (Y).

Component (X) \_\_\_\_\_

Component (Y) \_\_\_\_\_

(b) Determine, with reference to the Data Booklet, the resistance of the thermistor type 3 at 0 °C.


\_\_\_\_\_

KU	RNA
2	1
1	0
0	0
2	1
1	0
0	0
1	0
0	0

7. (continued)

- (c) The relay is part of a 110 V electrical circuit which is made up of component (1) and the heater connected in series. Component (2) is connected in parallel with the heater.

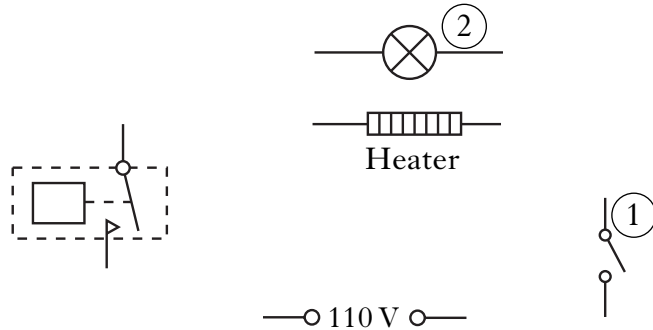- (i) Complete the wiring of this electrical circuit.



- (ii) State the name of components (1) and (2).

Component (1) \_\_\_\_\_

Component (2) \_\_\_\_\_

- (iii) State why a relay is required to switch on the heater circuit.

\_\_\_\_\_  
\_\_\_\_\_

- (d) The heater is rated at 3.3 kW operating at 110 V. Calculate:

- (i) the heater current;

- (ii) the resistance of the heater.

KU	RNA
	4 3 2 1 0
2 1 0	
	1 0
	2 1 0
	2 1 0

[END OF QUESTION PAPER]

**[BLANK PAGE]**