M			
	1		

/lark

NATIONAL QUALIFICATIONS 2013

TECHNOLOGICAL STUDIES INTERMEDIATE 2

TUESDAY, 21 MAY 9.00 AM - 11.30 AM

*	Х	0	3	e	5	1	1	0	1	*

X036/11/01

Full name of centre		Town
Forename(s)	Surname	Number of seat
Date of birth		
Day Month	Year Scottish cano	didate number
1 Answer all the questions in	Section A and any two ques	stions in Section B.
2 Read each question careful	ly before you answer.	
3 Write your answers in the s	paces provided.	
4 Show all working and unit	ts.	
5 Do not write in the margins		
6 Do not sketch in ink.		
7 Reference should be ma (2008 edition) which is prov	de to the Standard Grad ided.	le and Intermediate 2 Data Booklet
8 Before leaving the examina you may lose all the marks	tion room you must give this for this paper.	s book to the Invigilator. If you do not,
Use blue or black ink. Pencil n	nay be used for graphs and	diagrams only.





SECTION A

Attempt ALL questions (Total 60 marks)

1. A control diagram for the automatic positioning of a telescope is shown in Figure Q1.



* X 0 3 6 1 1 0 1 0 2 * Page two

[X036/11/01]

Image: transmission of the pressure is sensed The circuit shown in Figure Q2 uses AND control. (a) State the name of the pneumatic valve that is used to produce OR control. (a) Image: the symbol for this valve in the space below.	2. A pneumatic circuit used in a production line is shown in Figure Q2.	Marks	DO NOT WRITE IN THIS MARGIN
Figure Q2 (a) State the full name of the following pneumatic components. Component (\$)		5	
(a) State the full name of the following pneumatic components.	Figure Q2		
Component (\$) Valve (2) (b) Describe, using appropriate terminology, the operation of the pneumatic circuit. An increase in pressure is sensed	(<i>a</i>) State the full name of the following pneumatic components.		
Valve 2 2 (b) Describe, using appropriate terminology, the operation of the pneumatic circuit. An increase in pressure is sensed An increase in pressure is sensed The circuit shown in Figure Q2 uses AND control. (c) (i) State the name of the pneumatic valve that is used to produce OR control. (ii) Draw the symbol for this valve in the space below.	Component (5)		
(b) Describe, using appropriate terminology, the operation of the pneumatic circuit. An increase in pressure is sensed	Valve 2	2	
An increase in pressure is sensed An increase in pressure in the space below. An increase in pressure	(<i>b</i>) Describe, using appropriate terminology, the operation of the pneumatic circuit.		
Image: state of the symbol for this value in the space below. 1 (ii) Draw the symbol for this value in the space below. 1 (iii) Draw the symbol for this value in the space below. 1	An increase in pressure is sensed		
Image: state of the symbol for this value in the space below. 1 1 1 (8) 1			
Image: state of the symbol for this value in the space below. 1 1 1 (a) 1 (b) 1 (b) 1 (c) 1 <td></td> <td></td> <td></td>			
The circuit shown in Figure Q2 uses AND control. (c) (i) State the name of the pneumatic valve that is used to produce OR control. (ii) Draw the symbol for this valve in the space below. 1 (8)		4	
 (c) (i) State the name of the pneumatic valve that is used to produce OR control. (ii) Draw the symbol for this valve in the space below. 	Γhe circuit shown in Figure Q2 uses AND control.		
(ii) Draw the symbol for this value in the space below. 1 1 1 1 1 1 1 1 1 1 1 1 1	(c) (i) State the name of the pneumatic valve that is used to produce OR control.		
(11) Draw the symbol for this value in the space below. 1 (8)		1	
	(11) Draw the symbol for this value in the space below.		
		1	
		(8)	

Page three

[Turn over

3. The speed of the motor used in a ceiling fan is operated by a microcontroller. The flowchart and the input and output connections are shown in Figure Q3.



Figure Q3



Page four



Page five

MARGIN

Marks

4

4. The Boolean statement used to describe part of the operation of a coffee machine is shown.

$$(\overline{\mathbf{A}} \cdot \mathbf{B}) + (\mathbf{A} \cdot \mathbf{B}) = \mathbf{Z}$$

(*a*) Complete the truth table below, for the Boolean statement.

А	В	Z
0	0	
0	1	
1	0	
1	1	

(b) Complete, with reference to the Boolean statement, the logic diagram for the coffee machine using NOT, AND and OR gates.

Ао

οΖ

4

1 (9)

Во

The circuit is to be constructed from the 4000 series family of Integrated Circuits (ICs).

(c) State the name of this IC logic family.



Page six



Page seven

[Turn over

DO NOT WRITE IN THIS



3

1

2

6. A circuit used to warn when a vehicle is reversing is shown in Figure Q6.





- (*a*) Calculate:
 - (i) the equivalent resistance of the three lamps;

(ii) the total circuit resistance;

(iii) the total circuit current;



[X036/11/01]

Page eight





Page nine

7. A model railway uses a microcontroller to operate a barrier.





The operation of the system is shown below.

- When a train is sensed the barrier should lower.
- When a limit switch is pressed the barrier will stop.
- When the train is no longer sensed, wait for ten seconds.
- Barrier will rise.
- After three seconds the barrier will stop.
- Sequence will then repeat.



Page ten

DO NOT WRITE IN THIS Marks Margin

7. (continued)

Complete the flowchart for the barrier operation, with reference to the Data Booklet.



(7)

[Turn over



[X036/11/01]

Page eleven





Page thirteen

[X036/11/01]



Page fourteen

			Marks	WRITE THIS MARGI
. (0	contin	ued)		
(1	b) (i)	Determine the resistance of the LDR for a light level of 300 lux, with reference to the Data Booklet.		
			1	
	(ii)	State the full name for the LDR.		
			1	
C	Calculat	e:		
(4	c) (i)	the base current, I_B , when the current in the relay is 48 mA and the current gain, h_{FE} , is 80;		
			2	
	(ii)	the voltage V_1 , when the transistor is saturated.		
			2	
А	SPD7	relay is used in the circuit.		
(4	<i>d</i>) (i)	State the full name of this relay.	1	
	(ii)	Explain why a relay is required in the circuit.	I	
			1	
		[Turn over		
				. 1

Page fifteen

9. (continued)

A pneumatic cylinder used to clamp wood in place as it is being sawn is shown in Figure Q9(b).



Figure Q9(*b*)

(e) Calculate the clamping force of the piston, as it outstrokes, if it has a diameter of 30 mm and air is supplied at a pressure of 0.5 N/mm^2 .

2

DO NOT WRITE IN THIS

MARGIN

Marks



Page sixteen



Page seventeen

[Turn over



Page eighteen



10.	(co	ntinu	ied)	Marks	DO N WRITI THI MARC	OT E IN IS GIN
	(<i>e</i>)	State	e, for the wiring diagram shown in Figure $10(c)$:	ĺ		
		(i)	the full name of the following Integrated Circuits (IC), with reference to the Data Booklet;			
			7404			
			7408	2		
		(ii)	the name of the IC logic family used;			
				1		
		(iii)	a suitable value for $+V_{cc}$;			
				1		
		(iv)	the function of the dot on each IC.			
				1		
				(20)		



I

Page twenty



[X036/11/01

Page twenty-one

[Turn over

11. (continued)

A microcontroller is used to operate the lifting system. A siren sounds before the lift moves. The flowchart for the *Warning* sub-procedure and the input and output connections are shown in Figure Q11(b).



input connection	pin	output connection
	7	siren
	6	
	5	
	4	
	3	
	2	
	1	
	0	

Figure Q11(*b*)



[X036/11/01]

Page twenty-two

11.	(co	ntinued)	Marks	DO NO WRITE THIS MARG	OT IN S IN
	(<i>c</i>)	Write, the PBASIC program for the sub-procedure <i>Warning</i> , with reference to Figure $Q11(b)$ and the Data Booklet.			
		warning:			
			6		



Page twenty-three

[Turn over

1.	(coi	ntinu	led)	Marks	DO NOT WRITE I THIS MARGII
	For (<i>d</i>)	the s (i)	ub-procedure <i>Warning</i> : calculate the length of time for the sub-procedure;		
		(ii)	state the PBASIC command used to call the sub-procedure <i>Warning</i> in the main program.	1	
	(<i>e</i>)	Desc prog	ribe why sub-procedures are often used in PBASIC rams.	1	
	The	PB	ASIC program is stored in the EEPROM on the	1	
	(<i>f</i>)	(i)	State the full name of EEPROM.		
		(ii)	State one property of this type of memory.	1	
		(iii)	State one other type of memory found on a microcontroller.	1	
			[END OF SECTION B]	(20)	
			[END OF QUESTION PAPER]		

Page twenty-four

[X036/11/01]

ADDITIONAL SPACE FOR ANSWERS

DO NOT WRITE IN THIS MARGIN



[X036/11/01]

Page twenty-five

ADDITIONAL SPACE FOR ANSWERS

DO NOT WRITE IN THIS MARGIN



[X036/11/01]

 $Page\ twenty-six$

ADDITIONAL SPACE FOR ANSWERS

DO NOT WRITE IN THIS MARGIN



[X036/11/01]

 $Page\ twenty\text{-}seven$

[BLANK PAGE]

DO NOT WRITE ON THIS PAGE

Acknowledgement of Copyright Question 11 Image of Motorised Lift



[X036/11/01]

Page twenty-eight