



2011 Technological Studies

Standard Grade Credit

Finalised Marking Instructions

© Scottish Qualifications Authority 2011

The information in this publication may be reproduced to support SQA qualifications only on a non-commercial basis. If it is to be used for any other purposes written permission must be obtained from SQA's NQ Delivery: Exam Operations Team.

Where the publication includes materials from sources other than SQA (secondary copyright), this material should only be reproduced for the purposes of examination or assessment. If it needs to be reproduced for any other purpose it is the centre's responsibility to obtain the necessary copyright clearance. SQA's NQ Delivery: Exam Operations Team may be able to direct you to the secondary sources.


These Marking Instructions have been prepared by Examination Teams for use by SQA Appointed Markers when marking External Course Assessments. This publication must not be reproduced for commercial or trade purposes.

[BLANK PAGE]

Mark Allocation

1. A street lighting system is controlled automatically. When the outside light drops below a set level a lamp comes on.

(a) Complete the diagram below.

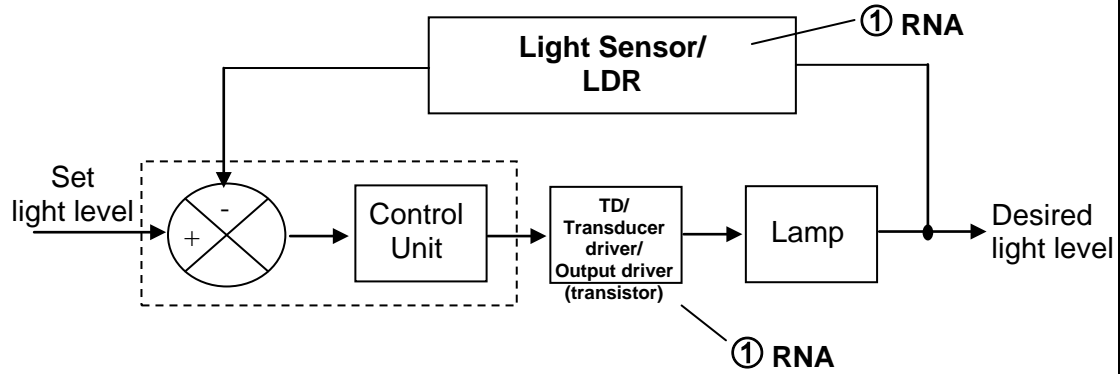

- (b) State the name of this type of diagram.

Control diagram

① KU

- (c) Describe the function of an error detector.


Compares the set level to the feedback level

① KU

① KU

Marks	
KU	RNA
	2 1 0
	1 0
	2 1 0

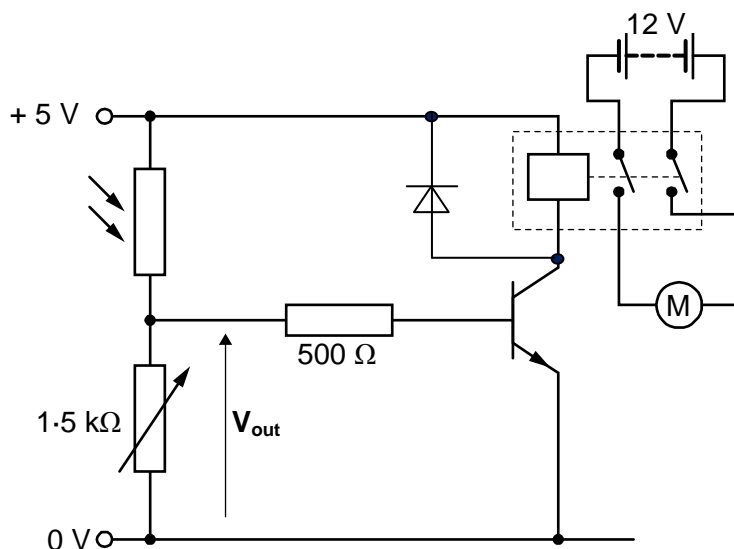2. A prototype electronic circuit is shown below.



(a) State the full name of an LDR.

Light Dependent Resistor

① KU

The variable resistor and the LDR form a voltage divider sub-system.

(b) Describe the operation of the **voltage divider sub-system**.

As the light level increases the LDR's resistance decreases.

As the light level increases V_{out} increases.

The variable resistor acts as a sensitivity control etc

① RNA for each correct descriptive statement up to 3.

(c) (i) Determine, with reference to the Data Booklet, the resistance of the LDR at 300 lux.

400 (-420)

(ii) Calculate V_{out} from the voltage divider sub-system at 300 lux.

$$V_{out} = \frac{R_1}{R_2} \times V_{CC}$$

$$= \frac{1500}{1900} \times 5$$

FTE \rightarrow

$$= 3.95 \text{ V} \quad \text{① RNA for answer from given working}$$

① RNA for substitution

Marks	
KU	RNA
1 0	3 2 1 0
	1 0
	2 1 0

2. (continued)

- (d) Complete the circuit diagram to show how a diode could be used to protect the transistor from back-voltage (e.m.f.).

① KU for diode symbol

① RNA for wiring

① RNA for orientation of diode


- (e) The transistor is fully switched on when V_{BE} is 0.7 V.

- (i) State the name given to this condition.

Saturated/saturation

① KU

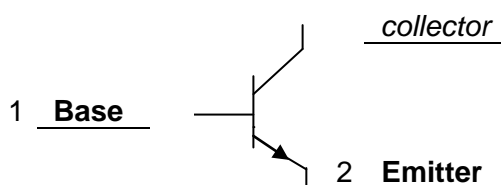- (ii) The symbol for a transistor is shown below. Label the connections **1** and **2**.



① KU for each correct

(① KU if names reversed)


- (f) (i) Explain why a relay is often used with electronic circuits.

It allows a low powered circuit to control a high powered circuit. There is no physical link between the circuits.

Control circuits can't work with very high currents

① KU for each correct answer up to 2

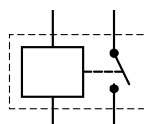
- (ii) A DPST (double pole single throw) relay is used in the circuit. State the names of the types of relays shown below.



SPST/

Single Pole Single Throw

① KU

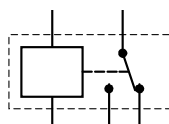

SPDT/

Single Pole Double Throw

① KU

- (iii) State the name of a relay that would allow forward **and** backward control of a motor.

DPDT/Double Pole Double Throw

① KU

Marks	
KU	RNA
1 0	2 1 0
1 0	
2 1 0	
2 1 0	
2 1 0	
1 0	

Marks	
KU	RNA
210	43210

Piston
30 mm diameter



Piston Rod
10 mm diameter

0.5 N/mm²

Page 7

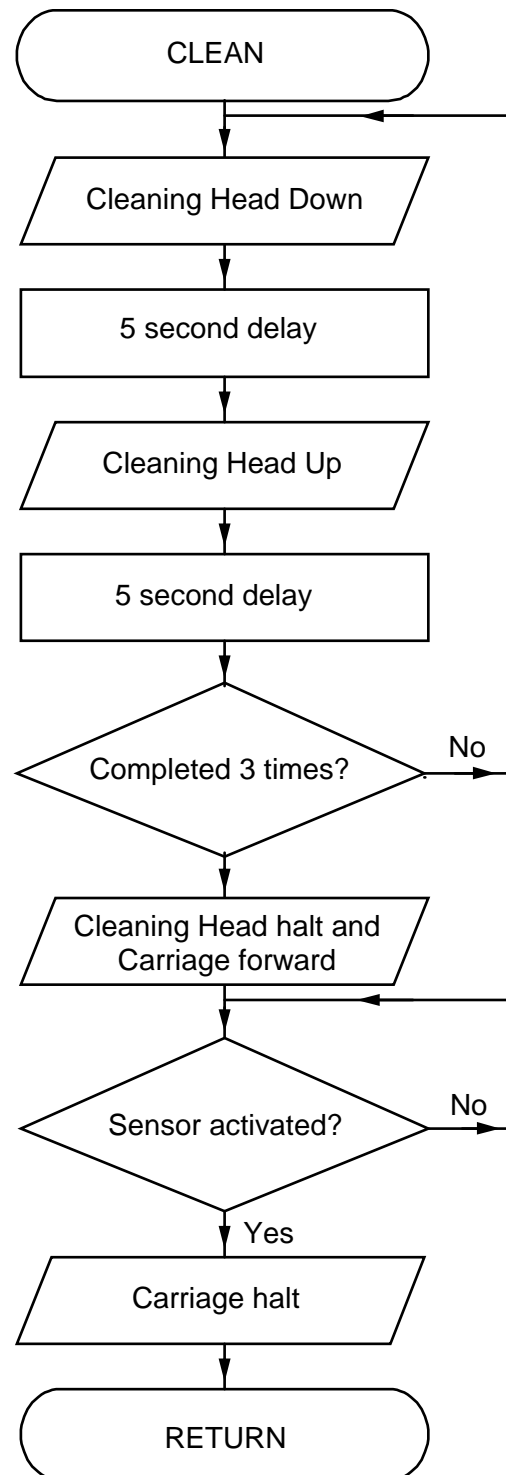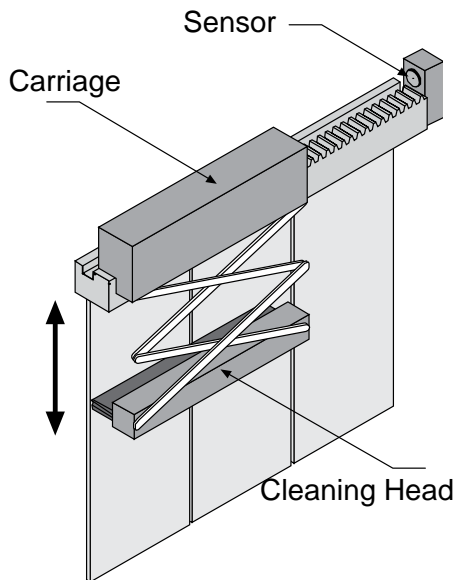4. A microcontroller is used to operate an automatic window cleaning system.

The flowchart for a sub-procedure used to control the system is shown below.



[illegible]

Input Connection	Pin	Output Connection
	7	Cleaning Head Up
	6	Cleaning Head Down
	5	Carriage forward
	4	
	3	
	2	
	1	
Sensor	0	

```

init:      symbol counter = b0
clean:     for counter = 1 to 3
OR { low 7 } — let pins = %0100000
   { high 6 } — pause 5000
OR { low 6 } — let pins = %10000000
   { high 7 } — pause 5000
alternative position for low 7
next counter
OR { high 5 } — let pins = %00100000
   { low 7 } —
label:      if pin0 = 0 then label
OR { let pins = 0 } — let pins = %00000000 or low 5
return
  
```

① RNA
① RNA
① RNA
① RNA
① RNA
① RNA for both

Page 9

Marks	
KU	RNA
1 0	
2 1 0	
2 1 0	

5. (continued)

- (c) Explain why it is important to make systems as efficient as possible.

Reduces energy consumption

Reduces cost of running system etc

① KU

10

Electrical energy can be generated from a variety of different sources.

- (d) (i) State **two** examples of **finite** energy sources.

1 Coal/gas/oil

① KU each up to 2

2
1
0

2

- (ii) Explain the **advantages** (other than cost) of using **renewable** energy source.

Energy source can be replenished/won't run out


Reduces pollution/greenhouse gas etc

Uses less resources

① KU each up to 2

2
1
0

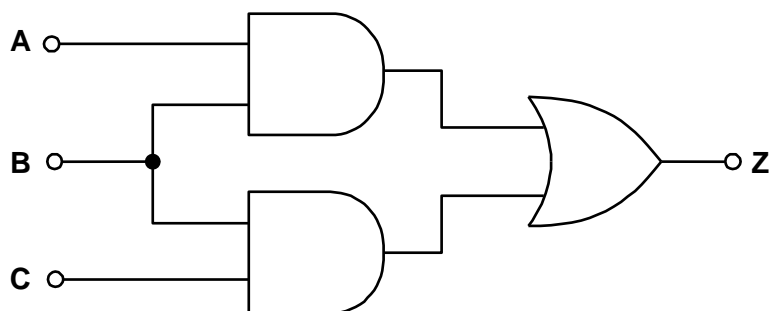6. The following logic diagram is required for an electronic alarm system.



- (a) Develop the Boolean expression for **Z**, in terms of **A**, **B** and **C**.

$$Z = (A \bullet B) + (B \bullet C)$$

① RNA for ANDing inputs

① RNA for OR conditions

$$\text{Alt } (\bar{A} \bullet B \bullet C) + (A \bullet \bar{B} \bullet C) + (A \bullet B \bullet C)$$

- (b) Complete the truth table below for the logic diagram.

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


① RNA each correct entry

Marks	
KU	RNA
	2 1 0
	3 2 1 0

Marks	
KU	RNA
1 0	
4 3 2 1 0	

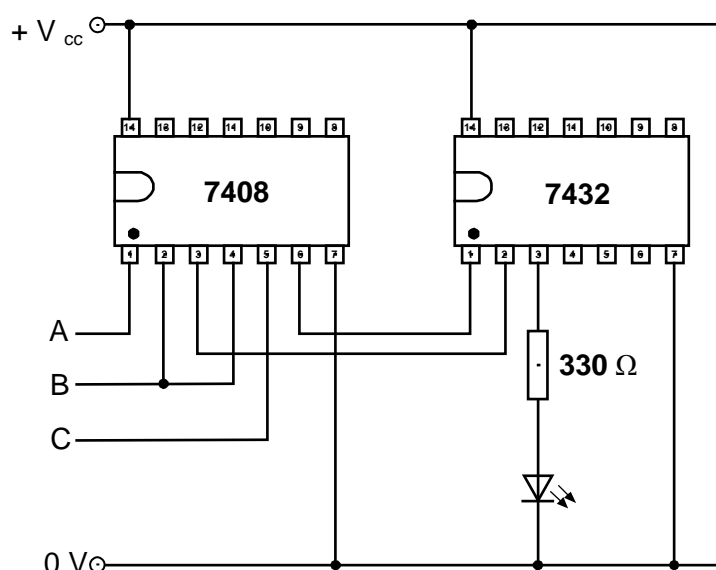6. (continued)

A wiring diagram for the circuit is shown below.



- (c) State why a resistor is placed in series with an LED.

Protects the LED (from large current)

① KU

- (d) The following table compares characteristics of TTL and CMOS.

Complete the table to match the characteristics to the correct Integrated Circuit (IC) family.

Characteristic	TTL	CMOS
Large fan out		✓
Higher power consumption	✓	
Easily damaged by static electricity		✓
Faster switching speed	✓	
Can use supply voltages from 3-18 V		✓

① KU for each correct single entry

7. Manufacturing companies often use microcontrollers instead of hardwired electronic circuits.

(a) State the full name of EEPROM as used in a microcontroller.

Electrically Erasable Programmable Read Only Memory

(b) Complete the following table to describe the function and a characteristic of the named microcontroller sub-systems.


Name	Function	Characteristic
ROM	<i>Stores PBASIC language for microcontroller operations.</i>	<i>Data remains after power is switched off.</i>
RAM	Stores data required when running the program.	Data will not remain when power is removed.
EEPROM	Stores the program.	Data remains after power is switched off. Data can be re-written.

① KU for each correct entry

Marks	
KU	RNA
1 0	
4 3 2 1 0	

Marks	
KU	RNA
210	3210
10	
10	

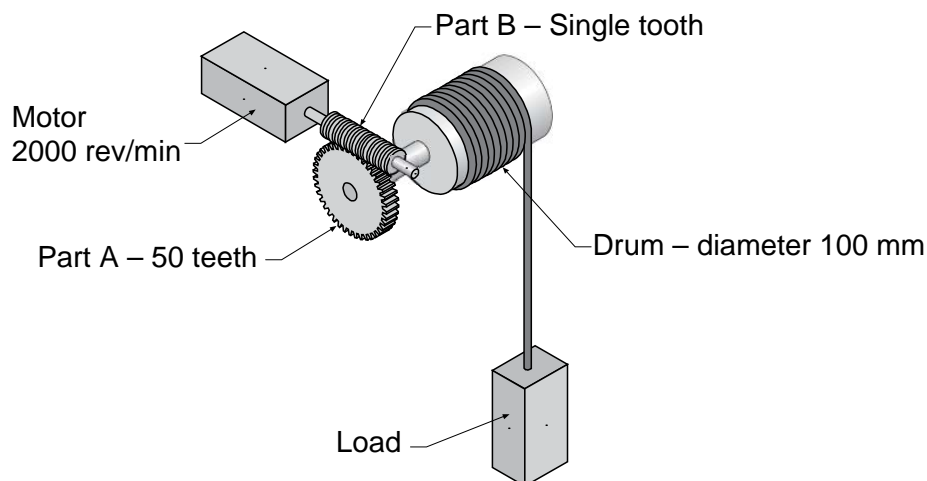(c) (i) Calculate the **linear** speed of the load as it is raised. (Ignore the thickness of the rope.)



<p>Speed of Drum $2000 \times 1 = 50 \times X$</p> <p style="margin-left: 150px;">$X = \frac{2000}{50}$</p> <p style="margin-left: 150px;">$= 40 \text{ rev/min}$</p>	<p>$\text{cir} = \pi d$</p> <p style="margin-left: 20px;">$= 3.14 \times 0.1 \text{ m}$</p> <p style="margin-left: 20px;">$= 0.314 \text{ m}$ ① RNA for circumference</p> <p style="margin-left: 20px;">① RNA for drum speed</p>
--	--

Speed of Load **Drum speed × Circumference**

= 40 × 314

= 12560 mm/min

OR

= 0.2 m/s

① RNA for answer from working

- (ii) State the name of the two parts of the mechanism that links the motor and the drum.

Part A **Wheel** ① KUPart B **Worm** ① KU

① KU total if answers reversed

- (d) State the name of a mechanism that could be used to convert:

- (i) rotational to linear motion:

Rack & Pinion ① KU

- (ii) reciprocating into rotational motion.

Crank & Slider ① KU