

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATIONS 2003

**ANALYSIS OF CIRCUITS**

Friday, 30 May 10:00 am

Time allowed: 2:00 hours

There are **FIVE** questions on this paper.

Answer **THREE** questions.

Any special instructions for invigilators and information for  
candidates are on page 1.

**Corrected Copy**

Examiners responsible      First Marker(s) :      R. Spence  
                                  Second Marker(s) : G. Weiss


**Special information for Invigilators:**      **none**

**Information for candidates:**


**For Question 2, a separate sheet is available on which waveforms can be drawn. If used, this sheet should be tied within the answer book.**

## The Questions

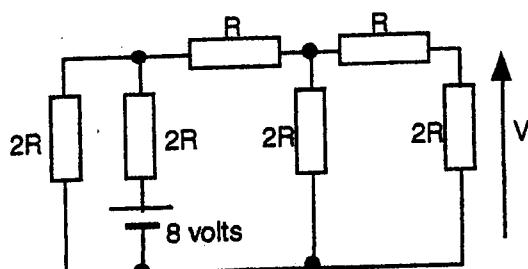
1. Preferably by inspection, but with brief explanation, find the value of the voltage  $V$  in each of the five circuits shown below.




(a) [5]

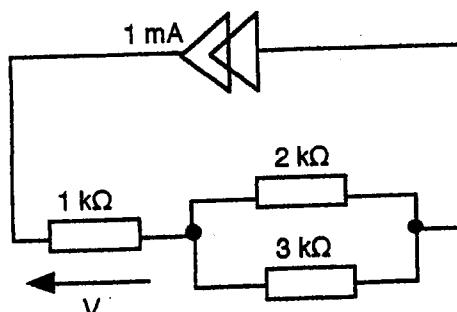


(b) [3]

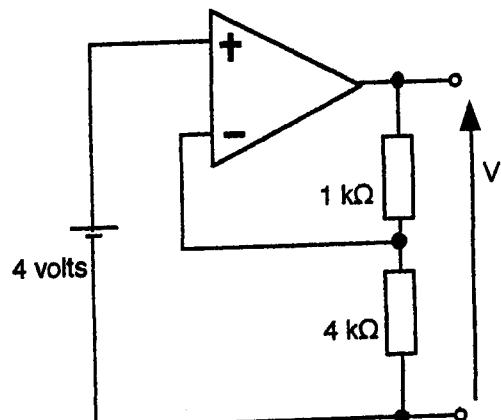

(c) [4]

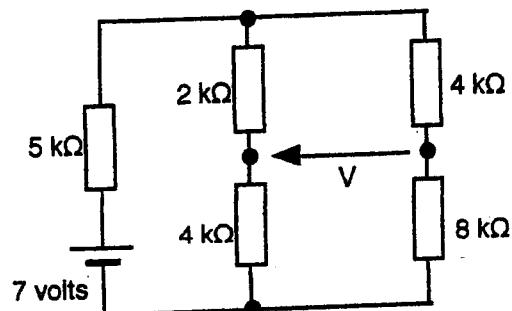


(d) [4]

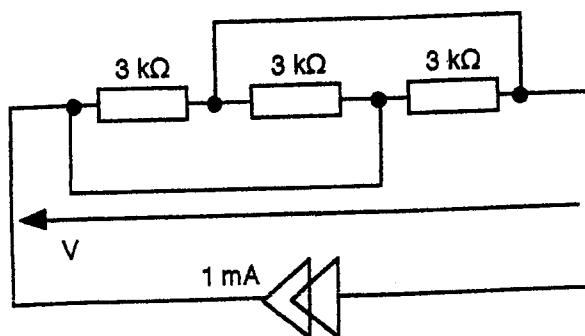

(e) [4]

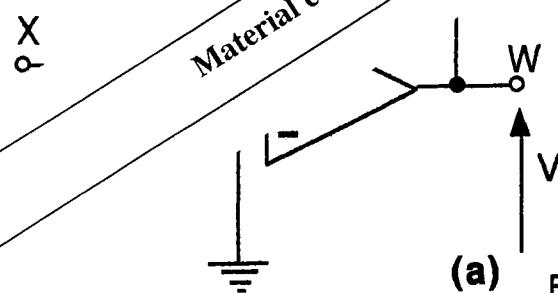2. The output voltage of the opamp in the circuits of Figure 2 saturates at  $\pm 10$  V.
- The voltage waveform  $V_i$  shown below (and repeated on a separate sheet) is applied to terminal X in the circuit of Figure 2a. Under the assumption that the value of 10 Volts at  $t=0$ , derive the waveform of the voltage  $v_o$  from  $t=0$  to  $t=20$  ms and plot it to the same scale. [10]
  - Terminal W is now connected to terminal Y. The voltage waveform  $V_i$  is again applied to terminal X. Derive the waveform of the voltage at terminal Z. [10]



(a)


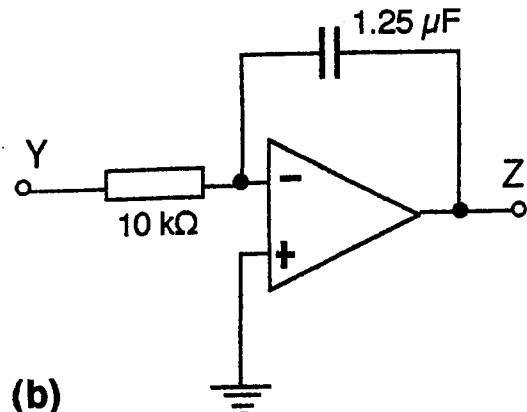


Figure 2 (b)

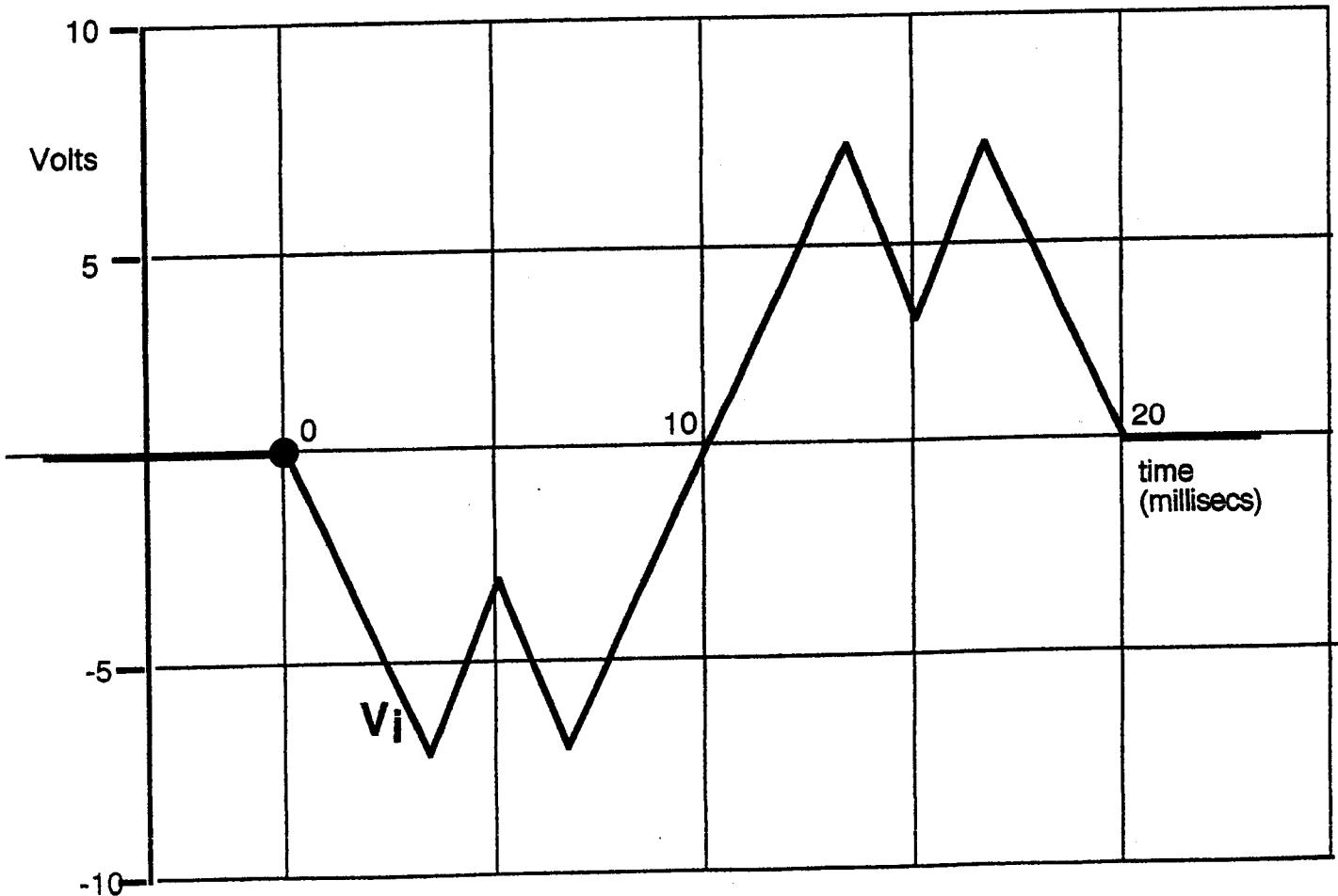

3. (a) Measurements have been made on a circuit comprising the series connection of a resistor, a capacitor and an inductor. The measured magnitude of the impedance of the series connection is plotted against frequency in Figure 3a. Estimate, with explanation, the capacitance of the capacitor, the inductance of the inductor and the combined series resistance of the resistor and inductor.

[8]

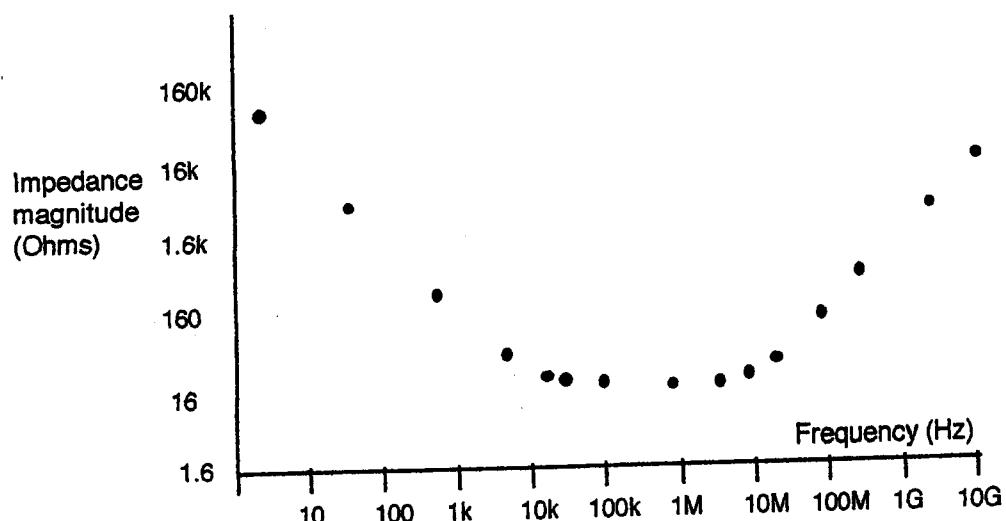


Figure 3a

- (b) In the circuit of Figure 3b,  $V_s$  is a sinusoidal voltage of radian frequency  $\omega$ . Derive an expression for the complex voltage  $V$  as a function of  $R$ ,  $L$ ,  $C$  and the radian frequency  $\omega$ . Hence show that  $V=0$  if  $R = (L/C)^{0.5}$ . Show that, if this relation between  $R$ ,  $L$  and  $C$  holds, the current supplied by the source is in phase with  $V_s$ .

[12]

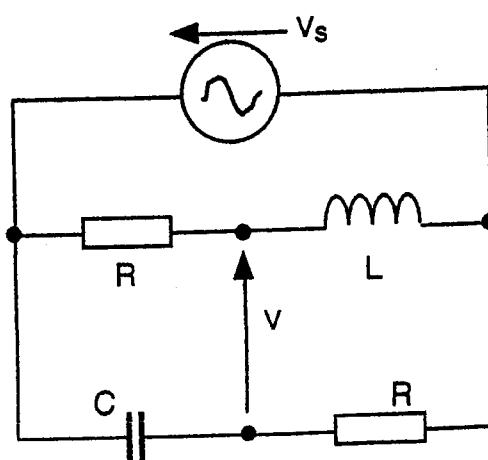


Figure 3b

4. As shown schematically in Figure 4a, the output of a linear amplifier of voltage  $V$  is connected to the input of a feedback circuit of voltage gain  $B$ . The voltage  $V$  and  $B$  are complex and they depend upon the frequency of the signal. The output of the feedback circuit is connected to the input of the amplifier.
- (a) Under the assumption that the gains  $A$  and  $B$  are non-negative, derive Barkhausen's criterion for the existence of sustained sinusoidal oscillation. Express the criterion in terms of  $A$  and  $B$ , and also in terms of the magnitude and phase of  $A$  and  $B$ . [4]
- (b) A circuit designer, in proposing the design of a Wien oscillator, has made a mistake in the circuit of Figure 4b. What mistake has been made? [8]
- (c) Using the information given in Figure 4b, and no others, draw the diagram of a circuit which will produce sustained sinusoidal oscillation. [4]
- (d) Use the values of  $R$  and  $C$  to ensure oscillation of your new circuit at a frequency of 10 Hz. [4]

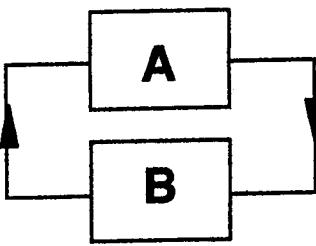


Figure 4a

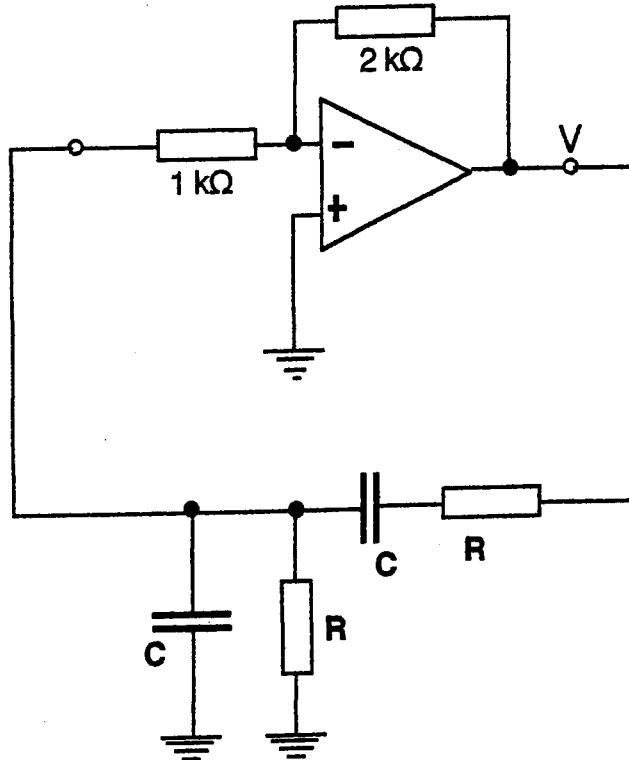


Figure 4b

5. (a) For the circuit of Figure 5, use the Superposition Principle to calculate the voltage  $V_o$ .

[10]


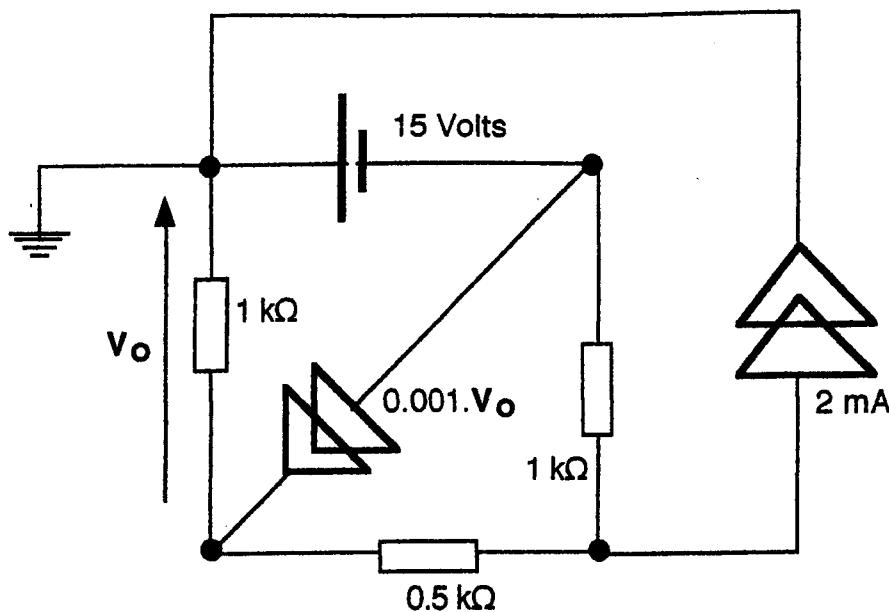


Figure 5

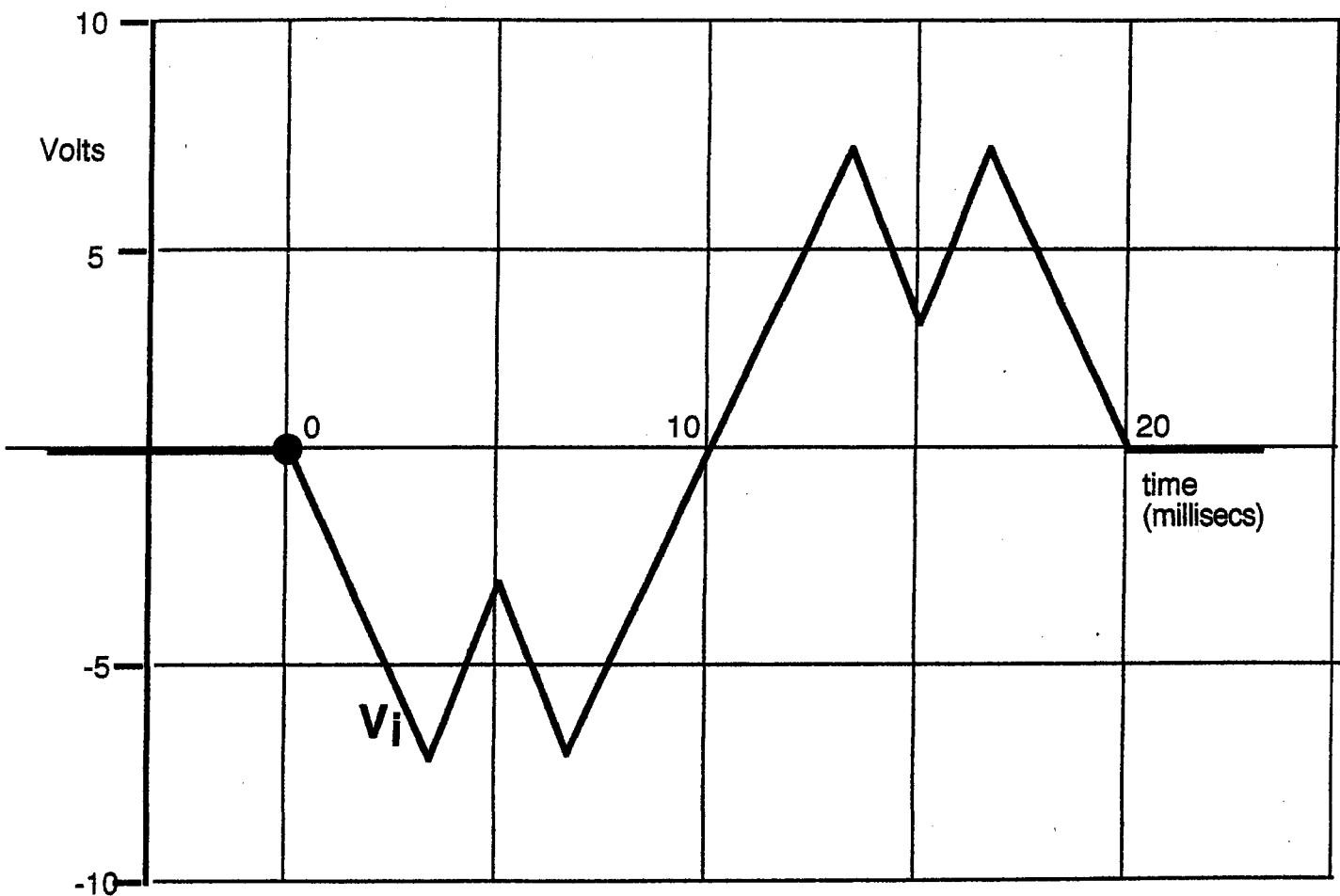- (b) Derive the nodal voltage equations relating the nodal voltages of the circuit of Figure 5 to the independent sources. Solve these equations to find the value of the voltage  $V_o$ .

[10]


Supplementary sheet for Question 2. To be tied inside the Answer Book



# Analysis of Circuits 2-007

## Answer 1

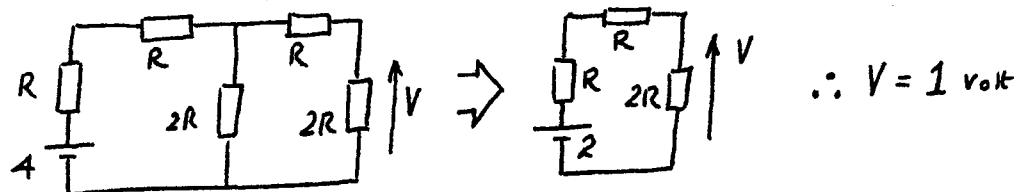(a) From the left, progressively represent by a Thevenin Equivalent Circuit.



(b) Apply Ohms Law to the  $1\text{k}\Omega$  resistor:

$$V = RI = 1\text{k}\Omega \times 1\text{mA} = 1\text{ Volt}$$

(c)  $V_- = 4$  Volts, therefore by voltage divider action  $V = 5$  Volts

(d) Because ratio of  $2\text{k}\Omega$  to  $4\text{k}\Omega$  is same as  $4\text{k}\Omega$  to  $8\text{k}\Omega$ ,  $V = 0$


(e) There are three  $3\text{k}\Omega$  resistors connected in parallel, with a combined resistance of  $1\text{k}\Omega$ . Ohms Law gives  $V = 1\text{k}\Omega \times 1\text{mA}$   
 $= 1\text{ Volt}$ .

## Answer 2

(a)

Circuit of Figure 2a is a Schmitt Trigger.

Calculate threshold values of  $V_i$ :

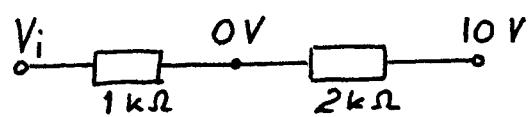

For zero voltage at +ve input

when  $V = 10$  (see circuit at right)

$V_i = -5$  Volts. Similarly, when  $V = -10$ , threshold for  $V_i$  is +5 Volts.

When  $V_i$  first falls below -5 V at  $t = 2.5 \text{ ms}$ ,  $V$  switches from 10 V to -10 V.

Later, when  $V_i$  first reaches +5 V,  $V$  switches back to +10 Volts.

(see waveform of  $V$  plotted on attached sheet)

(b)

Figure 2b is the circuit of an integrator.

Current into capacitor when  $V = 10$  Volts is  $10/10 \text{ k}\Omega = 1 \text{ mA}$

Capacitor current  $i = -C \frac{dV_Z}{dt}$  so  $10^{-3} = -1.25 \cdot 10^{-6} \cdot \frac{dV_Z}{dt}$

giving  $\frac{dV_Z}{dt} = -\frac{1}{1.25}$  volts per millisecond.


Hence when  $t = 2.5 \text{ ms}$ ,  $V_Z = -2$  Volts.

When  $V = -10$ ,  $\frac{dV_Z}{dt} = +\frac{1}{1.25}$  volts/millisecond.

Hence between  $t = 2.5 \text{ ms}$  and  $t = 12.5 \text{ ms}$ ,  $V_Z$  increases linearly by 8 volts to 6 volts.

From  $t = 12.5 \text{ ms}$  to  $t = 20 \text{ ms}$ ,  $V_Z$  decreases by 6 volts to zero.

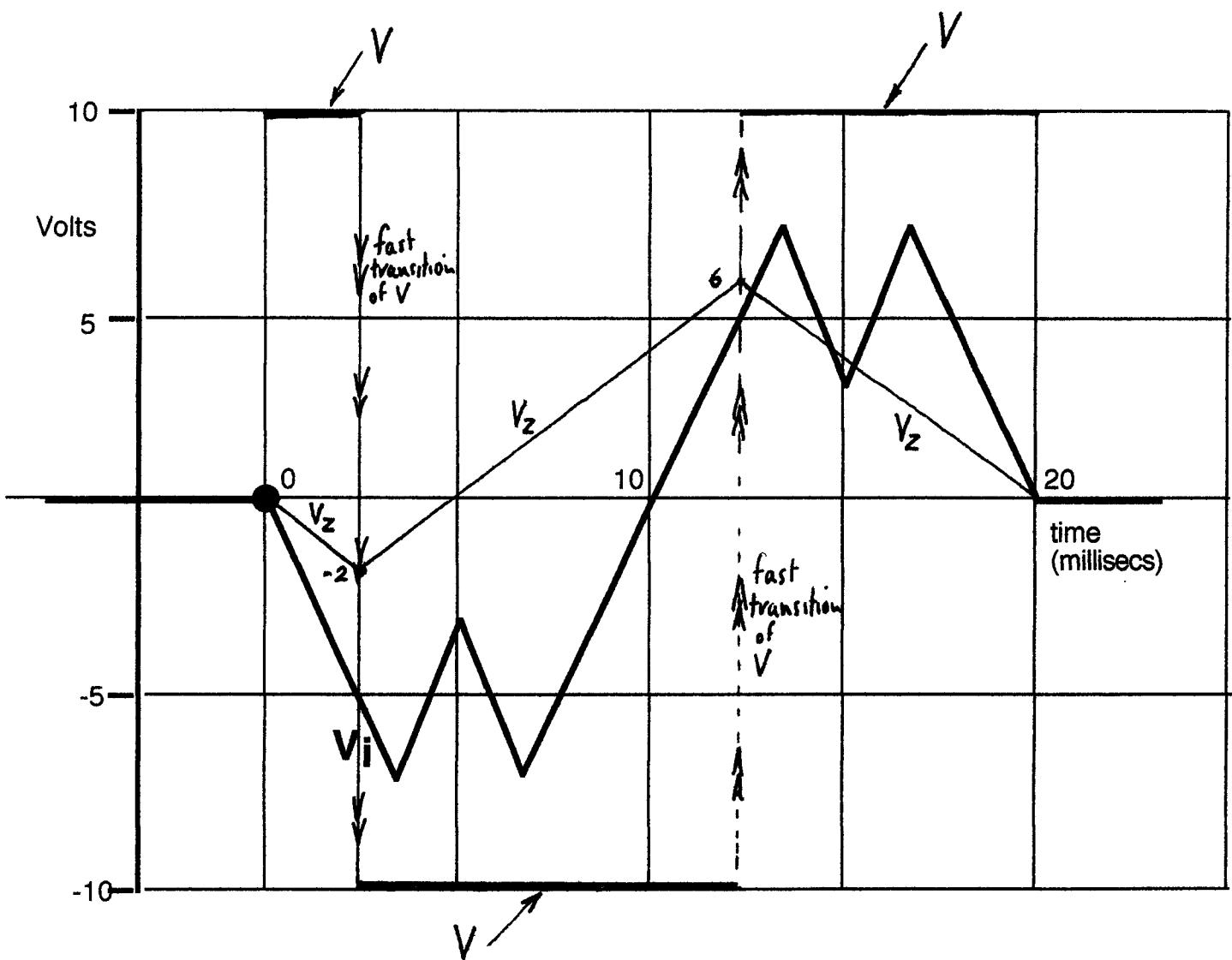
(see waveform of  $V_Z$  plotted on attached sheet)



### Answer 3

(a)

Draw the asymptotes as shown on right

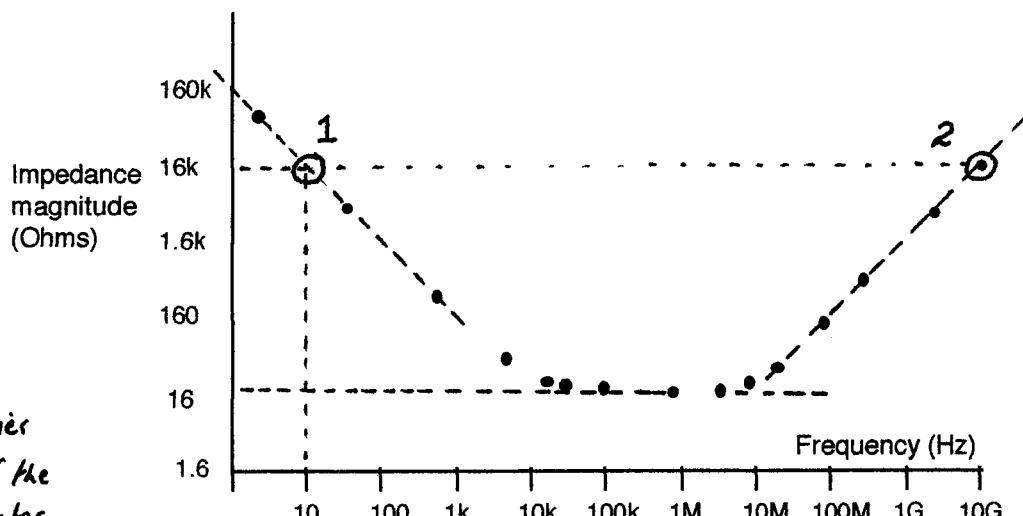

At low frequencies the impedance of the capacitor dominates.

Take the sample point 1

Figure 3a

$$|Z| = 16 \text{ k}\Omega, \omega = 2\pi \cdot 10 \text{ r/s} \therefore C \approx \frac{1}{\omega |Z|} = \frac{1}{2\pi \cdot 10 \cdot 16 \cdot 10^3} \approx 1 \mu\text{F}$$

At high frequencies the inductor dominates. Take sample point 2

$$|Z| = 16 \text{ k}\Omega, \omega = 2\pi \cdot 10^{10} \text{ r/s} \quad L \approx \frac{|Z|}{\omega} = \frac{16 \cdot 10^3}{2\pi \cdot 10^{10}} \approx 0.255 \mu\text{H}$$

At mid frequencies, resistance of resistor dominates. From asymptote  $R = 16 \Omega$

(b) By voltage divider principle (see circuit at right)

$$V_A = \frac{R}{R + j\omega L} V_s \quad V_B = \frac{j\omega C}{R + j\omega C} V_s$$

$$\text{So } V = V_B - V_A = V_s \left[ \frac{1}{1 + j\omega CR} - \frac{1}{1 + j\omega L/R} \right]$$

Thus,  $V = 0$  if  $CR = L/R$  i.e.,  $R = \sqrt{L/C}$

$$\text{Current in upper branch} = \frac{V_s}{R + j\omega L} \quad \text{Current in lower branch} = \frac{V_s}{R + j\omega C}$$

$$\begin{aligned} \text{So total current supplied by source} &= V_s \left[ \frac{1}{R + j\omega L} + \frac{1}{R + j\omega C} \right] \\ &= V_s \left[ \frac{R + j\omega C + R + j\omega L}{R^2 + \frac{L}{C} + j(LR - RC)} \right] = \frac{V_s}{R} \left[ \frac{2R + j(\omega L - 1/\omega C)}{R + jCR + j(\omega L - 1/\omega C)} \right] \end{aligned}$$

Because  $\frac{L}{CR} = R$ , the ratio of imaginary to real part is the same in both numerator and denominator, the current supplied by source is real:  
i.e., it is in phase with  $V_s$

## Answer 4

- (a) Assume a sinusoidal voltage at the input to A, and represented by a complex number  $V$ , causing an output voltage  $AV$  which is applied to the input of B. If the output of B, equal to  $ABV$ , is identical with  $V$ , oscillation at the frequency of  $V$  will be sustained. Thus, for sustained oscillation,

$$AB = 1 \quad \text{---} \quad (1)$$

this is the Barkhausen Criterion. Mindful of the fact that both A and B are complex we can write (1) as


$$|A| \angle A \cdot |B| \angle B = 1 \angle 0^\circ$$

giving  $|A \parallel B| = 1$  the "magnitude criterion"

and  $\angle A + \angle B = 0^\circ$  the "phase criterion"

- (b) The circuit of Figure 4b will NOT sustain oscillation because the phase criterion is not satisfied. The amplifier introduces a phase shift of  $180^\circ$  and the feedback circuit can only exhibit a phase shift between  $-90^\circ$  and  $+90^\circ$

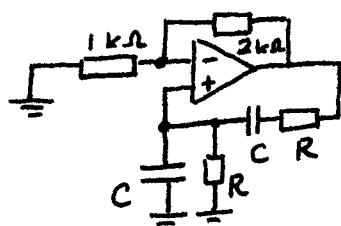- (c) Using the same components, a Wien oscillator can be realised as shown below



The amplifier has a gain  $A = 3 + j0$   
The voltage gain of the feedback circuit is


$$B = \frac{\frac{V_f}{V_i}}{\frac{1}{R} + j\omega C} = \frac{1}{\frac{1}{R} + j\omega C + R + \frac{1}{j\omega C}} = \frac{1}{3 + j(\omega CR - \frac{1}{\omega CR})}$$

So the feedback circuit has a phase shift of zero at a radian frequency  $\omega = 1/CR$  and, at that frequency, a gain of  $1/3$ . Since the amplifier has a gain of 3 and a phase shift of zero, the condition for oscillation is satisfied

- (d) If  $\omega = 2\pi 1590 = 10^4$ ,  $CR = 10^{-4}$ . Select  $R = 10^4$  ohms so that  
 $C = 10^{-8} = 0.01 \mu F$

## Answer 5

(a) Set the current source to zero

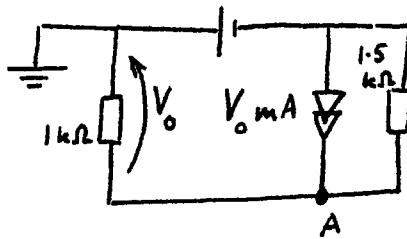



KCL at A:

$$-V_A + \frac{(-15-V_A)}{1.5} - V_A = 0$$

$$\therefore V_A = -3.75 \text{ Volts}$$


$$\text{so } V_o = 3.75 \text{ Volts}$$

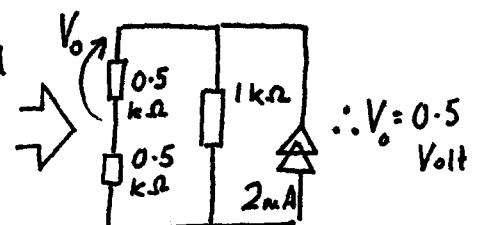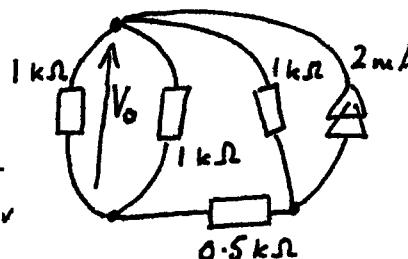Set the voltage source to zero, whereupon VCCS is equivalent to a 1kΩ resistor



$$\text{So, by Superposition, } V_o = 3.75 + 0.5 = 4.25 \text{ Volts}$$

(b)

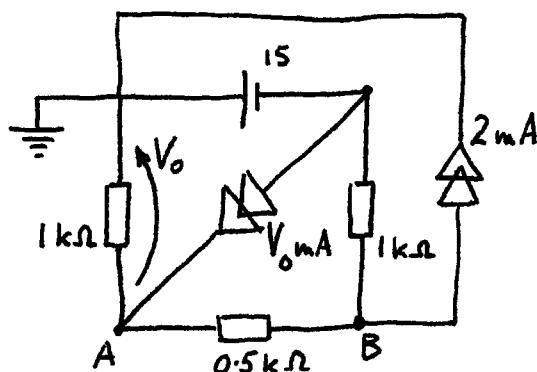

Note that  $V_o = -V_A$

$$\text{KCL at A (in)} \quad V_o + \frac{V_B - V_A}{0.5} - \frac{V_A}{1} \Rightarrow -4V_A + 2V_B = 0 \quad \text{--- (1)}$$

$$\text{KCL at B (in)} \quad -2 + \frac{(-15-V_B)}{1} + \frac{(V_A - V_B)}{0.5} \Rightarrow 2V_A - 3V_B = 17 \quad \text{--- (2)}$$

$[1 \times 3] + [2 \times 2]$  yields

$$-12V_A + 4V_A = 34 \quad \text{so } V_A = -4.25 \text{ Volts}$$

Therefore  $V_o = 4.25 \text{ Volts}$