

Master copy - Aug. 04

E2.1

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATIONS 2004

EEE/ISE PART II: MEng, BEng and ACGI

**DIGITAL ELECTRONICS 2**

Friday, 11 June 2:00 pm

Time allowed: 2:00 hours

**There are FIVE questions on this paper.**

**Answer THREE questions.**

*All questions carry equal marks*

**Corrected Copy**

**Any special instructions for invigilators and information for candidates are on page 1.**

Examiners responsible

First Marker(s) : D.M. Brookes

Second Marker(s) : T.J.W. Clarke

Notation:

Unless explicitly indicated otherwise, digital circuits throughout this paper are drawn with their inputs on the left and their outputs on the right. The notation  $X2:0$  denotes the three-bit number  $X2$ ,  $X1$  and  $X0$ . The least significant bit of a binary number is always designated bit 0. The numerical value of the number  $X2:0$  is given by  $x$ .

1. Figure 1.1 shows the circuit for a successive approximation Analog-to-Digital converter having an input voltage  $V$  and a two's-complement signed 8-bit output  $X7:0$  in the range  $-128$  to  $+127$ . One LSB of the converter is equal to  $0.2$  V and input voltages in the range  $\pm 0.1$  V are converted to the value 0.
  - (a) If the input voltage  $V$  equals  $-10.45$  V, determine the value of the output  $X7:0$ . [3]
  - (b) Give the sequence of values taken at  $X7:0$  during the process of converting an input voltage of  $-10.45$  V and give the corresponding voltages at  $W$ . [11]
  - (c) The aperture of the sampling switch is  $50$  ns and the propagation delays of the D/A converter and comparator are  $100$  ns and  $60$  ns respectively. Neglecting any propagation delays in the control logic, calculate the minimum time to convert an input voltage. You may assume that  $X7:0$  is set to the correct initial value before the conversion process begins. [3]
  - (d) If the comparator input current lies in the range  $\pm 2$   $\mu$ A, calculate the minimum value of  $C$  to ensure that the capacitor voltage changes by no more than  $\frac{1}{2}$  LSB during the conversion time found in part (c). [3]

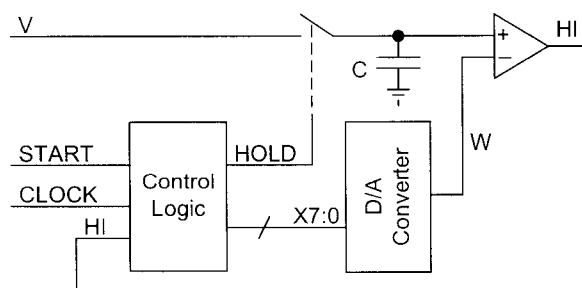


Figure 1.1

2. The state of a synchronous state machine is represented by a 3-bit number  $Q2:0$ . It has two inputs,  $A$  and  $B$ , and two outputs  $X$  and  $Y$ . The state table shown in *Table 2.1* gives the next state synchronized with the clock.

- (a) Draw a state diagram for the state machine using the relative positions of the states shown in *Figure 2.1*. Your diagram should indicate the state transitions and the output signals. Transitions from a state to itself should be omitted. [8]
- (b) If inputs  $A$  and  $B$  have the waveforms shown in *Figure 2.2*, determine the state sequence and the waveforms of  $X$  and  $Y$ . The clock rising edges are indicated by vertical lines and the state machine is initially in state 0. [6]
- (c) Determine Boolean expressions for  $D2$ ,  $D1$ ,  $D0$ ,  $X$  and  $Y$  that are as simple as possible. [6]

| D2:0/X,Y |   | A,B   |       |       |       |
|----------|---|-------|-------|-------|-------|
|          |   | 00    | 01    | 11    | 10    |
| Q2:0     | 0 | 0     | 1     |       | 6     |
|          | 1 | 0     | 1     | 3     |       |
|          | 2 | 0/1,0 |       | 7/1,0 | 6/1,0 |
|          | 3 |       | 1     | 3     | 2     |
|          | 4 | 0/0,1 | 1/0,1 |       | 6/0,1 |
|          | 5 | 4     | 5     | 7     |       |
|          | 6 | 0     |       | 7     | 6     |
|          | 7 |       | 5     | 7     | 6     |

Table 2.1

 


Figure 2.1

 


Figure 2.2

3. In a binary data transmission scheme, each transmitted bit occupies a bitcell having a duration of  $1 \mu\text{s}$ . For a logical 0, the transmitted signal is low throughout the bitcell whereas for a logical 1, a short pulse is transmitted at the start of the bitcell. In order to prevent long intervals without any transmitted pulses, the transmitter inserts an additional bitcell containing a pulse whenever four consecutive zero bits have been transmitted. *Figure 3.1* illustrates the transmission of the bit sequence 1110000101 in which the inserted bitcell is marked with \*. The frequency of *CLOCK* is 8 MHz.

- (a) The output signal, *D*, of the transmitter is connected to the receiver circuit of *Figure 3.2* which consists of a 6-bit counter and four gates. On each rising edge of *CLOCK* the counter increments unless *D* is high in which case it resets to 0. All pulses on *D* last for exactly one *CLOCK* cycle with signal transitions occurring slightly after the *CLOCK* rising edge.

Draw a timing diagram showing the data sequence of *Figure 3.1* and the resultant waveforms of *D*, *V*, *W*, *X* and *Y*. On your diagram, show the decimal value of *Q5:0* during each output pulse on *X* or *Y*. Do not attempt to show the waveform of *CLOCK* on your diagram. [10]

- (b) Modify the circuit so that output pulses are suppressed for the bitcell that immediately follows a sequence of four consecutive 0 bits. You may use any standard logic elements provided you fully specify their operation. [10]

 


Figure 3.1

 


Figure 3.2

4. In this question,  $P3:0$ ,  $Q$ ,  $R2:0$ ,  $D3:0$  and  $Y7:0$  all represent unsigned binary numbers whose numerical values are given respectively by  $p$ ,  $q$ ,  $r$ ,  $d$  and  $y$ .
- (a) The input to the “DIV” logic module shown in *Figure 4.1* is a number  $p$  in the range 0 to 9. The module outputs are the 1-bit quotient,  $q$ , and the 3-bit remainder,  $r$ , that result from dividing  $p$  by 5. Thus if  $p = 7$ , the circuit will give  $q = 1$  and  $r = 2$ .

Determine a Boolean expression for  $Q$  and hence show how the whole module may be formed using a 3-bit adder and appropriate gates. [5]

- (b) *Figure 4.2* shows a circuit that combines the “DIV” module of part (a) with a 4-bit register and an 8-bit shift register whose outputs shift in the direction  $Y0 \rightarrow Y1 \rightarrow \dots \rightarrow Y7$ . If  $p_n$  and  $y_n$  represents the values of  $p$  and  $y$  after the  $n^{\text{th}}$  clock pulse, give algebraic expressions for  $p_{n+1}$  and  $y_{n+1}$  in terms of  $p_n$  and  $y_n$  for each of the four cases [6]

- (i)  $p_n < 5$  and  $y_n < 128$
- (ii)  $p_n \geq 5$  and  $y_n < 128$
- (iii)  $p_n < 5$  and  $y_n \geq 128$
- (iv)  $p_n \geq 5$  and  $y_n \geq 128$ .

- (c) If  $p_0 = 0$  and  $y_0 = 215_{10} = 11010111_2$ , determine the values of  $p_n$  and  $y_n$  for  $n = 1, \dots, 8$ . [6]

- (d) Given that  $p_0 = 0$ , explain the relationship of  $p_8$  and  $y_8$  to the number  $y_0$ . Determine the maximum possible value of  $y_8$  and say what value of  $y_0$  will result in it. [3]

 


Figure 4.1

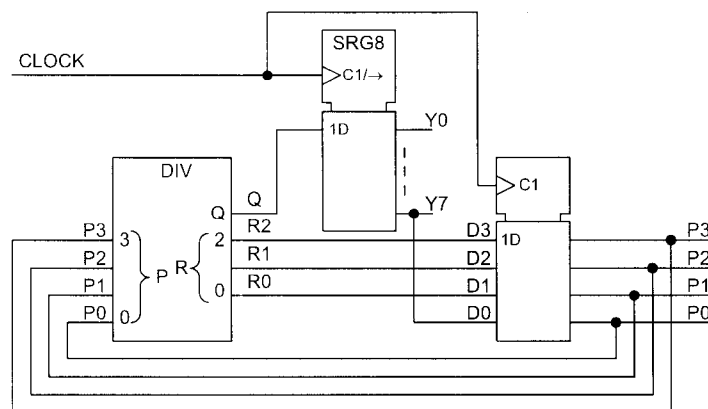


Figure 4.2

5. Figure 5.1 shows two 1-bit full adder modules, labelled  $\Sigma E$  and  $\Sigma O$ , which can be cascaded to form an  $n$ -bit adder with the two modules used respectively for the even and odd numbered bit positions. Thus a  $\Sigma E$  module is used for bit 0, the least significant bit. The propagation delays, in gate delays, of the two modules are

|            |     |       |            |     |      |
|------------|-----|-------|------------|-----|------|
| $\Sigma E$ | $S$ | $!CO$ | $\Sigma O$ | $S$ | $CO$ |
| $P, Q$     | 3   | 1     | $P, Q$     | 5   | 2    |
| $CI$       | 3   | 1     | $!CI$      | 4   | 1    |

(a) If  $n$  modules are cascaded to form an  $n$ -bit adder as described above, calculate for both even and odd  $n$  the worst-case delays from any input to (i) any  $S$  output and (ii) any  $CO$  or  $!CO$  output. [5]

(b) In Figure 5.2 the two  $n$ -bit adders have the same  $P$  and  $Q$  inputs but their  $CI$  inputs are fixed at 0 and 1 respectively. Using a multiplexer, the input signal  $CIN$  is used to select between the outputs of the adders.

- (i) Show that the combined circuit acts as a single  $n$ -bit adder.
- (ii) Design the circuitry for the part of the multiplexer that generates the  $COUT$  output.
- (iii) Using the propagation delays from part (a) above and assuming that  $n$  is even, calculate the four propagation delays for the circuit from each of  $CIN$  and  $P_0$  to each of  $COUT$  and  $S_{n-1}$ . [9]

(c) If we denote by  $A_n$  and  $B_n$  the  $n$ -bit adders of part (a) and of Figure 5.2 respectively, determine the worst-case propagation delay from any  $P$  input to the  $S_{63}$  output for each of the 64-bit adders using (i) a single  $A_{64}$  adder and (ii) an  $A_{32}$  adder followed by a  $B_{32}$  adder. [6]

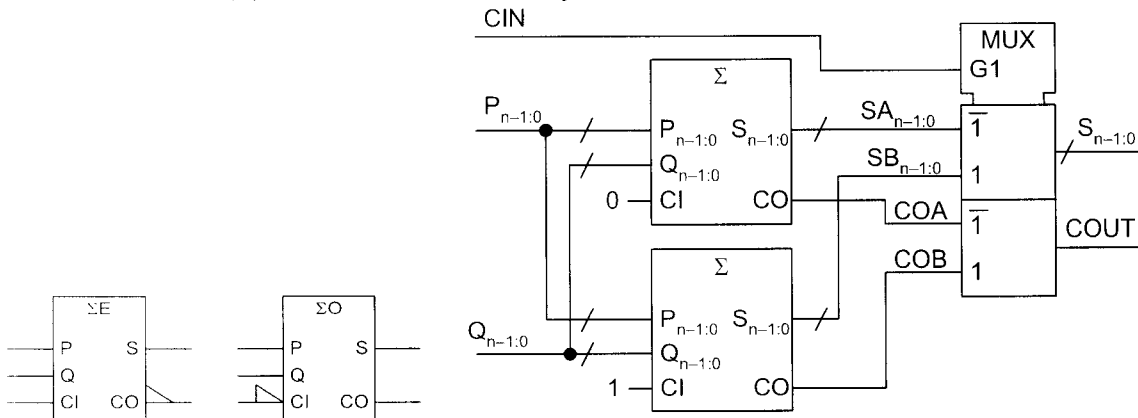


Figure 5.1

Figure 5.2

Master August 2009

ANALOG ELECTRONICS II

SECURUMS - 2009

[E2.1, ISE2.2]

1 (a)  $x = \text{round}(V/0.2) = \text{round}(-52.25) = -52 = 11001100$  [3]


(b) The voltage  $W$  must be the lower threshold of the corresponding input interval and is therefore  $w = 0.2x - 0.1$ . The sequence is as follows: [11]

| Clock | Step | X   | X (binary) | W     |
|-------|------|-----|------------|-------|
| 0     | 128  | 0   | 0000 0000  | -0.1  |
| 1     | 64   | -64 | 1100 0000  | -12.9 |
| 2     | 32   | -32 | 1110 0000  | -6.5  |
| 3     | 16   | -48 | 1101 0000  | -9.7  |
| 4     | 8    | -56 | 1100 1000  | -11.3 |
| 5     | 4    | -52 | 1100 1100  | -10.5 |
| 6     | 2    | -50 | 1100 1110  | -10.1 |
| 7     | 1    | -51 | 1100 1101  | -10.3 |
| 8     | 0.5  | -52 | 1100 1100  | -10.5 |

(c) If we assume that  $X_{7:0}$  is set to 0 before the conversion starts, then we don't have to wait for the 100 ns the first time around. The minimum conversion time is therefore  $50 + 60 + 7 \times 160 = 1.23 \mu\text{s}$ . [3]


(d)  $C = \frac{I \times \Delta t}{\Delta V} = \frac{2 \mu\text{A} \times (1.23 - 0.05) \mu\text{s}}{0.1\text{V}} = 23.6 \text{ pF}$  [3]

2. (a) The state diagram is:

 

Inputs: A,B  
Default: X=Y=0 [8]

(b) The timing diagram is:

 

[6]

(c) These are all straightforward except for D2 for which we need a Karnaugh map and find the two groups of 8 shaded below:

| D2   |   | A,B |    |    |    |         |
|------|---|-----|----|----|----|---------|
|      |   | 00  | 01 | 11 | 10 |         |
| Q2:0 | 0 | 0   | 0  | 1  | 1  | ← A!Q0  |
|      | 1 | 0   | 0  | 0  |    |         |
|      | 3 |     | 0  | 0  | 0  |         |
|      | 2 | 0   |    | 1  | 1  |         |
|      | 6 | 0   |    | 1  | 1  |         |
|      | 7 |     | 1  | 1  | 1  | ← Q2·Q0 |
|      | 5 | 1   | 1  | 1  |    |         |
|      | 4 | 0   | 0  |    | 1  |         |

$D2=Q2.Q0 + A.!Q0$


$D1=A$   
 $X=!Q2.Q1.!Q0$

$D0=B$   
 $Y=Q2.!Q1.!Q0$


[6]



 
3. (a) Because of the AND-gate, pulses on X or Y can only occur when  $Q2:0 = 011_2$  which means that that  $Q5:0 = 3 + 8k$  for some integer  $k$ . The falling edges of W occur when the counter resets to zero which is immediately at the end of the input pulses. Pulses on V occur midway between the input pulses. In the timing diagram below, Q is the value of  $Q5:0$ . [10]



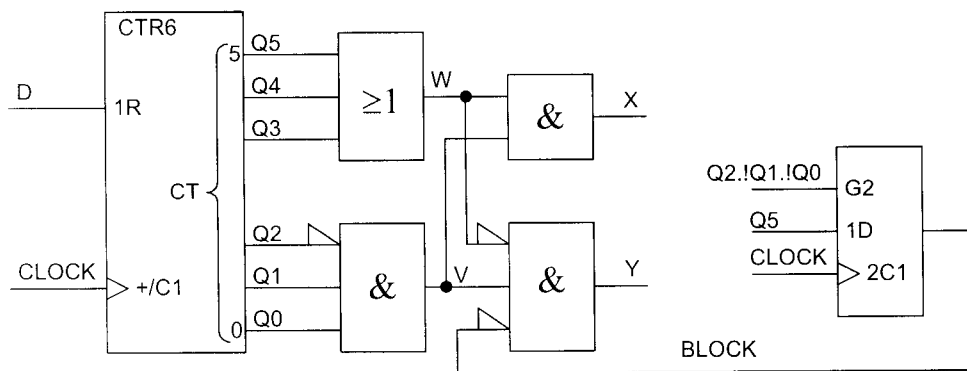- (b) We need to remember that we have had four consecutive zeros and then suppress the next pulse. The easiest way to do this is to use a flipflop with a clock enable input to remember the value of Q5 at the last pulse: [10]



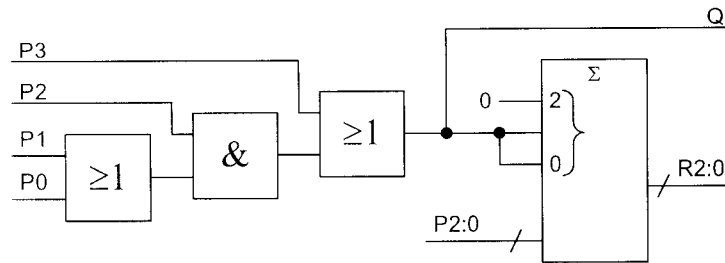4. (a)  $Q = (p \geq 5) = P3 + P2.(P1+P0)$  and whenever  $Q=1$ , we need to subtract 5 (= add 3 modulo 8) from  $P$  to give  $R$ . hence:



[5]

- (b)  $y_{n+1} = 2y_n + q_n - 256(y_n \geq 128) = 2y_n + (p_n \geq 5) - 256(y_n \geq 128)$  and  
 $p_{n+1} = 2r_n + (y_n \geq 128) = 2p_n - 10(p_n \geq 5) + (y_n \geq 128)$

Hence we get:

- (i)  $p < 5, y < 128$        $y_{n+1} = 2y_n$  and  $p_{n+1} = 2p_n$   
 (ii)  $p \geq 5, y < 128$        $y_{n+1} = 2y_n + 1$  and  $p_{n+1} = 2p_n - 10$   
 (iii)  $p < 5, y \geq 128$        $y_{n+1} = 2y_n - 256$  and  $p_{n+1} = 2p_n + 1$   
 (iv)  $p \geq 5, y \geq 128$        $y_{n+1} = 2y_n - 255$  and  $p_{n+1} = 2p_n - 9$

[6]

- (c) Using the above expressions, we can generate the following table:

[6]

| clock | $y$ | $y$ (binary) | $p$ | $q$ | $r$ | $d$ |
|-------|-----|--------------|-----|-----|-----|-----|
| 0     | 215 | 1101 0111    | 0   | 0   | 0   | 1   |
| 1     | 174 | 1010 1110    | 1   | 0   | 1   | 3   |
| 2     | 92  | 0101 1100    | 3   | 0   | 3   | 6   |
| 3     | 184 | 1011 1000    | 6   | 1   | 1   | 3   |
| 4     | 113 | 0111 0001    | 3   | 0   | 3   | 6   |
| 5     | 226 | 1110 0010    | 6   | 1   | 1   | 3   |
| 6     | 197 | 1100 0101    | 3   | 0   | 3   | 7   |
| 7     | 138 | 1000 1010    | 7   | 1   | 2   | 5   |
| 8     | 21  | 0001 0101    | 5   | 1   | 0   | 0   |

- (d) The numbers  $y_8$  and  $p_8$  are the quotient and remainder after dividing  $y_0$  by 10. The maximum possible value of  $y_0$  is 255 which will result in  $y_8 = 25$  and  $p_8 = 5$ . This is therefore the maximum value of  $y_8$ .

[3]

5. (a) We get one delay from each stage except the last which has more:

[5]


|        | S   | CO/!CO |
|--------|-----|--------|
| n even | n+3 | n      |
| n odd  | n+2 | n      |

(b) (i) If CIN=0 then the outputs come from the top adder which has CI=0. Similarly for CIN=1.

[2]

(ii) This is a standard multiplexer:

[3]

 

(iii) The multiplexer adds 2 onto the delays from P but reduces the delay from CIN to only 3 (independent of n).

[4]

|     | S   | COUT |
|-----|-----|------|
| CIN | 3   | 3    |
| P0  | n+5 | n+2  |

(c) (i)  $P0 \rightarrow S63 = 67$

[2]

(ii)  $\max(P0 \rightarrow C31 \rightarrow S63, P32 \rightarrow S63)$   
 $= \max(32+3, 32+5) = \max(35, 37) = 37$

[4]