

6.(a) Figure 6.1 shows a doubly-terminated passive LC-ladder lowpass filter.

(i) Give three advantages of the LC-ladder approach for implementing continuous time filters and state two reasons why passive LC ladders are unsuitable for implementing fully-integrated filters.

[5]

(ii) By constructing a signal flow graph of the ladder topology shown in Figure 6.1, outline how this filter can be transformed into a topology suitable for integration, and sketch a block diagram of the resulting filter architecture.

[10]

(b) Figure 6.2 shows a differential input transconductor that can be used to make integrators for the above filter. Assuming that devices M1-M4 are saturated, whilst M5, M6 are in the linear region, derive an expression for the transconductance gain I_{out}/V_{in} .

[5]

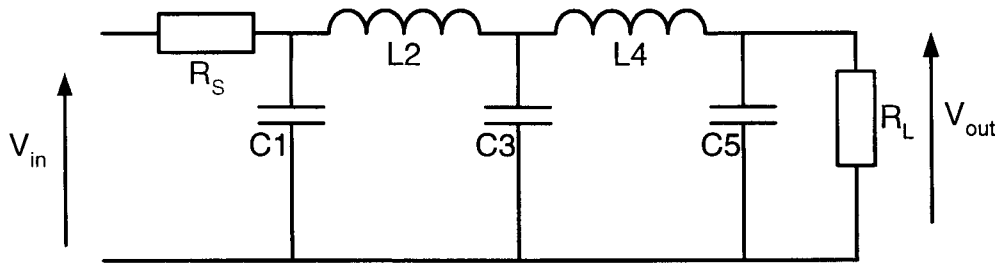


Figure 6.1

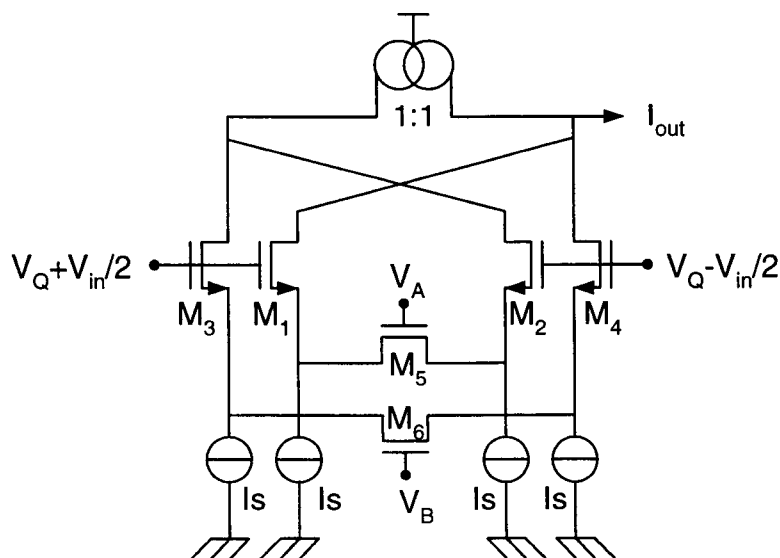


Figure 6.2

