

Electronics Classwork 3 - Solutions, 13th January 2005

Dr Mark Neil

1. (a) 22mH and 47mH in parallel form a combined inductance of $22 \times 47 / (22 + 47) = 15.0\text{mH}$. In series combination with the 33mH inductor the total inductance is $15.0 + 33 = 48.0\text{mH}$

(b) 20nF in series with 20nF gives combined capacitance of $20 \times 20 / (20 + 20) = 10\text{nF}$. 10nF in parallel with 10nF gives $10 + 10 = 20\text{nF}$.

2. Kirchhoff's voltage law on loop

$$V = IR + V_C$$

But from Ohms law on capacitor:

$$I = C dV_C / dt$$

So

$$V = RC dV_C / dt + V_C$$

Or

$$dV_C / dt = (V - V_C) / RC$$

Integrate:

$$\int_0^{V_C} \frac{dV_C}{V_C - V} = \int_0^t \frac{-dt}{RC}$$

Limits given by $V_C = 0$ at $t = 0$ and $V_C = V_C$ at time $t = t$.

$$\left[\ln(V_C - V) \right]_0^{V_C} = \left[\frac{-t}{RC} \right]_0^t$$

$$\ln(V_C - V) - \ln(-V) = \ln\left(\frac{V - V_C}{V}\right) = \frac{-t}{RC}$$

Take exponential of both sides:

$$\frac{V - V_C}{V} = \exp\left(\frac{-t}{RC}\right)$$

$$V_C = V \left(1 - \exp\left(\frac{-t}{RC}\right) \right)$$

$$V = V_0 = 10\text{V}, \quad \tau = RC = 10^3 \times 10^{-6} = 10^{-3}\text{s} = 1\text{ms}$$

Voltage across resistor $V_R = V - V_C$; $I = V_R / R$

$$V_C = V \left(\exp\left(\frac{-t}{RC}\right) \right); \quad I = \frac{V}{R} \left(\exp\left(\frac{-t}{RC}\right) \right)$$

3. Take real part of complex value:

(a) $I = I_0 \cos(\omega t)$

Amplitude I_0 , angular frequency $= \omega$, frequency $= \omega / (2\pi)$, phase $= 0$

(b) $V = 240\sqrt{2} \cos(100\pi t + \pi/2) = -339.4 \sin(100\pi t) \text{ V}$

Amplitude 339.4V, $f = 50\text{ Hz}$, $\omega = 2\pi \times 50 = 100\pi$, phase $= \pi/2$ radians $= 90^\circ$

Convert to cos then change cos term to $\exp(j\dots)$ and drop the $\exp[j\omega t]$ term

(c) $\tilde{V} = 5.0 \exp[j\pi/4]$

Amplitude 5.0V, $\omega = 1000$, $f = 1000 / (2\pi) = 159\text{ Hz}$, phase $= \pi/4$ radians $= 45^\circ$

(d) $I = 7.0 \sin(62.8 \times 10^6 t - \pi/6) = 7.0 \cos(62.8 \times 10^6 t - 2\pi/3)$

$$\tilde{I} = 7.0 \exp[j(62.8 \times 10^6 t - 2\pi/3)]$$

Amplitude 7.0V, $\omega = 62.8 \times 10^6$, $f = 62.8 \times 10^6 / (2\pi) = 10^7 \text{ Hz} = 10\text{ MHz}$, phase $= -2\pi/3$ radians $= -120^\circ$

4. Complex impedance of capacitor, $Z_C = 1 / (j\omega C)$; Complex Ohm's Law $V = IZ_C$

(b) $Z_C = 1 / (j\omega C) = -j / (100\pi \times 10^{-9}) = -3.18 \times 10^6 j$

$$\begin{aligned} \tilde{I} &= \tilde{V} / Z_C = 240\sqrt{2} \exp[j\pi/2] / -3.18 \times 10^6 j = 1.07 \times 10^{-3} j \exp[j\pi/2] \\ &= 1.07 \times 10^{-3} \exp[j\pi] = -1.07 \times 10^{-3} \end{aligned}$$

Real current, take real part:

$$I = -1.07 \times 10^{-3} \cos(100\pi t) \text{ A} = -1.07 \cos(100\pi t) \text{ mA}$$

(c) $Z_C = 1 / (j\omega C) = -j / (1000 \times 10^{-9}) = -10^6 j$

$$\begin{aligned} \tilde{I} &= \tilde{V} / Z_C = 5 \exp[j\pi/4] / (-10^6 j) = 5 \times 10^{-6} j \exp[j\pi/4] \\ &= 5 \times 10^{-6} \exp[j3\pi/4] \end{aligned}$$

Real current, take real part:

$$I = 5 \times 10^{-6} \cos(1000\pi t + 3\pi/4) \text{ A} = 5 \cos(1000\pi t + 3\pi/4) \mu\text{A}$$

5. Complex impedance of inductor, $Z_L = j\omega L$; Complex Ohm's Law $V = IZ_L$

(a) $Z_L = j\omega L = j10^{-6} \omega$

$$\tilde{V} = \tilde{I} Z_L = I_0 j10^{-6} \omega \exp[j\omega t] = I_0 10^{-6} \omega \exp[j\pi/2]$$

Real current, take real part:

$$V = I_0 10^{-6} \omega \cos(\omega t + \pi/2) = -I_0 10^{-6} \omega \sin(\omega t + \pi/2)$$

(b) $Z_L = j\omega L = j62.8 \times 10^6 \times 10^{-6} = 62.8 j \Omega$

$$\tilde{V} = \tilde{I} Z_L = 7 \times 62.8 j \exp[-j\pi/6] = 439.6 \exp[j\pi/3]$$

Real voltage, take real part:

$$V = 439.6 \text{ Re}[\exp[j(\omega t + \pi/3)]] = 439.6 \cos(62.8 \times 10^6 t + \pi/3)$$