

# Electronics Classwork 4 - Solutions, 27<sup>th</sup> January 2005

Dr Mark Neil

1. Potential divider:

$$\frac{\tilde{V}_o}{\tilde{V}_i} = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}}$$

(a)

$$\text{as } \omega \rightarrow 0: \frac{\tilde{V}_o}{\tilde{V}_i} \rightarrow \frac{j\omega \frac{L}{R}}{1} = j\omega \frac{L}{R}$$


$$\text{as } \omega \rightarrow \infty: \frac{\tilde{V}_o}{\tilde{V}_i} \rightarrow \frac{j\omega \frac{L}{R}}{j\omega \frac{L}{R}} = 1$$

$\omega \rightarrow 0$  asymptote is straight line of +20dB/decade crossing 0dB at  $\omega = R/L = 10^5 \text{ rad s}^{-1}$

$\omega \rightarrow \infty$  asymptote is a straight horizontal line at 0dB

(b)  $\omega_{3dB} = 10^5$  (see above)  $f_{3dB} = \omega_{3dB} / (2\pi) = 15.9 \text{ kHz}$

(c)

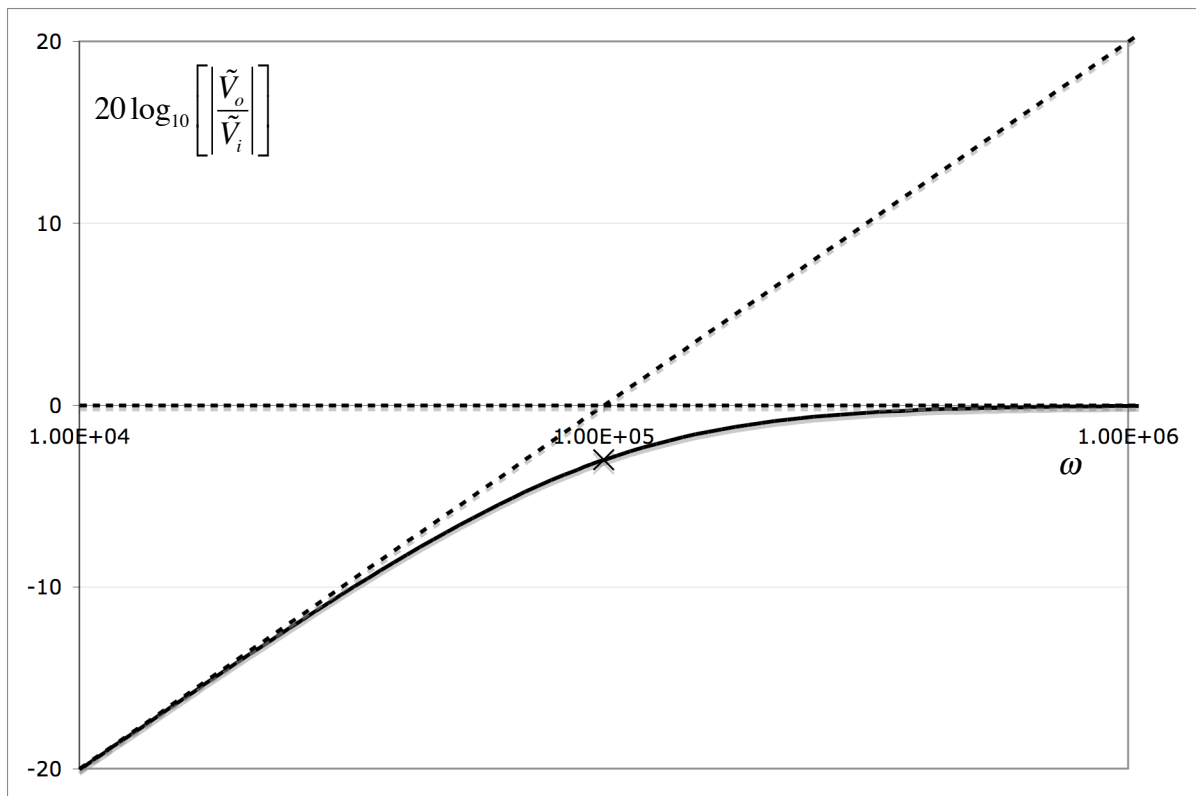

(d) High pass filter

2. (a)

$$Z = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

(b)

$$\tilde{V} = \tilde{I}_o Z = \tilde{I}_o \frac{j\omega L}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

(c)

$$\tilde{I}_R = \frac{\tilde{V}}{R} = \tilde{I}_o \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R} - \omega^2 LC} = \tilde{I}_o \frac{A\omega}{1 + j\frac{\omega}{\omega_o Q} - \frac{\omega^2}{\omega_o^2}}$$

$$A = j\frac{L}{R}; \omega_o = \frac{1}{\sqrt{LC}}; Q = \frac{R}{\omega_o L}$$

(d)

$$\omega_o = 2\pi f = 2\pi \times 125,000 = 7.85 \times 10^5 \text{ rad s}^{-1}$$

$$C = \frac{1}{\omega_o^2 L} = 463 \text{ nF}$$

$$Q = \frac{R}{\omega_o L} = 36.4$$

(e) At resonance  $\omega = \omega_o$

$$\tilde{V} = \tilde{I}_o \frac{j\omega L}{1 + j\omega \frac{L}{R} - 1} = \tilde{I}_o \frac{j\omega L}{j\omega \frac{L}{R}} = \tilde{I}_o R = 0.1 \times 100 = 10 \text{ V}$$

$$\tilde{I}_R = \frac{\tilde{V}}{R} = 0.1 \text{ A}$$

$$\tilde{I}_C = \tilde{V} j\omega_o C = 3.64 \text{ jA}$$

$$\tilde{I}_L = \frac{\tilde{V}}{j\omega_o L} = -3.64 \text{ jA}$$

(f) If there were no capacitor the current source would have to supply both the 100mA for the resistor and the 3.64A for the inductor. However these would be 90° out of phase and so would add in quadrature to give a total current of  $\sqrt{(0.1^2 + 3.64^2)} = 3.64 \text{ A}$

3.

$$\frac{\tilde{I}_R}{\tilde{I}_o} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

$$\text{as } \omega \rightarrow 0: \frac{\tilde{I}_R}{\tilde{I}_o} \rightarrow \frac{j\omega \frac{L}{R}}{1} = j\omega \frac{L}{R}$$

$$\text{as } \omega \rightarrow \infty: \frac{\tilde{I}_R}{\tilde{I}_o} \rightarrow \frac{j\omega \frac{L}{R}}{-\omega^2 LC} = \frac{1}{j\omega RC}$$

$$\text{at } \omega = \frac{1}{\sqrt{LC}}: \frac{\tilde{I}_R}{\tilde{I}_o} \rightarrow \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R} - 1} = 1$$

$\omega \rightarrow 0$  asymptote is straight line of +20dB/decade crossing 0dB at  $\omega = R/L = 2.86 \times 10^7 \text{ rad s}^{-1}$

$\omega \rightarrow \infty$  asymptote is straight line of -20dB/decade crossing 0dB at  $\omega = 1/RC = 2.16 \times 10^5 \text{ rad s}^{-1}$

$\omega = \omega_0 = 7.85 \times 10^5$  graph must pass through 0dB

