

Electronics problem sheet 2 - solutions, January 2005

Dr Mark Neil

1. Voltage difference across the resistor is $10-4=6V$.

So the current through the resistor is $I=6/100=0.06A=60mA$. Power in the resistor can be calculated in several ways: e.g. $I^2R = 0.06^2 \cdot 100 = 0.36W = 360mW$.

Increasing the voltage at both ends of the resistor by the same amount doesn't change the voltage difference across the resistor so the current and power remain the same.

- 2.

(a) Potential divider: Open circuit voltage $V_T = VR_2 / (R_1 + R_2 + R_3)$. R_o is resistance between terminals with V replaced by short circuit $= R_2 // (R_1 + R_3) = R_2(R_1 + R_3) / (R_1 + R_2 + R_3)$. $I_N = V_T / R_o = V / (R_1 + R_3)$.

(b) R_1 and R_2 in parallel gives impedance $R_4 = R_1 R_2 / (R_1 + R_2)$. Now looks like potential divider again:

Open circuit voltage $V_T = VR_3 / (R_3 + R_4) = VR_3 / (R_3 + R_1 R_2 / (R_1 + R_2))$

$$V_T = VR_3(R_1 + R_2) / (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

R_o is resistance between terminals if V is replaced by short circuit

$$R_o = R_1 // R_2 // R_3 = R_1 R_2 R_3 / (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

$$I_N = V_T / R_o = V(R_1 + R_2) / (R_1 R_2)$$

(c) Two 2Ω resistors in parallel are equivalent to a single 1Ω resistor. $2A$ current source in parallel with 1Ω resistor is equivalent to a $2V$ source in series with 1Ω resistor. Adding $2V$ source in series with $3V$ source gives a total $5V$ source still in series with a 1Ω resistor. Circuit now looks like a simple potential divider:


$$V_T = 5V \times 4\Omega / (1\Omega + 4\Omega) = 4V.$$

$$I_N = I_{SC} = 5V / 1\Omega = 5A.$$

$$R_o = V_T / I_N = 4/5\Omega$$

3. See notes "kirchhoff-nodal-mesh.pdf" on teaching website.

- 4.

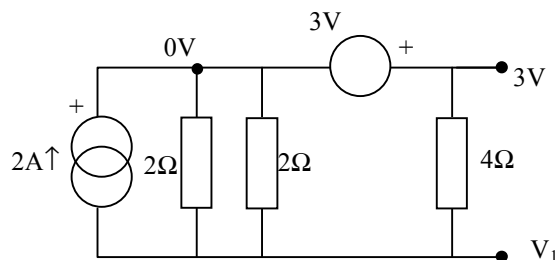


Choose reference node ($0V$) at bottom of voltage source and top of current source. Other nodes are then $3V$ and unknown V_1 .

Single node voltage equation summing currents into V_1 gives:

$$\begin{aligned}
 -2A + \frac{(3 - V_1)}{4} + \frac{(0 - V_1)}{2} + \frac{(0 - V_1)}{2} &= 0 \\
 -8 + 3 - V_1 - 2V_1 - 2V_1 &= 0 \\
 5V_1 &= -5 \\
 V_1 &= -1V
 \end{aligned}$$

Check $V_{oc} = 3 - V_1 = 4V$ (same as answer to 2(c))

5.

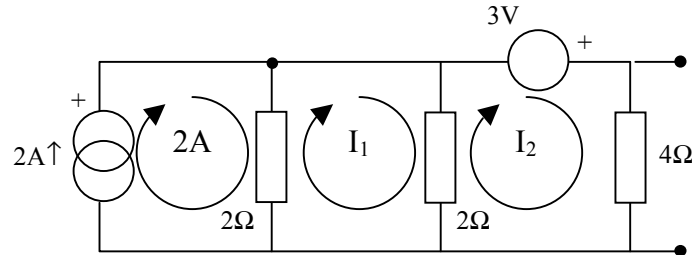


Three loops as shown. One loop has known current 2A flowing round it, the other two have unknown currents I_1 and I_2 flowing round them. Sum voltages round the loops I_1 and I_2 :

$$\begin{aligned}
 (I_1 - 2) \times 2 + (I_1 - I_2) \times 2 &= 0 \\
 4I_1 - 2I_2 - 4 &= 0 \\
 (I_2 - I_1) \times 2 + (I_2) \times 4 &= 3 \\
 6I_2 - 2I_1 &= 3 \\
 6I_2 - (I_2 + 2) &= 3 \\
 5I_2 &= 5 \\
 I_2 &= 1A \\
 I_1 &= (4 + 2I_2) / 4 = 1.5A
 \end{aligned}$$

Current down 2Ω resistors = $2 - I_1 = 0.5A$ or $I_1 - I_2 = 0.5A$ (both should be the same anyway). Current down 4Ω resistor = $I_2 = 1A$.

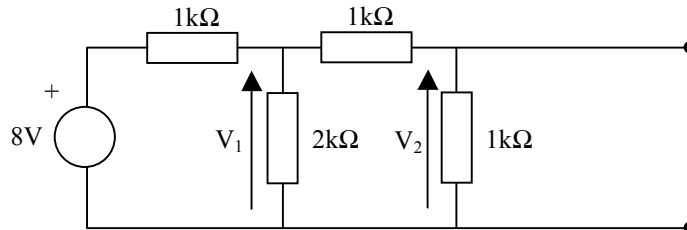6. The relationship between V_2 and V_3 can be easily obtained at the two $1k\Omega$ resistors form a potential divider such that $V_3 = V_2/2$.

These two $1k\Omega$ resistors also form a combined $2k\Omega$ resistance when added in series. This $2k\Omega$ resistance lies in parallel with the $2k\Omega$ resistance across which V_2 is measured and so the pair of them can be replaced by a single $1k\Omega$ resistor as shown below.



Thus the relationship between V_2 and V_1 becomes apparent as it is identical to that between V_3 and V_2 , ie $V_2 = V_1/2$.

By repeating the same resistor simplification we can also see that $V_1=8V/2=4V$.

Thus $V_1=4V$, $V_2=2V$ and $V_3=1V$.

7. In all cases apply the virtual earth approximation $V_+=V_-$ and no current flows into the input.

- (a) $V_+=V_-=V_i=1V$. Summing currents into V_- and using $R_2=9k\Omega$ and $R_1=1k\Omega$:

$$\frac{(V_o - V_-)}{R_2} + \frac{(0 - V_-)}{R_1} = 0$$

$$(V_o - V_i)R_1 - V_iR_2 = 0$$

$$V_o = V_i \left(1 + \frac{R_2}{R_1} \right) = 1V \left(1 + \frac{9k\Omega}{1k\Omega} \right) = 10V$$

- (b) $V_+=V_-=0V$. Summing currents into V_- and using $R_2=200k\Omega$ and $R_1=10k\Omega$:

$$\frac{(V_o - V_-)}{R_2} + \frac{(V_i - V_-)}{R_1} = 0$$

$$V_oR_1 + V_iR_2 = 0$$

$$V_o = -V_i \left(\frac{R_2}{R_1} \right) = -10mV \left(\frac{200k\Omega}{10k\Omega} \right) = -200mV$$

- (c) $V_+=V_-=0V$. Summing currents into V_- and using $R=1M\Omega$, $I=5\mu A$:


$$-I + \frac{(V_o - V_-)}{R_1} = 0$$

$$V_o - IR = 0$$


$$V_o = IR = 5\mu A \times 1M\Omega = 5V$$

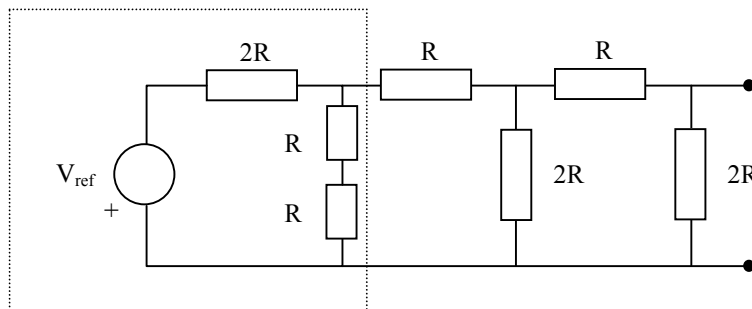8. With all switches connected to ground the Thevenin equivalent up to the op-amp input must have 0V as its voltage source. Switching in each of the S_n to $-V_{ref}$ individually will produce a Thevenin voltage source V_{Tn} which can be summed appropriately (by superposition) to give the total Thevenin voltage according to the combination of S_n .


First consider case of S_o closed to $-V_{ref}$ and S_1 and S_2 closed to ground (0V). A slight rearrangement of the circuit up to the input to the op-amp gives:



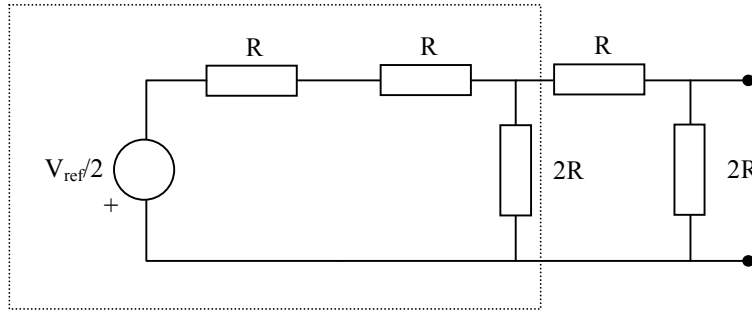
Replacing the boxed circuit with its Thevenin equivalent gives:



Repeating the process gives:

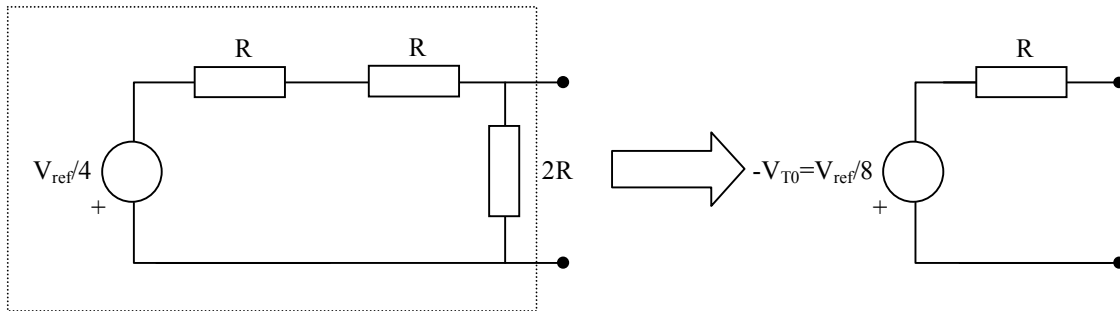

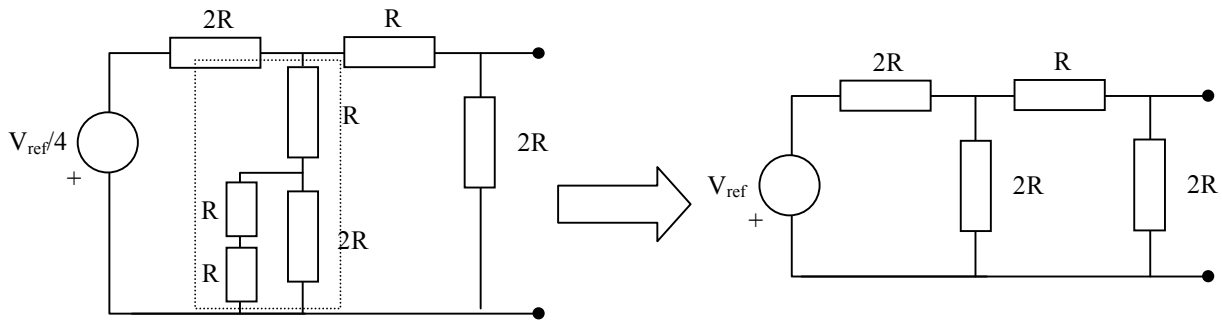
Now look at S_1 closed to $-V_{ref}$ and S_2 and S_3 closed to ground (0V). Rearrangement of the circuit and then simplifying the boxed network of resistors gives:



Now looks like case above at top of page but producing $V_{T1} = -V_{ref}/4$.

Similar approach for S_2 produces $V_{T2} = -V_{ref}/2$.

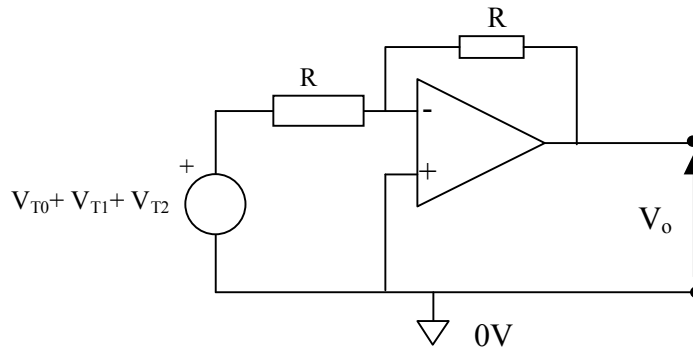Summing all Thevenin voltages by superposition gives a circuit:



Circuit now forms inverting amplifier with gain -1. So $V_o = -(V_{T0} + V_{T1} + V_{T2}) = 7V_{ref}/8$.

Circuit can generate voltages up to $7V_{ref}/8$ in steps of $V_{ref}/8$ according to the positions of the various S_n .