

Electronics problem sheet 3 - solutions, January 2005

Dr Mark Neil

1.

Resistors $V = IR$

Inductors $V = L \frac{dI}{dt}$ $I = \frac{1}{L} \int V dt$

Capacitors $V = \frac{1}{C} \int I dt$ $I = C \frac{dV}{dt}$

2.

$$C = \frac{\epsilon_r \epsilon_o A}{d}$$

$$A = \frac{Cd}{\epsilon_o} = \frac{10^{-6} \times 10^{-3}}{8.85 \times 10^{-12}} = 113m^2$$

If breakdown voltage is 1kV/mm then maximum voltage allowed is 1kV. Energy stored = $0.5CV^2 = 0.5 \times 10^{-6} \times (10^3)^2 = 0.5J$.

3.

$$L = \frac{\mu N^2 A}{l}$$

$$N = \sqrt{\frac{lL}{\mu_r \mu_o A}} = \sqrt{\frac{0.05 \times 10^{-4}}{400 \times 4\pi \times 10^{-7} \times \pi \times 0.004^2}} = 14.06$$

14 turns is closest value

4. At DC the inductor looks like a short circuit and so there can be no voltage across L. There is therefore no current through R_2 and the whole of the source voltage V falls across R_1 . The current through R_1 is therefore $I_0 = V/R_1$. This current then all flows through L too.

At the instant the switch is opened there can be no current in R_1 as it is open circuited and hence the voltage across R_1 is 0V. However the full value of I_0 must still be flowing down L and hence up R_2 (as drawn in the question) i.e. in a loop through L and R_2 . The voltage across the inductor and the resistor R_2 must have identical magnitude ($I_0 R_2$), but of opposite sign in respect to the direction of current flow as they form a loop where the total voltage around the loop must be zero. The sign is defined by the fact the top of the resistor and inductor is at a negative voltage relative to the bottom as drawn. Applying Kirchoff's voltage law around this loop:

$$L \frac{dI}{dt} + IR_2 = 0 \qquad \frac{dI}{dt} = -\frac{R_2}{L} I$$

$$\int_{I_o}^I \frac{1}{I} dI = \int_0^t -\frac{R_2}{L} dt$$

$$[\ln(I)]_{I_o}^I = \ln\left(\frac{I}{I_o}\right) = \left[-\frac{R_2}{L} t\right]_0^t = -\frac{R_2}{L} t$$

$$I(t) = I_o e^{-\frac{R_2}{L} t}$$


Instantaneous power in the resistor is given by $P(t) = I^2(t)R$ and integrating power with respect to time gives the total energy, U , dissipated in the resistor (and which originally was stored in the inductor):

$$P(t) = I(t)^2 R_2 = I_o^2 R_2 e^{-\frac{2R_2}{L} t}$$

$$U = \int_0^{\infty} P(t) dt = \int_0^{\infty} I_o^2 R_2 e^{-\frac{2R_2}{L} t} dt = \left[-\frac{L}{2R_2} I_o^2 R_2 e^{-\frac{2R_2}{L} t} \right]_0^{\infty} = \frac{1}{2} LI_o^2$$

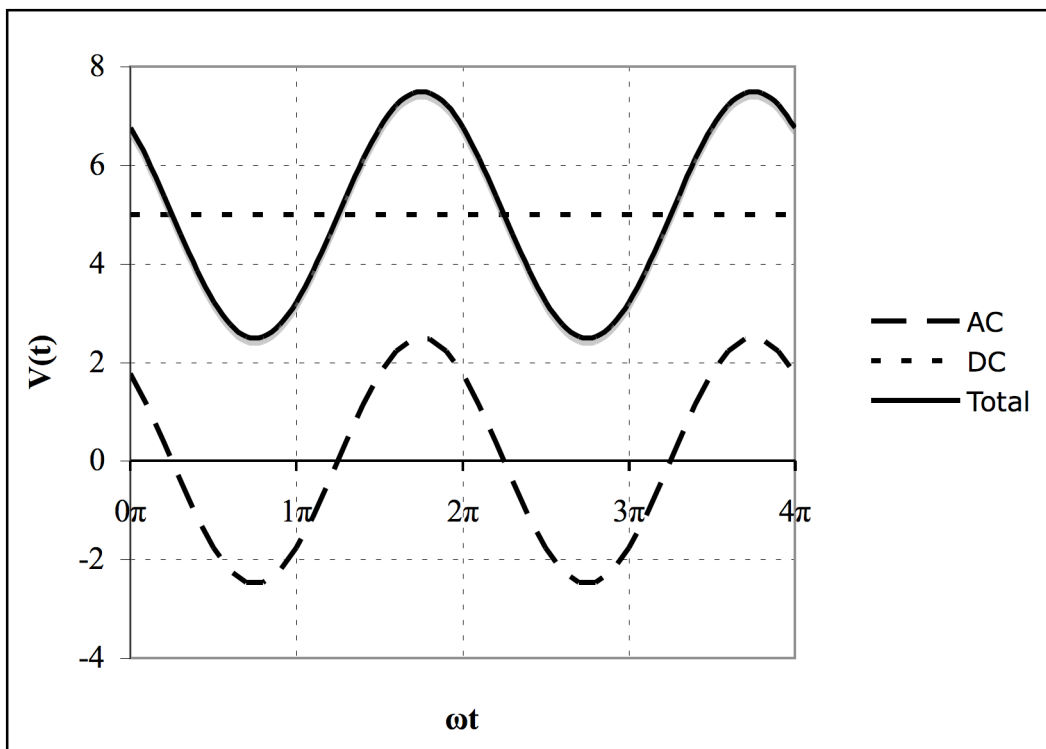5. See graph below labelling DC and AC components for the required signal

$$V(t) = 5 + 2.5 \cos(\omega t + \pi/4).$$



6. Assume *circular* contact capacitor electrodes of diameter 10mm.

(i)

$$C = \frac{\epsilon_r \epsilon_o A}{d} = \frac{80 \times 8.85 \times 10^{-12} \times \pi (5 \times 10^{-3})^2}{10^{-5}} = 5.56 \times 10^{-9} F = 5.6 nF$$

(ii)

$$|Z| = \frac{1}{\omega C} = \frac{1}{2\pi \times 10^9 \times 5.6 \times 10^{-9}} = 0.0286\Omega = 29m\Omega$$

Note that the capacitor looks very much like a short circuit (the peak current is actually $V_{\max}/|Z|=35A!!$)

(iii) Maximum charge is stored when voltage is a maximum so:

$$Q_{\max} = CV_{\max} = 5.6 \times 10^{-9} \times 1 = 5.6nC$$

7.

(i)

$$V(t) = 7 \cos\left(\omega t + \frac{\pi}{2}\right)$$

$$\tilde{V} = 7e^{j\frac{\pi}{2}} = 7j$$

(ii)

$$V(t) = 3 \sin(\omega t) = 3 \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\tilde{V} = 3e^{-j\frac{\pi}{2}} = -3j$$

(iii)



$$V_1(t) = 2 \cos\left(\omega t + \frac{\pi}{4}\right)$$

$$\tilde{V}_1 = 2e^{j\frac{\pi}{4}} = \sqrt{2}(1 + j)$$

$$V_2(t) = 4 \sin\left(\omega t + \frac{\pi}{2}\right) = 4 \cos(\omega t)$$

$$\tilde{V}_2 = 4e^{j0} = 4$$
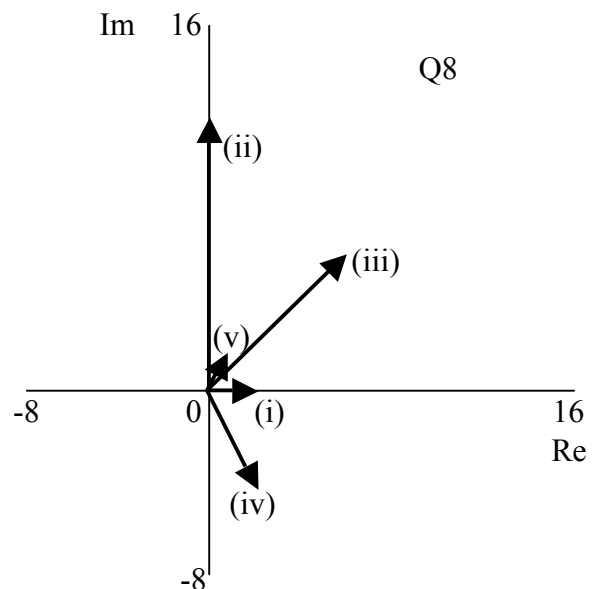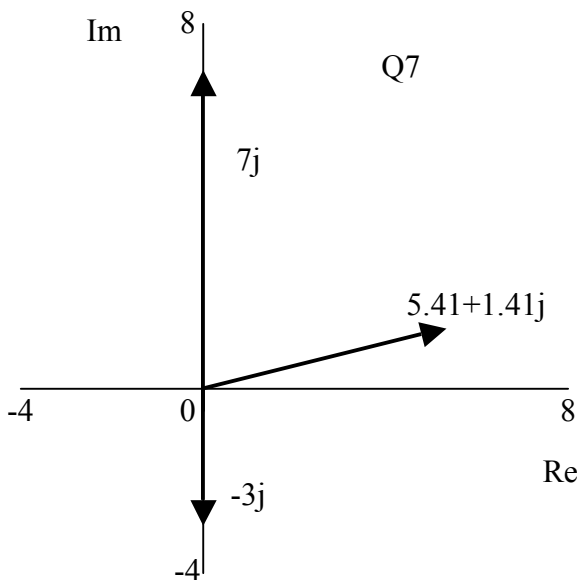
$$\tilde{V} = \tilde{V}_1 + \tilde{V}_2 = (4 + \sqrt{2}) + \sqrt{2}j = 5.60e^{j0.255}$$



8. See above for Argand diagram

$$(i) \quad \tilde{V} = 2 = 2e^{j0} \qquad V(t) = 2 \cos(\omega t)$$

$$(ii) \quad \tilde{V} = 12j = 12e^{j\frac{\pi}{2}} \qquad V(t) = 12 \cos\left(\omega t + \frac{\pi}{2}\right) = -12 \sin(\omega t)$$


$$(iii) \quad \tilde{V} = 6 + 6j = 6\sqrt{2}e^{j\frac{\pi}{4}} \qquad V(t) = 6\sqrt{2} \cos\left(\omega t + \frac{\pi}{4}\right) = 8.49 \cos\left(\omega t + \frac{\pi}{4}\right)$$

$$(iv) \quad \tilde{V} = 2 - 4j = \sqrt{2^2 + 4^2} e^{j \tan^{-1}\left(\frac{-4}{2}\right)} = \sqrt{20} e^{-j1.11}$$

$$V(t) = \sqrt{20} \cos(\omega t - 1.11) = 4.47 \cos(\omega t - 1.11)$$

$$(v) \quad \tilde{V} = 2e^{j\frac{\pi}{3}} = 1 + \sqrt{3}j \qquad V(t) = 2 \cos\left(\omega t + \frac{\pi}{3}\right)$$

9.

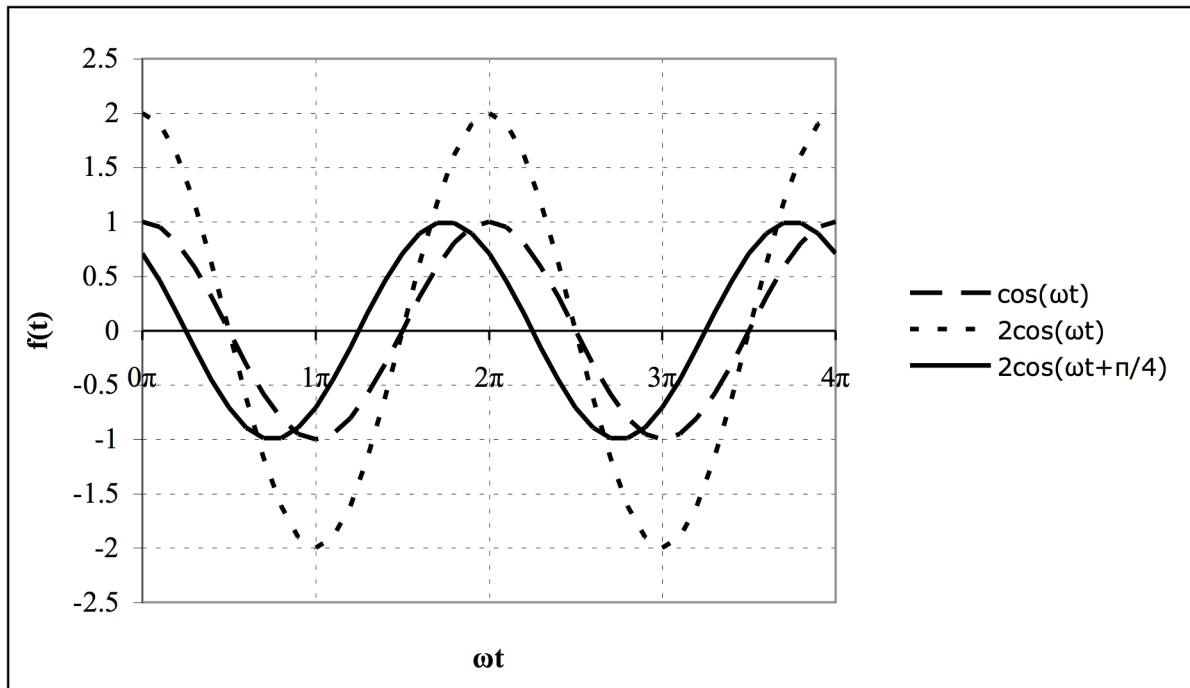

10.

$$\tilde{V} = V_o e^{j\frac{\pi}{4}}$$

$$\tilde{I} = \frac{V_o}{2} e^{j0}$$

$$Z = \frac{\tilde{V}}{\tilde{I}} = \frac{V_o e^{j\frac{\pi}{4}}}{\frac{V_o}{2} e^{j0}} = 2e^{j\frac{\pi}{4}} = \sqrt{2}(1 + j)\Omega$$

Equivalent to a resistor and inductor in series where the magnitude of the impedance of the inductor equals that of the resistor ($\sqrt{2}\Omega$).