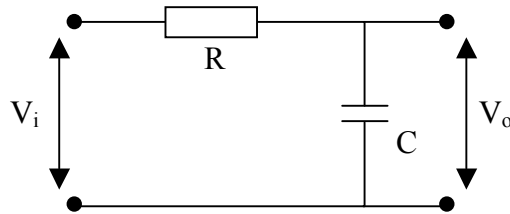



Electronics problem sheet 4 - solutions, January 2005

Dr Mark Neil

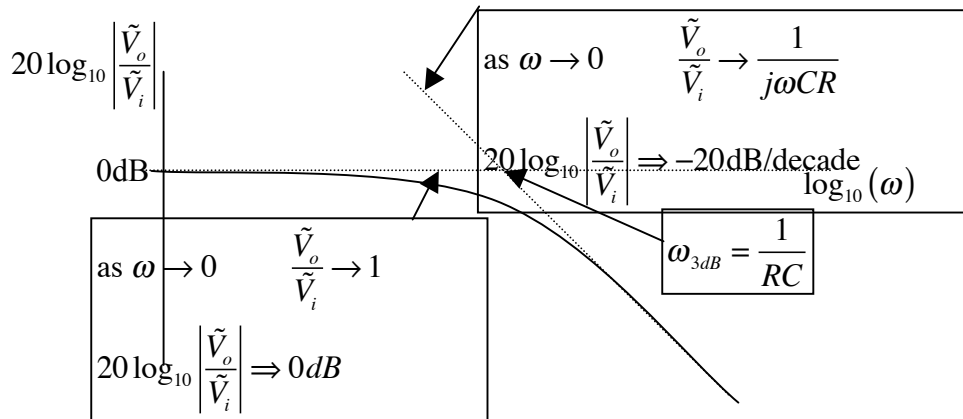1.



$$\frac{\tilde{V}_o}{\tilde{V}_i} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega CR}$$



$$f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi RC} = 7.95 \text{ Hz}$$

$$\text{At } \omega = 70: \quad \frac{\tilde{V}_o}{\tilde{V}_i} = \frac{1}{1 + j70 \times 10^4 \times 2 \times 10^{-6}} = \frac{1}{1 + j1.4} = \frac{1}{\sqrt{2.96}} e^{-j \tan^{-1}(1.4)}$$


$$\text{At DC:} \quad \frac{\tilde{V}_o}{\tilde{V}_i} = 1$$

$$V_o(t) = \frac{10}{\sqrt{2.96}} \cos(70t - \tan^{-1}(1.4)) + 15 = 5.81 \cos(70t - 54.5^\circ)$$

2. Removal of 99.9% of 100KHz signal means that 0.1% or -60dB attenuation of signal at 100KHz. As the filter performance will be very close to the -20dB/decade high frequency asymptote then this implies that $f_{3dB}=100\text{Hz}$ (three decades lower in frequency). A simple RC filter as in question 1 will do and its output impedance (Thevenin or Norton equivalent) is just R in parallel with C. Its maximum value (modulus) is at DC and is therefore simply R so we should choose $R=1\Omega$.

$$f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi RC} = 100 \text{ Hz} \quad C = \frac{1}{2\pi R f_{3dB}} = \frac{1}{200\pi} = 1,600 \mu\text{F}$$


3.

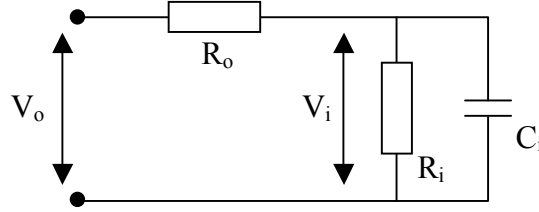

$$\frac{\tilde{V}_i}{\tilde{V}_o} = \frac{R_i // \frac{1}{j\omega C_i}}{R_o + R_i // \frac{1}{j\omega C_i}} = \frac{\frac{R_i}{1 + j\omega C_i R_i}}{R_o + \frac{R_i}{1 + j\omega C_i R_i}} = \frac{R_i}{R_o(1 + j\omega C_i R_i) + R_i} = \frac{R_i}{R_o + R_i} \frac{1}{1 + j\omega C_i \frac{R_o R_i}{R_o + R_i}}$$

$$\omega_{3dB} = \frac{1}{C_i \frac{R_o R_i}{R_o + R_i}} = \frac{R_o + R_i}{C_i R_o R_i} = 7.8 \text{ Mrads}^{-1} \quad f_{3dB} = \frac{\omega_{3dB}}{2\pi} = 1.24 \text{ MHz}$$

4.

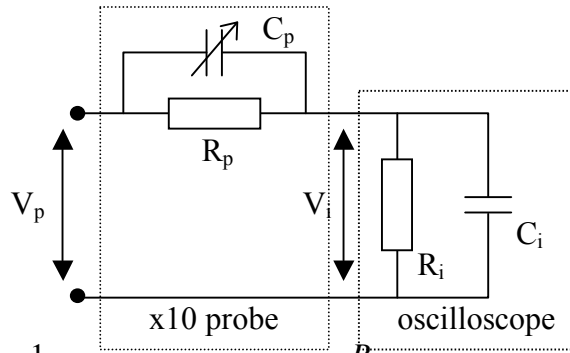

$$\frac{\tilde{V}_i}{\tilde{V}_p} = \frac{R_i // \frac{1}{j\omega C_i}}{R_p // \frac{1}{j\omega C_p} + R_i // \frac{1}{j\omega C_i}} = \frac{\frac{R_i}{1 + j\omega C_i R_i}}{\frac{R_p}{1 + j\omega C_p R_p} + \frac{R_i}{1 + j\omega C_i R_i}} = \frac{R_i}{R_p \frac{1 + j\omega C_i R_i}{1 + j\omega C_p R_p} + R_i}$$

$$\text{if } C_p R_p = C_i R_i \quad \frac{\tilde{V}_i}{\tilde{V}_p} = \frac{R_i}{R_p + R_i} = \frac{1}{10}$$

$$R_p = 9R_i \quad \therefore C_p = \frac{R_i C_i}{R_p} = \frac{R_i C_i}{9R_i} = \frac{C_i}{9} = 1.44 \text{ pF}$$

at $\omega = 2\pi \times 10^6 \text{ rads}^{-1}$

$$|Z_{C_p}| = \frac{1}{\omega C_p} = 110 \text{ k}\Omega \ll 9 \text{ M}\Omega \quad |Z_{C_i}| = \frac{1}{\omega C_i} = 12 \text{ k}\Omega \ll 1 \text{ M}\Omega$$

The total input capacitance C_T is approximately equal to C_p in series with C_i ,

$$C_T = \frac{C_p C_i}{C_p + C_i} = \frac{\frac{C_i}{9} C_i}{\frac{C_i}{9} + C_i} = \frac{C_i}{10} = 1.3 \text{ pF}$$

C_T forms a low pass filter in combination with $R_o = 10 \text{ k}\Omega$ from the output of the circuit.

Can get 3dB frequency from:

$$f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi R_o C_T} = 12 \text{ MHz}$$

5.

$$Z = Z_R + Z_C + Z_L = R + \frac{1}{j\omega C} + j\omega L = \frac{1 + j\omega CR - \omega^2 LC}{j\omega C}$$

$$|Z| = \frac{|1 + j\omega CR - \omega^2 LC|}{|j\omega C|} = \frac{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}}{\omega C}$$

$$\text{Arg}[Z] = \text{Arg}[1 + j\omega CR - \omega^2 LC] - \text{Arg}[j\omega C] = \tan^{-1}\left(\frac{\omega CR}{1 - \omega^2 LC}\right) - \frac{\pi}{2}$$

compare with standard form $\left(1 + j\frac{\omega}{\omega_o Q} - \frac{\omega^2}{\omega_o^2}\right)$

$$\omega_o = \frac{1}{\sqrt{LC}} \quad f_o = \frac{\omega_o}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{1}{\omega_o RC}$$

$$\tilde{I} = \frac{\tilde{V}_i}{Z} = \frac{j\omega C \tilde{V}_i}{1 + j\omega CR - \omega^2 LC}$$

$$\tilde{V}_R = \tilde{I}R = \frac{j\omega CR}{1 + j\omega CR - \omega^2 LC} \tilde{V}_i$$

6.

$$\frac{\tilde{V}_C}{\tilde{V}_i} = \frac{1}{1 + j\omega RC - \omega^2 LC} = \frac{1}{1 + j\frac{\omega}{\omega_o Q} - \frac{\omega^2}{\omega_o^2}}$$

$$\left|\frac{\tilde{V}_C}{\tilde{V}_i}\right|^2 = \frac{1}{\left(1 - \frac{\omega^2}{\omega_o^2}\right)^2 + \left(\frac{\omega}{\omega_o Q}\right)^2}$$

substitute $y = \left|\frac{\tilde{V}_C}{\tilde{V}_i}\right|^2, x = \left(\frac{\omega}{\omega_o}\right)^2 \Rightarrow y = \frac{1}{(1-x)^2 + \frac{x}{Q}}$

$$\frac{dy}{dx} = -\frac{-2(1-x) + \frac{1}{Q^2}}{\left((1-x)^2 + \frac{x}{Q}\right)^2} = -\frac{2x + \left(\frac{1}{Q^2} - 2\right)}{\left((1-x)^2 + \frac{x}{Q}\right)^2} = 0$$

$$\therefore x = 1 - \frac{1}{2Q^2} \quad \Rightarrow \quad \omega = \omega_o \sqrt{1 - \frac{1}{2Q^2}}$$

If $Q^2 < 0.5$ then the number inside the square root is -ve, the frequency at which the peak occurs would be imaginary and hence there is no peak.


$$Q = \frac{1}{\omega_o RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$R = \frac{1}{Q} \sqrt{\frac{L}{C}} = \frac{1}{0.5} \sqrt{\frac{4.7 \times 10^{-3}}{100 \times 10^{-12}}} = 13.7 k\Omega$$

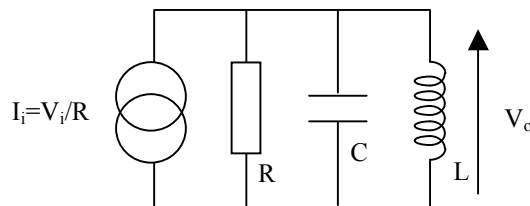7.

$$Q \approx \frac{\omega_o}{\Delta\omega_{3dB}} = \frac{f_o}{\Delta f_{3dB}} = \frac{10^6}{10^4} = 100$$

Convert suggested arrangement into Norton equivalent



Calculate equivalent impedance Z_T of LCR in parallel

$$Z_T = Z_R // Z_C // Z_L = \frac{1}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} = \frac{j\omega L}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

$$\tilde{V}_o = \tilde{I}_i Z_T = \tilde{I}_i \frac{j\omega L}{1 + j\omega \frac{L}{R} - \omega^2 LC} = \tilde{V}_i \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

Transfer function describes a band pass filter (because of ω dependence in numerator) with characteristics obtainable by comparison with the standard form (see above):

$$\omega_o = \frac{1}{\sqrt{LC}} \quad f_o = \frac{\omega_o}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

Choose $C = 100 pF$ (for instance)


$$L = \frac{1}{4\pi^2 f_o^2 C} = \frac{1}{4\pi^2 100} = 253 \mu H$$

$$Q = \frac{R}{\omega_o L} = 100$$

$$R = \omega_o L Q = 2\pi \times 10^6 \times 253 \times 10^{-6} \times 100 = 159 k\Omega$$

[You would be lucky to achieve a Q as high as 100, in practice the resistances present in the capacitor and inductor would limit the achievable Q and a much higher value of R than that calculated here would be needed]

8.

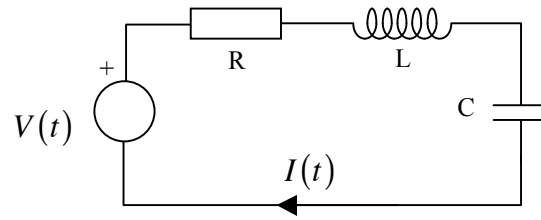

By applying Kirchhoff's voltage law around the loop we get:

$$V = V_R + V_L + V_C = IR + L \frac{dI}{dt} + \frac{1}{C} \int I dt = R \frac{dq}{dt} + L \frac{d^2q}{dt^2} + \frac{q}{C}$$

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = V_o \cos(\omega t)$$

For a simple mechanical forced harmonic oscillator:

$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = F(t)$$

displacement $x \Leftrightarrow q$

mass $m \Leftrightarrow L$

damping constant $b \Leftrightarrow R$

restoring force constant $k \Leftrightarrow \frac{1}{C}$

driving force $F(t) \Leftrightarrow V(t)$

9. V_o and ϕ essentially depend on the initial conditions, i.e. what is happening in the circuit at time $t=0$. Two conditions initial conditions are necessary to define V_o and ϕ . These might for instance be $V_o(0)$ and $dV_o/dt(0)$ or $V_L(0)$ and $V_R(0)$ or even $V_C(0)$ and $I(0)$.

For a series resonant circuit

$$\omega_o = \frac{1}{\sqrt{LC}} \quad Q = \frac{1}{\omega_o RC} = \frac{\omega_o L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\alpha = \frac{\omega_o}{2Q} = \frac{R}{2L} \quad \omega' = \omega_o \sqrt{1 - \frac{1}{4Q^2}} = \sqrt{\omega_o^2 - \frac{\omega_o^2}{4Q^2}} = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

For a parallel resonant circuit

$$\omega_o = \frac{1}{\sqrt{LC}} \quad Q = \omega_o RC = \frac{R}{\omega_o L} = R \sqrt{\frac{C}{L}}$$

$$\alpha = \frac{\omega_o}{2Q} = \frac{1}{2RC} \quad \omega' = \omega_o \sqrt{1 - \frac{1}{4Q^2}} = \sqrt{\omega_o^2 - \frac{\omega_o^2}{4Q^2}} = \sqrt{\frac{1}{LC} - \frac{1}{4R^2 C^2}}$$

Graph below shows of $V(t)$ for the case of $\omega=10$, $Q=10$, $V_o=1$ and $\phi=0$.

