

# Problem sheet 5, January 2005

Dr Mark Neil

The Electricity and Magnetism exam in the summer will carry questions from both the electronics and electromagnetism courses. There will be a compulsory section containing seven short questions (4 on electromagnetism, 3 on electronics) and second section of long problems where you will be required to answer two questions from a choice of four (3 on electromagnetism and 1 on electronics). Pay close attention to the wording of the questions and look for “key words” such as *derive* as these tell you what the examiner will be looking for in the answer. The exam is timed for 2 hours and the two sections are worth 50% of the marks each.

**No worked answer sheet will be provided for the questions below. You are encouraged to discuss your answers with other students on the course.**

1. **Short Exam Question Style, Should take 6 minutes max.** A simple series circuit containing a switch, a DC power supply with a constant output voltage  $V_o$ , a resistor  $R$  and a capacitor  $C$  is constructed. At a time before  $t = 0$  the capacitor is uncharged and the switch is open. At  $t = 0$  the switch is closed.

(i) *Derive* from first principles a differential equation that relates  $V_o$ ,  $R$  and  $C$  to the charge  $Q$  on the capacitor for all times after the switch is closed.


(ii) Find a general solution to the differential equation from part (i) that describes the voltage across the capacitor  $V_c(t)$  as a function of time.

2. **Short Exam Question Style.** A  $1000 \mu\text{F}$  capacitor is charged to  $1\text{kV}$  and then disconnected from the power supply. How long would it take for the voltage to fall to  $10\text{V}$  if the capacitor is slightly imperfect and has an internal resistance of  $10\text{M}\Omega$  between its two terminals.


3. **Short Exam Question Style.**

(i) State Kirchoff's voltage law as concisely as possible.

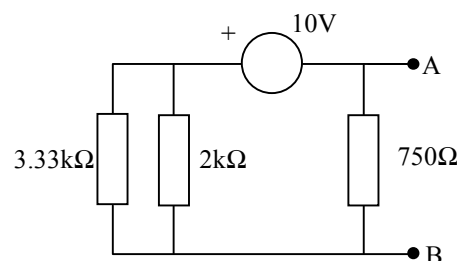(ii) Find a Thevenin equivalent circuit for the points A-B in the network shown opposite. How long would it take to charge a  $50 \mu\text{F}$  capacitor to  $2.37\text{V}$  if it was connected to the points A-B?



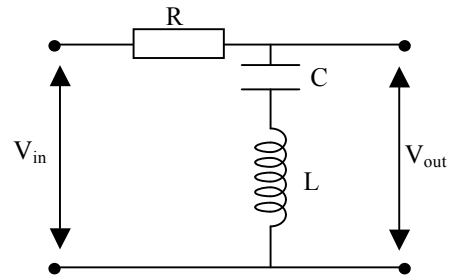4. **Half a long question, 15 minutes.** A “notch filter” can be constructed using a series RCL circuit as shown opposite. Derive an expression for  $V_{out}$  as a function of  $R$ ,  $C$ ,  $L$  and  $V_{in}$ . Use this to find an expression for the resonant frequency of the filter.




5. **Long Exam Question Style, Should take 30 minutes approx.**

- (i) Explain briefly why RMS voltages and currents are useful in AC power calculations. Under what condition does the simple relationship below between RMS and peak-to-peak voltage hold?

$$V_{RMS} = \frac{V_{P-P}}{2\sqrt{2}}$$

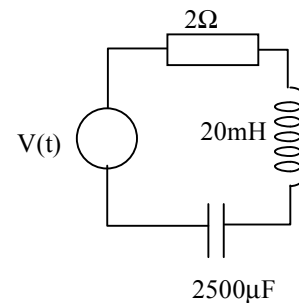- (i) Derive a general expression for the impedance  $Z_{total}$  of an RCL series circuit and write this in complex exponential form. Determine the value of the phase angle of  $Z_{total}$  in the circuit below for  $\omega = 200 \text{ rad s}^{-1}$  and draw a phasor diagram showing the relationship between  $\tilde{V}$ ,  $\tilde{I}$  and  $Z_{total}$



- (ii) Explain briefly what the power factor of a circuit is and give a value for the power factor of the circuit opposite.
- (iii) If the voltage source produces a signal  $V(t) = 15 \cos(200t)$  what is the average power dissipated in the circuit. Explain carefully where energy loss takes place in this circuit.