

3. The power supplied by the dc voltage source in the circuit shown below is



4. The current I supplied by the dc voltage source in the circuit shown below is



(A) 0A (B) 0.5A (C) 1A (D) 2A

5. For signal conditioning of a piezoelectric type transducer we require

- (A) a charge amplifier (B) a differential amplifier
- (C) an instrumentation amplifier (D) a transconductance amplifier
- 6. A linear variable differential transformer (LVDT) is
  - (A) a displacement transducer
  - (B) an impedance matching transformer
  - (C) a differential temperature sensor
  - (D) an auto transformer

- StudentBounty.com 7. The temperature being sensed by a negative temperature coefficient (NTC) thermistor is linearly increasing. Its resistance will
  - (A) linearly increase with temperature
  - (B) exponentially increase with temperature
  - (C) linearly decrease with temperature
  - (D) exponentially decrease with temperature
- 8. For a single stage BJT common base amplifier
  - (A) current gain as well as voltage gain can be greater than unity
  - (B) current gain can be greater than unity but voltage gain is always less than unity
  - (C) voltage gain can be greater than unity but current gain is always less than unity
  - (D) current gain as well as voltage gain is always less than unity
- 9. In the circuit shown below, the ideality factor nof the diode is unity and the voltage drop across it is 0.7V. The dynamic resistance of the diode at room temperature is approximately



- (A) 15Ω (C) 50Ω (B) 25Ω (D) 700 Ω
- 10. An ideal op-amp has the characteristics of an ideal
  - (A) voltage controlled voltage source
- (B) voltage controlled current source

www.

- (C) current controlled voltage source
- (D) current controlled current source
- 11. The inverters in the ring oscillator circuit shown below are identical. If the output waveform has a frequency of 10 MHz, the propagation delay pf each inverter is



- 12. A 2K×8 bit RAM is interfaced to an 8-bit microprocessor. If the address of the first memory location in the RAM is 0800H, the address of the last memory location will be
  - (A) 1000H (B) OFFFH (C) 2848H (D) 47FFH

IN Gate 2008

- The fundamental period of the discrete-time signal  $x[n] = e^{f(\frac{5\pi}{6})n}$  is 13.
- StudentBounty.com (A)  $\frac{6}{5\pi}$ (B)  $\frac{12}{5}$ (C) 6 (D)12
- Which one of the following discrete-time systems is time invariant? 14. (A) y[n] = nx[n](B) y[n] = x[3n] (C) y[n] = x[-n] (D) y[n] = x[n-3]
- If a current of  $\left|-6\sqrt{2}\sin(100\pi t)+6\sqrt{2}\cos(300\pi t)+\frac{\pi}{4}\right|$  A is passed through a true 15. RMS ammeter, the meter reading will be (A)  $6\sqrt{2}A$ (B) √126A (C) 12A (D) √216A
- 16. If the ac bridge circuit shown below is balanced, the element Z can be a (A) Pure capacitor
  - (B) Pure inductor
  - (C) R-L series combination
  - (D) R-L parallel combination

(A) 3 poles ands 1 zero



www

17. The Bode asymptotic plot of a transfer function is given below. In the frequency range shown, the transfer function has



- (B) 1 pole and 2 zeros
- (C) 2 poles and 1 zero
  - (D) 2 poles and 2 zeros
- For radioisotope imaging, an Anger camera is fitted with a parallel hole 18. collimator. If the thickness of the collimator is increased, the camera
  - (A) resolution and sensitivity will increase
  - (B) resolution and sensitivity will decrease
  - (C) resolution will increase and sensitivity will decrease
  - (D) resolution will decrease and sensitivity will increase

www.StudentBounty.com

GATEFORUM	IN	0 1 0000
Engineering Success		Gate 2008

StudentBounty.com 19. In the standard 12-lead ECG recording system, the minimum numb electrodes required to be attached to a human subject for recording any one the unipolar chest lead signals is

(A) 1 (B) 2 (C) 4 (D)5

20. A laser light with a wavelength of 633nm is passed through 1cm length of tissue and 2cm length of glass. The refractive indices of tissue ad glass are 1.33 ad 1.5 respectively. The velocities of laser light in the tissue and in the glass are in the ratio of

(A) 1.33:0.75 (B) 1.33:3.0 (C) 1.33:15 (D) 1.5: 1.33

Q. No. 21 – 75 Carry Two Marks Each

The expression  $e^{-\ln x}$  for x > 0 is equal to 21.

(A)

Consider the differential equation  $\frac{dy}{dx} = 1 + y^2$ . Which one of the following can be 22. a particular solution of this differential equation? (A) y = tan(x + 3)(B) y = tan x + 3(C) x = tan(y+3) (D) x = tan y + 3

- Consider the function  $y=x^2-6x+9$ . The maximum value of y obtained when x 23. varies over the interval 2 to 5 is (A) 1 (B) 3 (C) 4 (D)9
- It is known that two roots of the nonlinear equation  $x^3 6x^2 + 11x 6 = 0$  are 1 24. and 3. The third root will be
  - (A) j (B) - j (C) 2 (D) 4
- 25. Consider a Gaussian distributed random variable with zero mean and standard deviation  $\sigma$ . The value of its cumulative distribution function at the origin will be (A) 0 (B) 0.5 (C) 1 (D) 10σ
- A random variable is uniformly distributed over the interval 2 to 10. Its variance 26. will be
  - (A)  $\frac{16}{2}$ (C)  $\frac{256}{9}$ (B) 6 (D) 36
- 27. The Fourier transform of  $x(t) = e^{-at}u(-t)$ , where u(t) is the unit step function
  - (A) Exists for any real value of a
  - (B) Does not exist for any real value of a
  - (C) Exists if the real value of a is strictly negative
  - (D) Exists if the real value of a is strictly positive

## www.StudentBounty.com nework Help & Pasi

28. In the circuit shown below the maximum power that can be transferred load  $\rm Z_{\rm L}$  is

www.g



29. A complete variable Z = x + j0.1 has its real part x varying in the range  $-\infty$  to  $+\infty$ . Which one of the following is the locus (shown in thick lines) of 1/Z in the complex plane?







(A) 50W (B) 1050W (C) 5000W (D) 10100W

32. Which one of the following equations is valid for the circuit shown below?



- (A)  $I_3 + I_5 I_6 + I_7 = 0$ (B)  $I_3 - I_5 + I_6 + I_7 = 0$ (C)  $I_3 + I_5 + I_6 + I_7 = 0$ (D)  $I_3 + I_5 + I_6 - I_7 = 0$
- 33. For the circuit shown below the steady-state current I is



34. For the circuit shown below the voltage across the capacitor is



- 35. The speed of a gear having 60 teeth is measured using a proximity sensor. The output of the proximity sensor is fed to a counter with a gating time of 1s. The counter indicates a value of 120. The speed at which the gear is rotating is (A) 60 rpm (B) 120 rpm (C) 600 rpm (D) 1200 rpm
- 36. A piezoelectric type accelerometer has a sensitivity of 100mV/g. The transducer is subjected to a constant acceleration of 5g. The steady state output of the transducer will be

(A)	OV	(B) 100mV	(C) 0.5V	(D)5V
• •		• •		• •

37. A pair of identical thermocouples is employed for measuring the temperature of a specimen as shown below. The characteristic is tabulated below. The reference junction is at  $2^{\circ}$ C. The meter reads  $48 \,\mu$ V. The correct temperature of the specimen is



Temperature ( <sup>0</sup> C)	0	10	20	30	40	50	60	70	80	90
Output ( µV )	35	45	55	65	75	85	95	105	115	125

- (A) 13<sup>0</sup>C (B) 46<sup>0</sup>C (C) 48<sup>0</sup>C (D)  $50^{\circ}C$
- 38. A strain gauge has a nominal resistance of  $600 \Omega$  and a gauge factor of 2.5. The strain gauge is connected in a dc bridge with three other resistances of  $600\,\Omega$ each. The bridge is excited by a 4V battery. If the strain gauge is subjected to a strain of  $100 \,\mu\text{m}/\text{m}$ , the magnitude of the bridge output will be
  - (A) 0V (B) 250µV (C) 500µV (D) 750µV



StudentBounty.com 39. The torque in a rotating shaft is measured using strain gauges. The strain o must be positioned on the shaft such that the axes of the strain gauges are at

www.

- (A)  $0^{0}$  with respect to the axis of the shaft
- (B)  $30^{\circ}$  with respect to the axis of the shaft
- (C) 45° with respect to the axis of the shaft
- (D)  $90^{\circ}$  with respect to the axis of the shaft
- 40. To reduce the effect of fringing in a capacitive type transducer
  - (A) the transducer is shielded and the shield is kept at ground potential
  - (B) a guard ring is provided ad it is kept at ground potential
  - (C) the transducer is shielded and the shied is kept at the same potential as the moving plate
  - (D) a guard ring is provided and it is kept at the same potential as the moving plate
- A differential amplifier shown below has a differential mode gain of 100 and a 41. CMRR of 40dB. If  $V_1 = 0.55V$  and  $V_2 = 0.45V$ , the output  $V_0$  is



The op-amp circuit shown below is that of a 42.



- (A) low-pass filter with a maximum gain of 1
- (B) low-pass filter with a maximum, gin of 2
- (C) high-pass filter with a maximum gain of 1
- (D) high-pass filter with a maximum gain of 2

StudentBounty.com 43. In the op-amp circuit shown below is that of a v<sub>in</sub> is gradually increased from to +10V. Assuming that the output voltage  $v_{out}$  saturates at -10V and +10V,



(B) -10V to +10V when  $v_{in} = +1V$ (D) +10V to -10V when  $v_{in} = +1V$ 

www.g

For the op-amp circuit shown below  $v_0$  is approximately equal to 44.





In the amplifier circuit shown below, assume  $\,V_{BE}^{}=0.7V\,$  and the  $\,\beta\,$  of the transistor and the values of  $\rm C_1$  and  $\rm C_2$  are extremely high. If the amplifier is designed such that at the quiescent point its  $V_{CE} = \frac{V_{CC}}{2}$ , where  $V_{CC}$  is the power supply voltage, its small signal voltage gain  $\frac{V_{out}}{V_{in}}$  will be 8.8kΩ



www.StudentBounty.com

- 46. The result of  $(45)_{10} - (45)_{16}$  expressed in 6-bit 2's complement representation (A) 011000 (B) 100111 (C) 101000 (D) 101001
- StudentBounty.com 47. The output F of the multiplexer circuit shown below expressed in terms of the inputs P, Q and R is

www



(B) F = PQ + QR + RP (C)  $F = (P \oplus Q)R$  (D)  $F = (P \oplus Q)\overline{R}$ (A)  $F = P \oplus Q \oplus R$ 

A part of a program written for an 8085 microprocessor is shown below. When 48. the program execution reaches LOOP2, the value of register C will be

- 49. The minimum sum of products form of the Boolean expression  $Y = \overline{P} \overline{O} \overline{R} \overline{S} + P \overline{O} \overline{R} \overline{S} + P \overline{O} \overline{R} S + P \overline{O} R S + P \overline{O} R \overline{S} + \overline{P} \overline{O} R \overline{S}$ is (A)  $Y = P \overline{Q} + \overline{Q} \overline{S}$  (B)  $Y = P \overline{Q} + \overline{Q} R \overline{S}$  (C)  $Y = P \overline{Q} + \overline{Q} R \overline{S}$  (D)  $Y = \overline{Q} \overline{S} + \overline{P} \overline{Q} R$
- 50. An X-ray tube is operated at 80kV anode voltage. In order to filter the low intensity X-rays, a 2.5mm thick aluminium filter is used. It is given that at 80kV anode voltage, the mass attenuation coefficients and densities of aluminium are  $0.02m^{2}ka^{-1}$  and  $2699kam^{-3}$ respectively and for copper these are 0.075m<sup>2</sup>kg<sup>-1</sup> and 8960 kgm<sup>-3</sup> respectively. If a copper filter is to replace the aluminium filter with the same effect, the thickness of the copper filter should be (A) 0.2mm (B) 0.66mm (C) 1.5mm (D) 5mm

StudentBounty.com A 5 MHz acoustic pulse travels from a transducer through a 2cm thick fat 51. before it encounters ad interface with a liver tissue at normal incidence. attenuation amplitude factors of fat and 0.075 Npcm<sup>-1</sup> / MHz and 0.1 Npcm<sup>-1</sup> / MHz respectively. The amplitude reflectivity coefficient of fat-liver interface is 0.1. Taking both attenuation and reflection losses into a account, the amplitude loss (in dB) of echo pulse when it returns to the transducers is

www.g

(C) -6 (A) 0.74 (B) -2.6 (D) - 33

- Consider a discrete-time LTI system with input  $x[n] = \delta[n] + \delta[n-1]$  and impulse 52. response  $h[n] = \delta[n] - \delta[n - 1]$ . The output of the system will be given by
  - (B)  $\delta[n] \delta[n-1]$ (A)  $\delta[n] - \delta[n-2]$ (D)  $\delta[n] + \delta[n-1] + \delta[n-2]$ (C)  $\delta[n-1] + \delta[n-2]$
- 53. Consider a discrete-time system for which the input x[n] and the output y[n] are related as  $y[n] = x[n] - \frac{1}{3}y[n-1]$ . If y[n] = 0 for n < 0 and  $x[n] = \delta[n]$ , then y[n]can be expressed in terms of the unit step u[n] as
  - (A)  $\left(\frac{-1}{3}\right)^{n} u[n]$  (B)  $\left(\frac{1}{3}\right)^{n} u[n]$  (C)  $(3)^{n} u[n]$  (D)  $(-3)^{n} u[n]$

If the bandwidth of a low-pass signal g(t) is 3kHz, the bandwidth of  $g^{2}(t)$  will be 54.

- (A)  $\frac{3}{2}$ kHz (B) 3kHz (C) 6kHz (D) 9kHz
- 55. Consider the AM signal  $s(t) = [1 + m(t)] cos(2\pi f_c t)$ . It is given that the bandwidth of the real, low-pass message signal m(t) is 2kHz. If  $f_c = 2MHz$ , the bandwidth of the band-pass signal s(t) will be (A) 2.004MHz (B) 2MHz (C) 4kHz (D) 2kHz
- Ten, real, band-pass message signals, each of bandwidth 3kHz, are to be 56. frequency division multiplexed over a band-pass channel with bandwidth B kHz. If the guard band in between any two adjacent signals should be of 500 Hz width and there is no need to provide any guard band at the edges of the band-pass channel, the value of B should be at least
  - (A) 30 (B) 34.5 (C) 35 (D) 35.5
- The region of convergence of the z-transform of the discrete-time signal 57.  $x[n] = 2^n u[n]$  will be
  - (A) |z| > 2 (B) |z| < 2 (C)  $|z| > \frac{1}{2}$  (D)  $|z| < \frac{1}{2}$

StudentBounty.com The step response of a linear invariant system is  $y(t) = 5e^{-10t}u(t)$ , where 58. the unit step function. If the output of the system corresponding to an impul input  $\delta(t)$  is h(t), then h(t) is

www.

- (A)  $-50e^{-10t}u(t)$ (B)  $5e^{-10t}\delta(t)$ (C)  $5u(t) - 50e^{-10t}\delta(t)$ (D)  $5\delta(t) - 50e^{-10t}u(t)$
- 59. A 2A full-scale PMMC type dc ammeter has a voltage drop of 100 mV at 2A. The meter can be converted into a 10A full-scale dc ammeter by connecting a
  - (A) 12.5 m $\Omega$  resistor in parallel with the meter
  - (B)  $12.5 \text{ m}\Omega$  resistor in series with the meter
  - (C) 50.0 m $\Omega$  resistor in parallel with the meter
  - (D) 50.0 m $\Omega$  resistor in series with the meter
- 60. A 3½ digit, 200 mV full scale DVM has an accuracy specification of  $\pm 0.5\%$  of reading plus 5 counts. When the meter reads 100 mV, the voltage being measured is
  - (A) Any value between 99.5 mV and 100.5 mV
  - (B) Any value between 99.0 mV and 101.0 mV
  - (C) Exactly 99.5 mV (D) Exactly 100 mV
- A 230 V, 5A, 50 Hz single phase house service energy meter has a meter 61. constant of 360 rev/kWhr. The meter takes 50 s for making 51 revolutions of the disc when connected to a 10 kW, unity power factor load. The error in the reading of the meter is
  - (A) 0% (B) +0.5% (C) -2.0% (D) + 2.0%
- The op-amp based circuit of a half wave rectifier electronic voltmeter shown 62. below uses a PMMC ammeter with a full scale deflection (FSD) current of 1 mA and a coil resistance of  $1k\Omega$ . The value of R that gives FSD for a sinusoidal input voltage of 100 mV (RMS) is



www.Student	Bounty.com
Homework Hel	p & Pastpapers

mand for the former of the for 63. The x and y sensitivities of an analog oscilloscope are set as 2 ms/cm and respectively. The trigger is set at OV with negative slope. An input  $2\cos(100\pi t + 30^{\circ})V$  is fed to the y input of the oscilloscope. The waveform seen on the oscilloscope will be



- 64. The transfer function of a unity feedback open loop system is  $G(s) = \frac{K(s+2)}{(s+1+j1)(s+1-j1)}$ . The root locus plot of the system has
  - (A) two breakaway points located at s = -0.59 and s = -3.41
  - (B) one breakaway point located at s = -0.59
  - (C) one breakaway point located at s = -3.41
  - (D) one breakaway point located at s = -1.41
- 65. If a first order system and its time response to a unit step input are as shown below, the gain K is



The state space representation of a system is given by  $\begin{array}{c} x &= \begin{bmatrix} 0 & 1 \\ 0 & -3 \end{bmatrix} x + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u \\ y &= \begin{bmatrix} 1 & 0 \end{bmatrix} x$ 66.

The transfer function  $\frac{Y(s)}{U(s)}$  of the system will be

(B)  $\frac{1}{s(s+3)}$  (C)  $\frac{1}{s+3}$  (D)  $\frac{1}{s^2}$ (A)  $\frac{1}{s}$ 

# www.StudentBounty.com

StudentBounty.com 67. A closed loop control system is shown below. The range of the controller ga which will make the real parts of all the closed loop poles more negative than is



For the closed loop system shown below to be sable, the value of time delay 68.  $T_D$  (in seconds) should be less than



69. A tissue with a refractive index 1.33 is introduced on one of the light paths of a Michelson interferometer operating with a monochromatic coherent light source of wavelength 589nm. After the introduction of a tissue sample of thickness  $\Delta t$ , the fringe pattern is observed to shift by 50 fringes. If the thickness is  $2\Delta t$ , the fringe pattern will shift by

(A) 25 fringes (B) 50 fringes (C) 100 fringes (D) 200 fringes

- 70. In the process of non-destructive testing of a 10cm diameter cylinder, a crosssectional (trans-axial) image of the cylinder is reconstructed with the help of parallel beam computer tomography technique. To realize a spatial resolution of 1mm in the image, the minimum number of ray sample in each projection set and the minimum number of projection sets required are
  - (A) 200 and 315 respectively
  - (C) 200 and 629 respectively
- (B) 100 and 315 respectively

www.g

(D) 100 and 629 respectively

Common Data Questions 71, 72 & 73

A data acquisition system (DAS) shown below employs a successive approximation type 12-bit ADC having a conversion time of 5 µs.





- 73. If the multiplexer is controlled such that the channels are sequenced every 5  $\mu$ s as 1, 2, 1, 3, 1, 4, 1, 2, 1, 3, 1, 4, 1...., the input connected to channel 1 will be sampled at the rate of
  - (A) 25k samples/s (B) 50k samples/s
  - (C) 100k samples/s (D) 200k samples/s

# Common Data Questions: 74 & 75

Laser light is generated by energizing helium-neon gas in a chamber. The ground and metastable states of helium are 0eV and 20.61eV respectively. The ground, higher and metastable energies of neon is 0eV, 18.70eV and 20.66eV respectively. The values of speed of light, Planks constant and charge of electron are  $3 \times 10^8$  m/s,  $6.625 \times 10^{-34}$  Js and  $1.6 \times 10^{-19}$ C respectively

- 74. In this process, helium molecules
  - (A) play no role
  - (B) produce laser light
  - (C) give energy to neon molecules
  - (D) absorb energy from neon molecules
- 75. Wavelength of laser light generated in this process is
  - (A) 61.6nm (B) 66.4nm (C) 633.8nm (D) 650.3nm

Linked Answer Questions: Q.76 to Q.85 Carry Two Marks Each

Statement for Linked Answer Questions: 76 & 77

In the Wheatstone bridge shown below the galvanometer G has a current sensitivity of  $1 \mu A / mm$ , a resistance of  $2.5 k\Omega$  and a scale resolution of 1 mm. Let  $\Delta R$  be the minimum increase in R from its nominal value of  $2 k\Omega$  that can be detected by this bridge.





Statement for Linked Answer Questions 78 & 79

In the circuit shown below the steady-state is reached with the switch K open. Subsequently the switch is closed at time t = 0



78. At time  $t = 0^+$ , current I is

(A) 
$$-\frac{5}{3}A$$
 (B) OA (C)  $\frac{5}{3}A$  (D)  $\infty A$ 

79. At time 
$$t = 0^+$$
,  $\frac{dI_2}{dt}$  is  
(A) -5A/s (B)  $-\frac{10}{3}$ A/s (C) 0A/s (D) 5A/s